

SOLUTIONS MANUAL

MICROWAVE TRANSISTOR AMPLIFIERS

Analysis and Design

SECOND EDITION

Guillermo Gonzalez



PRENTICE HALL
Upper Saddle River, NJ 07458

Acquisitions Editor: *Eric Svendsen*
Project Editor: *Lorena Cerisano*
Production Manager: *Joan Eurell*
Production Coordinator: *Julia Meehan*

©1996 by Prentice-Hall, Inc.
Simon & Schuster / A Viacom Company
Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced, in any form or by any means, without permission in writing from the publisher.

Printed in the United States of America

10 9 8 7 6 5 4 3 2 1

ISBN 0-13-271255-5

Prentice-Hall International (UK) Limited, *London*
Prentice-Hall of Australia Pty. Limited, *Sydney*
Prentice-Hall Canada Inc., *Toronto*
Prentice-Hall Hispanoamericana, S.A., *Mexico*
Prentice-Hall of India Private Limited, *New Delhi*
Prentice-Hall of Japan, Inc., *Tokyo*
Simon & Schuster Asia Pte. Ltd., *Singapore*
Editora Prentice-Hall do Brasil, Ltda., *Rio de Janeiro*

CONTENTS

CHAPTER	1	page 1
CHAPTER	2	page 19
CHAPTER	3	page 42
CHAPTER	4	page 71
CHAPTER	5	page 88

CHAPTER 1

1.1) IN (1.3.41) LET $\Gamma_0 = |\Gamma_0| e^{j\psi_0}$:

$$|V(d)| = |A_1| |1 + |\Gamma_0| e^{j(\psi_0 - 2\beta d)}|$$

THE MAXIMUM VALUE OF $|V(d)|$ OCCURS WHEN $e^{j(\psi_0 - 2\beta d)} = 1$,
AND THE MINIMUM VALUE OCCURS WHEN $e^{j(\psi_0 - 2\beta d)} = -1$.

HENCE,

$$\begin{aligned} |V(d)|_{\max} &= |A_1| |1 + |\Gamma_0|| \quad \text{AND} \quad |V(d)|_{\min} = |A_1| |1 - |\Gamma_0|| \\ &= |A_1| (1 + |\Gamma_0|) \quad \quad \quad = |A_1| (1 - |\Gamma_0|) \end{aligned}$$

1.2) $v(d, t) = \operatorname{Re}[V(d) e^{j\omega t}]$

$$V(d) = 3.95 e^{j(\beta d - 63.44^\circ)} + 1.77 e^{-j\beta d}$$

$$\therefore v(d, t) = 3.95 \cos(\omega t + \beta d - 63.44^\circ) + 1.77 \cos(\omega t - \beta d)$$

$$\text{AND } i(d, t) = \frac{3.95}{50} \cos(\omega t + \beta d - 63.44^\circ) - \frac{1.77}{50} \cos(\omega t - \beta d)$$

1.3) (a) $\Gamma_0 = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{(100 + j100) - 50}{(100 + j100) + 50} = 0.62 \angle 29.7^\circ$

$$Z_{IN}\left(\frac{\lambda}{8}\right) = 50 \frac{(100 + j100) \cos 45^\circ + j50 \sin 45^\circ}{50 \cos 45^\circ + j(100 + j100) \sin 45^\circ} = 40 - j70 \Omega$$

$$\text{VSWR} = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|} = \frac{1 + 0.62}{1 - 0.62} = 4.26$$

(b)

$$V\left(\frac{\lambda}{8}\right) = \frac{1010}{40 - j70 + 100} = 5.15 \angle -33.7^\circ$$

$$I\left(\frac{\lambda}{8}\right) = V\left(\frac{\lambda}{8}\right) / Z_{IN}\left(\frac{\lambda}{8}\right) = 0.064 \angle 26.6^\circ$$

$$P\left(\frac{\lambda}{8}\right) = \frac{1}{2} \operatorname{Re}[V\left(\frac{\lambda}{8}\right) I^*\left(\frac{\lambda}{8}\right)] = 82 \text{ mW}$$

$$V\left(\frac{\lambda}{8}\right) = 5.15 \angle -33.7^\circ = A_1 e^{j\frac{\pi}{4}} [1 + 0.62 \angle 29.7^\circ e^{-j\frac{\pi}{4}}]$$

$$\therefore A_1 = 3.643 \angle -56.31^\circ$$

$$V(d) = 3.643 \underbrace{[-56.31^\circ]}_{e^{j\beta d}} [1 + 0.62 \underbrace{[29.7^\circ]}_{e^{-j^2\beta d}}]$$

$$V(0) = 3.643 \underbrace{[-56.31^\circ]}_{e^{j\beta d}} [1 + 0.62 \underbrace{[29.7^\circ]}_{e^{-j^2\beta d}}] = 5.72 \underbrace{[-45.02^\circ]}_{e^{-j^2\beta d}}$$

$$I(0) = \frac{5.72 \underbrace{[-45.02^\circ]}_{e^{-j^2\beta d}}}{100 + j100} = 0.04 \underbrace{[-90^\circ]}_{e^{-j^2\beta d}}$$

$$P(0) = \frac{1}{2} \operatorname{Re}[V(0) I^*(0)] = 82 \text{ mW}$$

$$\text{As EXPECTED: } P\left(\frac{\lambda}{8}\right) = P(0)$$

$$1.4) \quad b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

$$\text{LETTING } Z_o = Z_{o1} = Z_{o2}, \text{ THEN } b_1 = \frac{V^-_1}{\sqrt{Z_o}}, b_2 = \frac{V^-_2}{\sqrt{Z_o}}, \\ a_1 = \frac{V^+_1}{\sqrt{Z_o}}, \text{ AND } a_2 = \frac{V^+_2}{\sqrt{Z_o}}.$$

$$\therefore \frac{V^-_1}{\sqrt{Z_o}} = S_{11} \frac{V^+_1}{\sqrt{Z_o}} + S_{12} \frac{V^+_2}{\sqrt{Z_o}} \Rightarrow V^-_1 = S_{11} V^+_1 + S_{12} V^+_2$$

$$\frac{V^-_2}{\sqrt{Z_o}} = S_{21} \frac{V^+_1}{\sqrt{Z_o}} + S_{22} \frac{V^+_2}{\sqrt{Z_o}} \Rightarrow V^-_2 = S_{21} V^+_1 + S_{22} V^+_2$$

$$\text{WITH } b_1 = \sqrt{Z_o} I^-_1, b_2 = \sqrt{Z_o} I^-_2, a_1 = \sqrt{Z_o} I^+_1, a_2 = \sqrt{Z_o} I^+_2$$

$$\text{WE OBTAIN: } I^-_1 = S_{11} I^+_1 + S_{12} I^+_2$$

$$I^-_2 = S_{21} I^+_1 + S_{22} I^+_2$$

$$1.5) \quad \begin{cases} a_1 = T_{11} b_1 + T_{12} b_2 & (1) \\ b_1 = T_{21} b_2 + T_{22} b_2 & (2) \end{cases}$$

$$\begin{cases} b_1 = S_{11} a_1 + S_{12} a_2 & (3) \\ b_2 = S_{21} a_1 + S_{22} a_2 & (4) \end{cases}$$

FROM (3) AND (4):

$$a_1 = \frac{1}{S_{11}} b_1 - \frac{S_{12}}{S_{11}} a_2 \quad (5)$$

$$a_1 = \frac{1}{S_{21}} b_2 - \frac{S_{22}}{S_{21}} a_2 \quad (6)$$

EQUATING (5) AND (6):

$$\frac{1}{S_{11}} b_1 - \frac{S_{12}}{S_{11}} a_2 = \frac{1}{S_{21}} b_2 - \frac{S_{22}}{S_{21}} a_2$$

$$\therefore b_1 = \frac{S_{11}}{S_{21}} b_2 + \left[S_{12} - \frac{S_{11} S_{22}}{S_{21}} \right] a_2 \quad (7)$$

COMPARING (2) AND (7):

$$T_{21} = \frac{S_{11}}{S_{21}} \quad \text{AND} \quad T_{22} = S_{12} - \frac{S_{11} S_{22}}{S_{21}}$$

EQUATING (3) AND (7) GIVES

$$S_{11} a_1 + S_{12} a_2 = \frac{S_{11}}{S_{21}} b_2 + \left[S_{12} - \frac{S_{11} S_{22}}{S_{21}} \right] a_2$$

$$\therefore a_1 = \frac{1}{S_{21}} b_2 - \frac{S_{22}}{S_{21}} a_2 \quad (8)$$


COMPARING (1) AND (8):

$$T_{11} = \frac{1}{S_{21}} \quad \text{AND} \quad T_{12} = - \frac{S_{22}}{S_{21}}$$


SIMILARLY, STARTING WITH (1) AND (2), IT FOLLOWS
THAT:

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \begin{bmatrix} \frac{T_{21}}{T_{11}} & T_{22} - \frac{T_{12} T_{21}}{T_{11}} \\ \frac{1}{T_{11}} & -\frac{T_{12}}{T_{11}} \end{bmatrix}$$

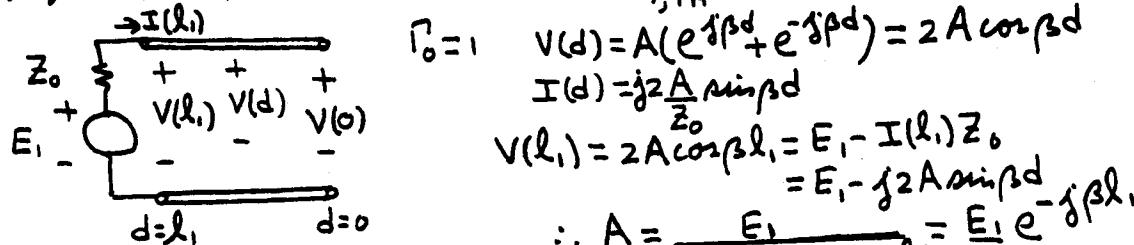1.6) THE OPEN-CIRCUIT VOLTAGE $E_{1,TH}$ IS OBTAINED AS FOLLOWS:



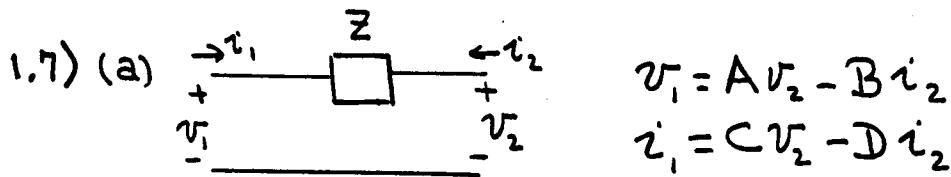HENCE: $E_{1,TH} = V(0) = 2A = E_1 e^{-j \beta l_1}$



$$A = \left. \frac{v_1}{v_2} \right|_{i_2=0}$$

With $i_2 = 0$: $v_1 = v_2$
 $\therefore A = 1$

$$B = \left. -\frac{v_1}{i_2} \right|_{v_2=0}$$

With $v_2 = 0$: $v_1 = i_1 Z = -i_2 Z$
 $\therefore B = -\frac{(-i_2 Z)}{i_2} = Z$

$$C = \left. \frac{i_1}{v_2} \right|_{i_2=0}$$

With $i_2 = 0$: $i_1 = -i_2 = 0$
 $\therefore C = 0$

$$D = \left. \frac{i_1}{v_2} \right|_{v_2=0}$$

With $v_2 = 0$: $i_1 = -i_2$
 $\therefore D = 1$

(b) From Fig. 1.8.1:

$$S_{11} = \frac{A' + B' - C' - D'}{A' + B' + C' + D'} = \frac{1 + \frac{Z}{Z_0} - 0 - 1}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{Z}{Z + 2Z_0}$$

$$S_{12} = \frac{2(A'D' - B'C')}{A' + B' + C' + D'} = \frac{2(1 - 0)}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{2Z_0}{Z + 2Z_0}$$

$$S_{21} = \frac{2}{A' + B' + C' + D'} = \frac{2}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{2Z_0}{Z + 2Z_0}$$

$$S_{22} = \frac{-A' + B' - C' + D'}{A' + B' + C' + D'} = \frac{-1 + \frac{Z}{Z_0} - 0 + 1}{1 + \frac{Z}{Z_0} + 0 + 1} = \frac{Z}{Z + 2Z_0}$$

FOR THE SHUNT ADMITTANCE Y THE ABCD MATRIX IS :

$$A = 1, B = 0, C = Y, \text{ AND } D = 1$$

AND


$$S_{11} = \frac{A' + B' - C' - D'}{A' + B' + C' + D'} = \frac{1 + 0 - YZ_0 - 1}{1 + 0 + YZ_0 + 1} = \frac{-YZ_0}{2 + YZ_0}$$

$$S_{12} = \frac{2(A'D' - B'C')}{A' + B' + C' + D'} = \frac{2(1 - 0)}{1 + 0 + YZ_0 + 1} = \frac{2}{2 + YZ_0}$$

$$\text{Also: } S_{22} = S_{11} \text{ AND } S_{21} = S_{12}$$

1.8) IN A Z_0 SYSTEM:

$$Z_{T1} = Z_0$$

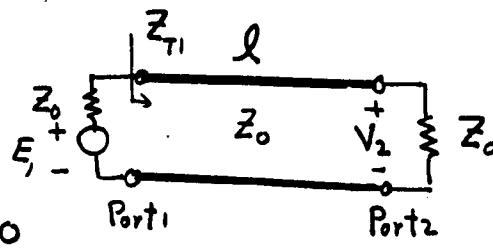

$$S_{11} = \frac{Z_{T1} - Z_0}{Z_{T1} + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$$

ALSO (FROM SYMMETRY): $S_{22} = 0$

$$S_{21} = 2 \frac{\sqrt{Z_0}}{\sqrt{Z_0}} \frac{V_2}{E_1} = 2 \frac{V_2}{E_1} . \text{ SINCE } V(x) = \frac{E_1}{2} e^{-j\beta x}$$

$$\therefore S_{21} = 2 \left(\frac{E_1}{2} e^{-j\beta l} \right) = e^{-j\beta l} \quad V_2 = V(l) = \frac{E_1}{2} e^{-j\beta l}$$

ALSO (FROM SYMMETRY): $S_{12} = e^{-j\beta l}$

AN ALTERNATE WAY OF DERIVING S_{21} IS:

$$S_{21} = \frac{b_2}{a_1} \quad \begin{array}{l} \text{SINCE } b_2 \text{ IS THE WAVE AT PORT 2 AND} \\ a_1 \text{ IS THE WAVE AT PORT 1, WE HAVE:} \end{array}$$

$$b_2 = a_1 e^{-j\beta l} \quad (a_2=0)$$

$$\therefore S_{21} = \frac{b_2}{a_1} = e^{-j\beta l}$$

$$T = \begin{bmatrix} \frac{1}{S_{21}} & -\frac{S_{22}}{S_{21}} \\ \frac{S_{11}}{S_{21}} & S_{12} - \frac{S_{11}S_{22}}{S_{21}} \end{bmatrix} = \begin{bmatrix} e^{j\beta l} & 0 \\ 0 & e^{-j\beta l} \end{bmatrix}$$


1.9)

$$\Rightarrow \quad Y = \frac{1}{Z_{oc}} = \frac{1}{-jZ_0 \cot \beta l} = jY_0 \tan \beta l$$

$$S_{11} = S_{22} = \frac{-Z_0 Y}{2 + Z_0 Y} = \frac{-1}{1 - j2 \cot \beta l}$$

$$S_{12} = S_{21} = \frac{2}{2 + Z_0 Y} = \frac{2}{2 + j \tan \beta l}$$

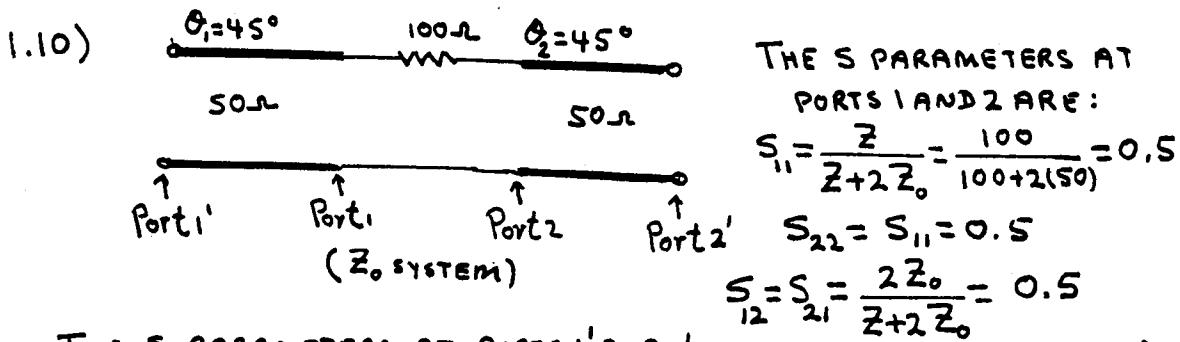
USE (1.4.11) TO EVALUATE THE T PARAMETERS.



THE S PARAMETERS AT PORTS 1' AND 2' ARE OBTAINED USING (1.5.4):

$$S'_{11} = S'_{22} = S_{11} e^{-j\theta_2} = 0.5 | -90^\circ = -j0.5$$

$$S'_{21} = S'_{12} = S_{21} e^{-j(\theta_1 + \theta_2)} = 0.5 | -90^\circ = -j0.5$$

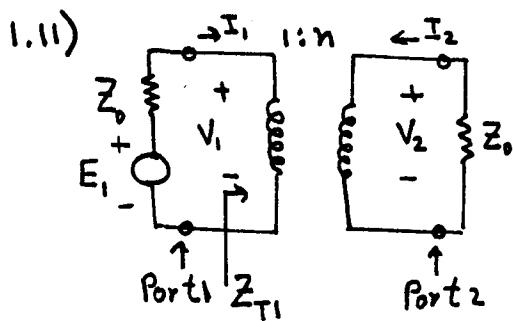

IN THE Z_0 SYSTEM SHOWN, THE PARAMETERS S_{11} AND S_{21} ARE CALCULATED AS FOLLOWS:

$$I_2 = \frac{I_1}{n}, V_2 = V_1 n$$

$$Z_{T1} = \frac{V_1}{I_1} = \frac{V_2}{I_2 n} = \frac{Z_0}{n^2}$$

$$S_{11} = \left| \frac{b_1}{a_1} \right|_{a_2=0} = \frac{Z_{T1} - Z_0}{Z_{T1} + Z_0} = \frac{\frac{Z_0}{n^2} - Z_0}{\frac{Z_0}{n^2} + Z_0} = \frac{1-n^2}{1+n^2}$$


$$S_{21} = 2 \sqrt{\frac{Z_{02}}{Z_{01}}} \frac{V_2}{E_1} = 2 \frac{V_2}{E_1} \quad (1)$$

$$V_1 = \frac{E_1 Z_{T1}}{Z_{T1} + Z_0} = \frac{E_1 \frac{Z_0}{n^2}}{\frac{Z_0}{n^2} + Z_0} = \frac{E_1}{n^2 + 1}$$

$$V_2 = n V_1 = \frac{n E_1}{n^2 + 1} \quad \text{OR} \quad \frac{V_2}{E_1} = \frac{n}{n^2 + 1} \quad (2)$$

(2) INTO (1):

$$S_{21} = \frac{2n}{n^2 + 1}$$

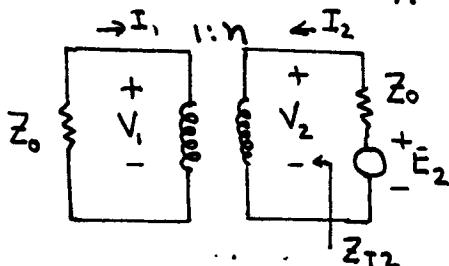

THE PARAMETERS S_{22} AND S_{12} ARE CALCULATED AS FOLLOWS:

$$Z_{T2} = Z_0 n^2$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \frac{Z_{T2} - Z_0}{Z_{T2} + Z_0} = \frac{n^2 Z_0 - Z_0}{n^2 Z_0 + Z_0} = \frac{n^2 - 1}{n^2 + 1}$$

$$S_{12} = 2 \frac{V_1}{E_2} \quad (3)$$

$$V_2 = \frac{E_2 Z_{T2}}{Z_{T2} + Z_0} = \frac{E_2 Z_0 n^2}{Z_0 n^2 + Z_0} = \frac{E_2 n^2}{n^2 + 1}$$

$$V_1 = \frac{V_2}{n} = \frac{E_2 n}{n^2 + 1} \quad \text{OR} \quad \frac{V_1}{E_2} = \frac{n}{n^2 + 1} \quad (4)$$


(4) INTO (3):

$$S_{12} = \frac{2n}{n^2 + 1}$$

AT PORTS 1' AND 2', WITH $\theta = \theta_1 = \theta_2$, WE OBTAIN:

$$[S'] = \begin{bmatrix} S_{11} e^{-j2\theta} & S_{12} e^{-j2\theta} \\ S_{21} e^{-j2\theta} & S_{22} e^{-j2\theta} \end{bmatrix} = e^{-j2\theta} \begin{bmatrix} \frac{1-n^2}{1+n^2} & \frac{2n}{n^2+1} \\ \frac{2n}{n^2+1} & \frac{n^2-1}{n^2+1} \end{bmatrix}$$

1.12)

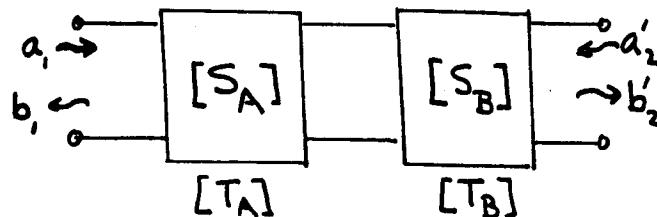

[T] AND [S]
PARAMETERS ARE
RELATED BY (1.4.11)

FROM (1.4.13):

$$\begin{bmatrix} a_1 \\ b_1 \end{bmatrix} = \begin{bmatrix} T_{11}^A & T_{12}^A \\ T_{21}^A & T_{22}^A \end{bmatrix} \begin{bmatrix} T_{11}^B & T_{12}^B \\ T_{21}^B & T_{22}^B \end{bmatrix} \begin{bmatrix} b'_2 \\ a'_2 \end{bmatrix}$$


OVERALL T_{11} IS: $T_{11} = T_{11}^A T_{11}^B + T_{12}^A T_{21}^B$

$$T_{11} = \frac{1}{S_{21}^A} \frac{1}{S_{21}^B} + \left(-\frac{S_{22}^A}{S_{21}^A} \right) \left(\frac{S_{11}^B}{S_{21}^B} \right)$$

$$\text{SINCE } T_{11} = \frac{1}{S_{21}} = \frac{1 - S_{22}^A S_{21}^B}{S_{21}^A S_{21}^B} \Rightarrow S_{21} = \frac{S_{21}^A S_{21}^B}{1 - S_{22}^A S_{11}^B}$$

$$1.13) (a) \Gamma_0 = \frac{100 - 50}{100 + 50} = \frac{1}{3}, \text{ VSWR} = \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = 2$$

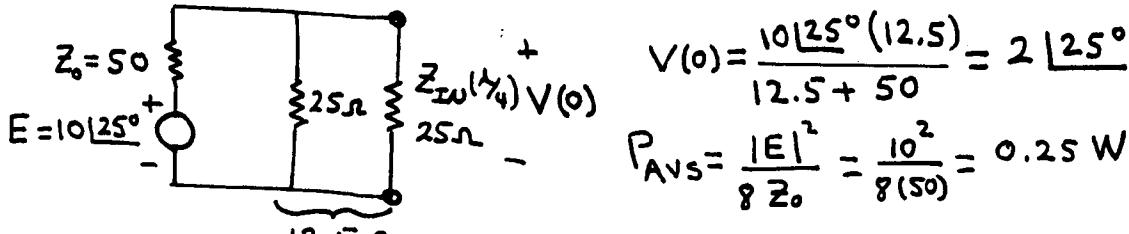
$$(b) Z_{IN}(\lambda_4) = \frac{\Gamma_0^2}{Z_L} = \frac{50^2}{100} = 25 \Omega$$



$$\text{THE INPUT POWER IS: } P_{IN} = \frac{(V(0))_{rms}^2}{12.5} = \frac{\left(\frac{2}{\sqrt{2}}\right)^2}{12.5} = 0.16 \text{ W}$$

SINCE THE TRANSMISSION LINE IS LOSSLESS, THE POWER DELIVERED TO THE LOAD (P_L) IS THE SAME AS P_{IN} .
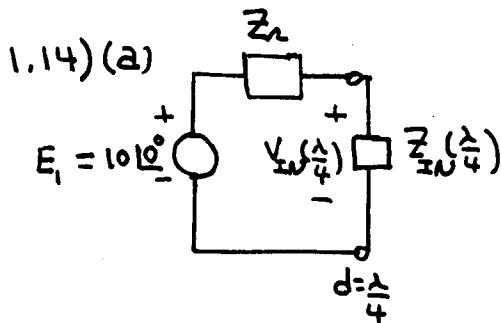
$$\therefore P_L = P_{IN} = 0.16 \text{ W}$$



$$Z_{IN}(\lambda/4) = \frac{Z_0^2}{Z_L} = \frac{50^2}{50+j50} = 25-j25$$

NOTE: IF Z_L IS GIVEN, THE VALUE OF Z_{IN} FOR MAXIMUM POWER IS

$$Z_{IN} = Z_L^*$$

HOWEVER, IN THIS PROBLEM Z_{IN} IS GIVEN. HENCE, THE VALUE OF Z_L FOR MAX. POWER DELIVERED TO Z_{IN} IS: $Z_L = -\text{Im}[Z_{IN}]$

$$\therefore Z_L = j25$$


$$V_{IN}(\lambda/4) = \frac{10\angle 0^\circ (25-j25)}{j25 + (25-j25)} = 10 - j10 = 14.14\angle -45^\circ$$

$$I_{IN}(\lambda/4) = \frac{14.14\angle -45^\circ}{25-j25} = 0.4$$

$$P_{IN} = \frac{1}{2} \text{Re}[14.14\angle -45^\circ (0.4)] = 2 \text{ W}$$

$$P_L = P_{IN} = 2 \text{ W}$$

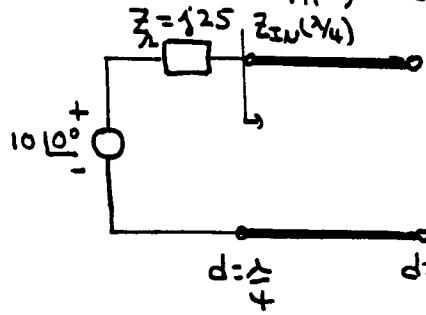(b) To find E_{TH} , we find the open circuit voltage at $d=0$:



$$Z_o = 1, V(d) = 2 \text{ A} \cos \beta d$$

$$I(d) = j \frac{2}{Z_o} A \sin \beta d \quad (1)$$

$$Z_{IN}(\frac{\lambda}{4}) = 0 \text{ (A short circuit)}$$

$$\therefore I(\frac{\lambda}{4}) = \frac{10\angle 10^\circ}{j25+0} = -j0.4 \quad (2)$$

From (1) and (2): $-j0.4 = j \frac{2}{50} \sin \frac{\pi}{2} \Rightarrow A = -10$


Hence: $V(d) = 2(-10) \cos \beta d = -20 \cos \beta d$

$$E_{TH} = V(0) = -20$$

To find Z_{TH} we set $E_i = 0$, then:

$$Z_{TH} = \frac{Z_o^2}{Z_L} = \frac{50^2}{j25} = -j100$$

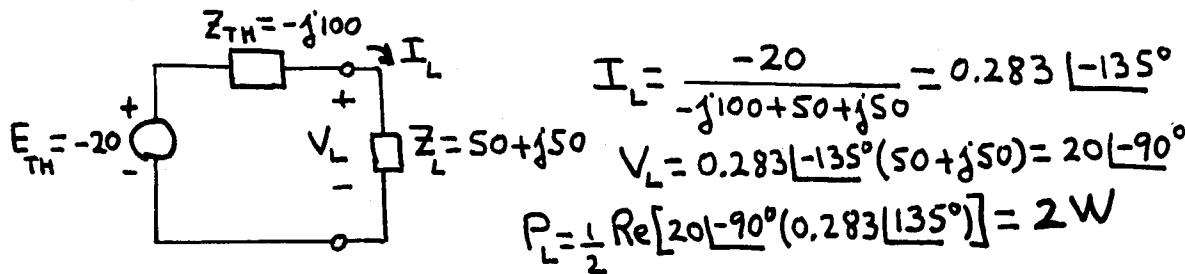The Thevenin's equivalent circuit at $d=0$ is:



$$1.15) V_2(0) = \frac{V_2(0)}{\sqrt{Z_o}} = a_2(0) + b_2(0) = 0 + 3.54 \angle 45^\circ$$

$$\therefore V_2(0) = \sqrt{50} (3.54 \angle 45^\circ) = 25.03 \angle 45^\circ$$

$$I_2(0) = \sqrt{Z_o} I_2(0) = a_2(0) - b_2(0) = 0 - 3.54 \angle 45^\circ$$

$$\therefore I_2(0) = \frac{-3.54 \angle 45^\circ}{\sqrt{50}} = 0.501 \angle -135^\circ$$

$$P_2(0) = \frac{1}{2} |I_2(0)|^2 50 = \frac{1}{2} (0.501)^2 50 = 6.27 \text{ W}$$

$$P_2(0) = \frac{1}{2} \frac{|V_2(0)|^2}{50} = \frac{1}{2} \frac{(25.03)^2}{50} = 6.27 \text{ W}$$

$$\text{Also: } P_2(0) = \frac{1}{2} |a_2(0)|^2 - \frac{1}{2} |b_2(0)|^2 = \frac{1}{2} (3.54)^2 = 6.27 \text{ W}$$

$$1.16) (a) \left| Z_{IN}(0) = Z_{IN}(d) \right| = 50 \frac{(150 + j150) + j50 \tan 45^\circ}{50 + j(150 + j150) \tan 45^\circ} = 23 - j65 \Omega$$

$d = \frac{\lambda}{8}$

$$(b) a_1(0) = \frac{1}{2\sqrt{Z_0}} [V_i(0) + Z_0 I_1(0)] , V_i(0) = E_i - Z_0 I_1(0)$$

$$\therefore a_1(0) = \frac{E_i}{2\sqrt{Z_0}} = \frac{10}{2\sqrt{50}} = 0.707$$

$$a_1\left(\frac{\lambda}{8}\right) = a_1(0) e^{j\pi/4} = 0.707 \angle -45^\circ$$

$$b_1(0) = \frac{1}{2\sqrt{50}} [V_i(0) - 50 I_1(0)] = \frac{1}{2\sqrt{50}} [10 - 50 I_1(0) - 50 I_1(0)] \quad (1)$$

$$I_1(0) = \frac{10 \angle 0^\circ}{50 + 23 - j65} = 0.102 \angle 41.68^\circ \quad (2)$$

$$(2) INTO (1): b_1(0) = \frac{1}{2\sqrt{50}} [10 - 2(50)(0.102 \angle 41.68^\circ)] = 0.508 \angle -70.65^\circ$$

$$b_1\left(\frac{\lambda}{8}\right) = b_1(0) e^{j\pi/4} = 0.508 \angle -25.65^\circ$$

SINCE $Z_2 = Z_0$, THE OUTPUT IS MATCHED. HENCE, $a_2(0) = 0$

$$(c) V_i(0) = I_1(0) Z_{IN}(0) = 0.102 \angle 41.68^\circ (23 - j65) = 7.05 \angle -28.8^\circ$$

$$\text{OR } V_i(0) = \sqrt{Z_0} [a_1(0) + b_1(0)] = \sqrt{50} [0.707 + 0.508 \angle -70.65^\circ] = 7.05 \angle -28.8^\circ$$

$$V_i\left(\frac{\lambda}{8}\right) = \sqrt{Z_0} [a_1\left(\frac{\lambda}{8}\right) + b_1\left(\frac{\lambda}{8}\right)] = \sqrt{50} [0.707 \angle -45^\circ + 0.508 \angle -25.65^\circ] = 8.47 \angle -36.92^\circ$$

$$I_1\left(\frac{\lambda}{8}\right) = \frac{8.47 \angle -36.92^\circ}{150 + j150} = 0.04 \angle -81.92^\circ$$

$$(d), (e) P_i(0) = \frac{1}{2} \operatorname{Re}[V_i(0) I_1^*(0)] = 0.12 W , P_i\left(\frac{\lambda}{8}\right) = \frac{1}{2} \operatorname{Re}[V_i\left(\frac{\lambda}{8}\right) I_1^*\left(\frac{\lambda}{8}\right)] = 0.12 W$$

$$\text{Also: } P_i(0) = P_i\left(\frac{\lambda}{8}\right) = \frac{1}{2} |a_1(0)|^2 - \frac{1}{2} |b_1(0)|^2 = \frac{1}{2} |a_1\left(\frac{\lambda}{8}\right)|^2 - \frac{1}{2} |b_1\left(\frac{\lambda}{8}\right)|^2 = \frac{1}{2} (0.707)^2 - \frac{1}{2} (0.508)^2 = 0.12 W$$

$$(f) S_{11}\left(\frac{\lambda}{8}\right) = \frac{Z_{T1} - Z_0}{Z_{T1} + Z_0} = \frac{150 + j150 - 50}{150 + j150 + 50} = 0.721 \angle 19.44^\circ$$

$$S_{11}(0) = S_{11}\left(\frac{\lambda}{8}\right) e^{-j2(\pi/4)} = 0.721 \angle 19.44^\circ (-90^\circ) = 0.721 \angle -70.56^\circ$$

$$(g) (\text{VSWR})_{in} = \frac{1 + |S_{11}|}{1 - |S_{11}|} = 6.17 , (\text{VSWR})_{out} = 1$$

$$(h) \lambda = \frac{3 \cdot 10^8}{10^9} = 0.3 \text{ m (or 30 cm)} . \lambda = \frac{\lambda}{8} = \frac{30}{8} = 3.75 \text{ cm}$$

$$(i) b_2\left(\frac{\lambda}{8}\right) = S_{21} a_1\left(\frac{\lambda}{8}\right) + S_{22} a_2\left(\frac{\lambda}{8}\right) = 3 \angle 60^\circ (0.707 \angle -45^\circ) = 2.12 \angle 15^\circ$$

$$P_2(0) = \frac{1}{2} |b_2(0)|^2 = \frac{1}{2} |b_2\left(\frac{\lambda}{8}\right)|^2 = \frac{1}{2} (2.12)^2 = 2.25 W$$

$$1.17) (a) \left| Z_{IN}(0) = Z_{IN}(\frac{d}{4}) \right| = 75 \frac{(150 + j150) + j75 \tan 45^\circ}{75 + j(150 + j150) \tan 45^\circ} = 60 - j105 \Omega$$

(b) THE VSWR IN THE $\lambda_2 = \frac{\lambda}{4}$ LINE IS UNITY, SINCE THE LINE IS MATCHED.

$$\text{IN THE } \lambda_1 = \frac{\lambda}{8} \text{ LINE : } \Gamma_0 = \frac{(150 + j150) - 75}{(150 + j150) + 75} = 0.62 \angle 29.7^\circ$$

$$\therefore \text{VSWR} = \frac{1 + 0.62}{1 - 0.62} = 4.26$$

$$(c) V_1(0) = \frac{10 \angle 0^\circ Z_{IN}(0)}{Z_{IN}(0) + Z_1} = \frac{10(60 - j105)}{60 - j105 + 100} = 6.32 \angle -26.98^\circ$$

$$I_1(0) = \frac{V_1(0)}{Z_{IN}(0)} = \frac{6.32 \angle -26.98^\circ}{60 - j105} = 0.0523 \angle 33.27^\circ$$

$$a_1(0) = \frac{1}{2\sqrt{75}} [V_1(0) + 75 I_1(0)] = 0.516 \angle -4.6^\circ$$

$$b_1(0) = \frac{1}{2\sqrt{75}} [V_1(0) - 75 I_1(0)] = 0.32 \angle -64.88^\circ$$

$$a_1(\frac{\lambda}{8}) = a_1(0) e^{-j\pi/4} = 0.516 \angle -49.6^\circ$$

$$b_1(\frac{\lambda}{8}) = b_1(0) e^{j\pi/4} = 0.32 \angle -19.8^\circ$$

$$a_2(0) = 0$$

$$(d) P_1(0) = \frac{1}{2} |a_1(0)|^2 - \frac{1}{2} |b_1(0)|^2 = \frac{1}{2} (0.516)^2 - \frac{1}{2} (0.32)^2 = 0.082 \text{ W}$$

$$P_1(\frac{\lambda}{8}) = \frac{1}{2} |a_1(\frac{\lambda}{8})|^2 - \frac{1}{2} |b_1(\frac{\lambda}{8})|^2 = \frac{1}{2} (0.516)^2 - \frac{1}{2} (0.32)^2 = 0.082 \text{ W}$$

$$(e) P_{AVS} = \frac{|E_1|^2}{8 \operatorname{Re}[Z]} = \frac{(10)^2}{8 (100)} = 0.125 \text{ W}$$

$$\frac{1}{2} |a_1(0)|^2 = 0.133 \text{ W}$$

SINCE $Z_1 \neq Z_0$, IT FOLLOWS THAT $P_{AVS} \neq \frac{1}{2} |a_1(0)|^2$

$$1.18) (a) V = \frac{5 \angle 30^\circ (100)}{100 + (50 + j50)} = 3.162 \angle 11.565^\circ$$

$$I = \frac{V}{Z_L} = \frac{3.162 \angle 11.565^\circ}{100} = 0.0316 \angle 11.565^\circ$$

$$a_1 = \frac{1}{2\sqrt{R_L}} (V + Z_L I) = \frac{1}{2\sqrt{50}} (3.162 \angle 11.565^\circ + (50 + j50)(0.0316 \angle 11.565^\circ)) \\ = 0.355 \angle 30.14^\circ$$

$$b_p = \frac{1}{2R_n} (V - Z_n^* I) = \frac{1}{2\sqrt{50}} (3.162 \angle 11.565^\circ - (50-j50)(0.0316 \angle 11.565^\circ)) \\ = 0.158 \angle 56.53^\circ$$

$$V_p^+ = \frac{E_n Z_n^*}{2 R_n} = \frac{5 \angle 30^\circ (50-j50)}{2(50)} = 3.536 \angle -15^\circ$$

$$V_p^- = V - V_p^+ = 3.162 \angle 11.565^\circ - 3.536 \angle -15^\circ = 1.581 \angle 101.59^\circ$$

$$I_p^+ = \frac{E_n}{2 R_n} = \frac{5 \angle 30^\circ}{2(50)} = 0.05 \angle 30^\circ$$

$$I_p^- = I_p^+ - I = 0.05 \angle 30^\circ - 0.0316 \angle 11.565^\circ = 0.022 \angle 56.52^\circ$$

(b) $V_p^+ = \frac{Z_n^*}{\sqrt{R_n}} a_p = \frac{(50-j50)}{\sqrt{50}} 0.355 \angle 30.14^\circ = 3.54 \angle -15^\circ$

(c) $V_p^- = \frac{Z_n}{\sqrt{R_n}} b_p = \frac{(50+j50)}{\sqrt{50}} 0.158 \angle 56.53^\circ = 1.58 \angle 101.5^\circ$

$$V = V_p^+ + V_p^- = 3.16 \angle 11.56^\circ$$

$$I_p^+ = \frac{a_p}{\sqrt{R_n}} = \frac{0.355 \angle 30.14^\circ}{\sqrt{50}} = 0.05 \angle 30.14^\circ$$

$$I_p^- = \frac{b_p}{\sqrt{R_n}} = \frac{0.158 \angle 56.53^\circ}{\sqrt{50}} = 0.022 \angle 56.53^\circ$$

$$I = I_p^+ - I_p^- = 0.0316 \angle 11.56^\circ$$

1.19) IN EXAMPLE 1.71: $V = 5.59 \angle -26.57^\circ$, $a_p = 0.5$, $b_p = 0$

(a) $V_p^+ = \frac{E_n Z_n^*}{2 R_n} = \frac{10(100-j50)}{2(100)} = 5.59 \angle -26.57^\circ$

$$V_p^- = V - V_p^+ = 5.59 \angle -26.57^\circ - 5.59 \angle -26.57^\circ = 0$$

(b) $a_p = \frac{\sqrt{R_n}}{Z_n^*} V_p^+ = \frac{\sqrt{100}}{100-j50} (5.59 \angle -26.57^\circ) = 0.5$

$$b_p = \frac{\sqrt{R_n}}{Z_n} V_p^- = 0$$

1.20) IN EXAMPLE 1.7.2: $V = 10$, $a_p = 1.5$, $b_p = -0.5$


$$(a) V_p^+ = \frac{E_n Z_n^*}{2R_n} = \frac{30(100)}{2(100)} = 15$$

$$V_p^- = V - V_p^+ = 10 - 15 = -5$$

$$(b) a_p = \frac{\sqrt{R_n}}{Z_n^*} V_p^+ = \frac{\sqrt{100}}{100} (15) = 1.5$$

$$b_p = \frac{\sqrt{R_n}}{Z_n} V_p^- = \frac{\sqrt{100}}{100} (-5) = -0.5$$

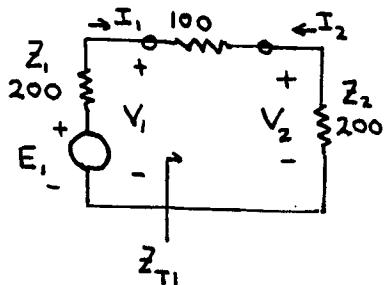1.21) WITH $E_2 = 0$: $Z_{T1} = 100 + 200 = 300$



$$S_{p11} = \frac{Z_{T1} - Z_1^*}{Z_{T1} + Z_1} = \frac{300 - 200}{300 + 200} = 0.2$$

$$V_1 = \frac{E_1}{300+200} = \frac{3}{5} E_1, \quad I_1 = \frac{E_1}{500}$$

$$V_2 = \frac{E_1}{200+300} = \frac{2}{5} E_1, \quad I_2 = -\frac{E_1}{500}$$

$$a_{p1} = \frac{1}{2\sqrt{200}} (V_1 + Z_1 I_1) = \frac{1}{2\sqrt{200}} \left(\frac{3}{5} E_1 + 200 \frac{E_1}{500} \right) = \frac{E_1}{2\sqrt{200}}, \quad a_{p2} = 0$$

$$b_{p2} = \frac{1}{2\sqrt{200}} (V_2 - Z_2^* I_2) = \frac{1}{2\sqrt{200}} \left(\frac{2}{5} E_1 + 200 \frac{E_1}{500} \right) = \frac{2E_1}{5\sqrt{200}}$$

$$S_{p21} = \frac{b_{p2}}{a_{p1}} \Big|_{a_{p2}=0} = \frac{2E_1}{5\sqrt{200}} \frac{2\sqrt{200}}{E_1} = \frac{4}{5}$$

FROM SYMMETRY: $S_{p22} = S_{p11}$ AND $S_{p12} = S_{p21}$

THE MAGNITUDE OF S_{p21} CAN ALSO BE CALCULATED AS FOLLOWS:


$$|S_{p21}|^2 = \frac{P_L}{P_{AVS}}, \quad P_L = \frac{1}{2} \frac{|E_1(\frac{2}{5})|^2}{200}, \quad P_{AVS} = \frac{|E_1|^2}{8(200)}$$

$$\therefore |S_{p21}|^2 = \frac{16}{25} \quad \text{OR} \quad |S_{p21}| = \frac{4}{5}$$

SINCE IN THIS EXAMPLE S_{p21} IS REAL, THEN $S_{p21} = \frac{4}{5}$.

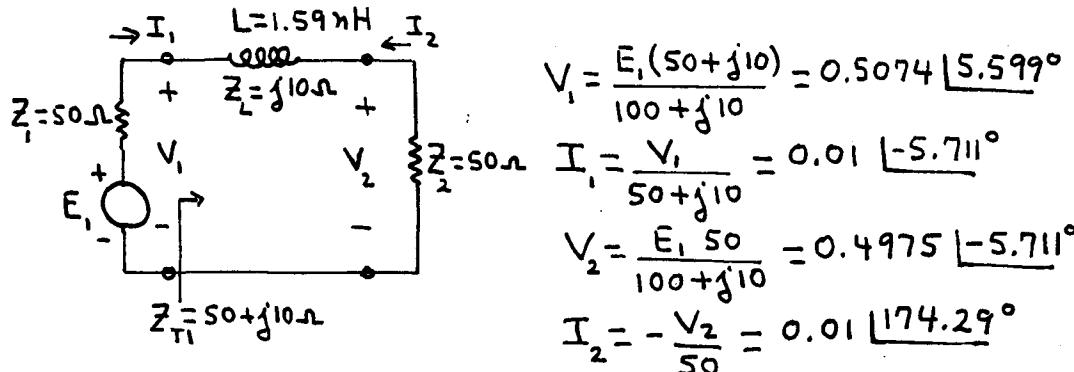1.22) (a) $f = 1 \text{ GHz}$

EVALUATION OF S_{p11} AND S_{p21} (LET $E_1 = 110^\circ$)



$$a_{p1} = \frac{1}{2\sqrt{R_1}} (V_1 + Z_1 I_1) = \frac{1}{2\sqrt{50}} (0.5074 [5.599^\circ] + 50(0.01 [-5.711^\circ])) = 0.0709 [-0.0143^\circ]$$

$$b_{p1} = \frac{1}{2\sqrt{R_1}} (V_1 - Z_1^* I_1) = \frac{1}{2\sqrt{50}} (0.5074 [5.599^\circ] - 50(0.01 [-5.711^\circ])) = 0.007 [85.70^\circ]$$

$$a_{p2} = \frac{1}{2\sqrt{R_2}} (V_2 + Z_2 I_2) = 0$$

$$b_{p2} = \frac{1}{2\sqrt{R_2}} (V_2 - Z_2^* I_2) = \frac{1}{2\sqrt{50}} (0.4975 [-5.711^\circ] - 50(0.01 [174.29^\circ])) = 0.0705 [-5.711^\circ]$$

$$S_{p11} = \left. \frac{b_{p1}}{a_{p1}} \right|_{a_{p2}=0} = \frac{0.007 [85.7^\circ]}{0.0709 [-0.0143^\circ]} = 0.099 [85.7^\circ]$$

S_{p11} CAN ALSO BE CALCULATED USING:

$$S_{p11} = \frac{Z_{T1} - Z_1^*}{Z_{T1} + Z_1} = \frac{50 + j10 - 50}{50 + j10 + 50} = 0.099 [84.3^\circ]$$

$$S_{p21} = \left. \frac{b_{p2}}{a_{p1}} \right|_{a_{p2}=0} = \frac{0.0705 [-5.711^\circ]}{0.0709 [-0.0143^\circ]} = 0.994 [-5.7^\circ]$$

(b) WITH $Z_o = 50 \Omega$, IT FOLLOWS FROM (1.6.24) AND (1.6.25) THAT

$$S_{11} = S_{22} = \frac{Z_L}{Z_L + 2Z_o} = \frac{j10}{j10 + 100} = 0.099 [84.3^\circ]$$

$$S_{21} = S_{12} = \frac{2Z_o}{Z_L + 2Z_o} = \frac{100}{j10 + 100} = 0.995 [-5.7^\circ]$$

AS EXPECTED, FOR $Z_1 = Z_2 = Z_o = 50 \Omega$ THE S_p PARAMETERS ARE IDENTICAL TO THE S PARAMETERS.

$$1.23) \text{ At } P: I_1^+ = I_1^- + I_2^- + I_3^-$$

$$\text{AND } b_1 = S_{11}a_1 \Rightarrow \sqrt{Z_0} I_1^- = S_{11}\sqrt{Z_0} I_1^+ \text{ OR } I_1^- = S_{11}I_1^+$$

$$b_2 = S_{21}a_1 \Rightarrow \sqrt{Z_0} I_2^- = S_{21}\sqrt{Z_0} I_1^+ \text{ OR } I_2^- = S_{21}I_1^+$$

$$b_3 = S_{31}a_1 \Rightarrow \sqrt{Z_0} I_3^- = S_{31}\sqrt{Z_0} I_1^+ \text{ OR } I_3^- = S_{31}I_1^+$$

$$\therefore I_1^+ = S_{11}I_1^+ + S_{21}I_1^+ + S_{31}I_1^+$$

$$S_{11} + S_{21} + S_{31} = 1$$

SIMILARLY, WITH E_2 APPLIED TO PORT 2 WITH THE OTHER PORTS MATCHED GIVES

$$S_{12} + S_{22} + S_{32} = 0$$

WITH E_3 APPLIED TO PORT 3, WITH THE OTHER PORTS MATCHED GIVES

$$S_{13} + S_{23} + S_{33} = 0$$

WITH ALL THE SOURCES EQUAL TO E_0 , AS SHOWN IN FIG. 1.22b, THE CURRENTS I_1 , I_2 , AND I_3 ARE EQUAL TO ZERO. HENCE,

$$I_1^+ = I_1^-, I_2^+ = I_2^-, I_3^+ = I_3^-, \text{ AND } I_1^+ = I_2^+ = I_3^+$$

$$\text{FROM } b_1 = S_{11}a_1 + S_{12}a_2 + S_{13}a_3$$

$$\text{OR } I_1^- = S_{11}I_1^+ + S_{12}I_2^+ + S_{13}I_3^+ \Rightarrow S_{11} + S_{12} + S_{13} = 1$$

SIMILARLY:

$$I_2^- = S_{21}I_1^+ + S_{22}I_2^+ + S_{23}I_3^+ \Rightarrow S_{21} + S_{22} + S_{23} = 1$$

$$I_3^- = S_{31}I_1^+ + S_{32}I_2^+ + S_{33}I_3^+ \Rightarrow S_{31} + S_{32} + S_{33} = 1$$

$$1.24) \quad (a) \quad v_1 = j_{11}i_1 + j_{12}i_2 \quad (1) \quad i_1 = y_{11}v_1 + y_{12}v_2 \quad (3)$$

$$v_2 = j_{21}i_1 + j_{22}i_2 \quad (2) \quad i_2 = y_{21}v_1 + y_{22}v_2 \quad (4)$$

$$\text{FROM (2): } i_2 = \frac{v_2}{j_{22}} - \frac{j_{21}}{j_{22}} i_1 \quad (5)$$

$$(5) \text{ INTO (1): } i_1 = \frac{j_{22}}{|j|} v_1 - \frac{j_{12}}{|j|} v_2 \quad (6), |j| = j_{11}j_{22} - j_{12}j_{21}$$

$$\text{COMPARING (6) WITH (3) GIVES: } y_{11} = \frac{j_{22}}{|j|} \text{ AND } y_{12} = -\frac{j_{12}}{|j|}$$

$$(6) \text{ INTO } (2): V_2 = j_{21} \left(\frac{j_{22}}{|j|} V_1 - \frac{j_{12}}{|j|} V_2 \right) + j_{22} i_2$$

OR $i_2 = -\frac{j_{21}}{|j|} V_1 + \frac{j_{11}}{|j|} V_2 \quad (7)$

COMPARING (7) WITH (4) GIVES: $j_{21} = -\frac{j_{21}}{|j|}$ AND $j_{22} = \frac{j_{11}}{|j|}$.

THE DERIVATION BETWEEN γ AND j PARAMETERS IS SIMILAR.

$$(b) \quad V_1 = A V_2 - B i_2 \quad (8)$$

$$i_1 = C V_2 - D i_2 \quad (9)$$

FROM (9): $V_2 = \frac{1}{C} i_1 + \frac{D}{C} i_2 \quad (10)$

$$(10) \text{ INTO } (8): V_1 = \frac{A}{C} i_1 + \frac{AD-BC}{C} i_2 \quad (11)$$

COMPARING (11) WITH (1) GIVES: $j_{11} = \frac{A}{C}$ AND $j_{12} = \frac{AD-BC}{C}$

$$(11) \text{ INTO } (8): \frac{A}{C} i_1 + \frac{AD-BC}{C} i_2 = A V_2 - B i_2$$

OR $V_2 = \frac{1}{C} i_1 + \frac{D}{C} i_2 \quad (12)$

COMPARING (12) WITH (2) GIVES: $j_{21} = \frac{1}{C}$ AND $j_{22} = \frac{D}{C}$

THE DERIVATION BETWEEN j AND ABCD IS SIMILAR.

1.25)(a) FOR REAL $[Z_o]$ AND $[Y_o]$

$$[I] = [y][V]$$

$$[I^-] = [I^+] - [I]$$

$$[V^-][Y_o] = [V^+][Y_o] - [y](V^+ + V^-)$$

$$([Y_o] + [y])[V^-] = ([Y_o] - [y])[V^+]$$

$$\begin{aligned} [V^-] &= ([Y_o] + [y])^{-1} ([Y_o] - [y])[V^+] \\ &= [S][V^+] \end{aligned}$$

$$\therefore [S] = -([Y_o] + [y])^{-1} ([y] - [Y_o]) \quad (1)$$

$$[Y_0] - [y] = [Y_0][s] + [y][s]$$

$$[Y_0]([I] - [s]) = [y]([I] + [s])$$

$$[y] = [Y_0]([I] - [s])([I] + [s])^{-1}$$

(b) FROM (1) :

$$[s] = - \left[\begin{bmatrix} Y_0 & 0 \\ 0 & Y_0 \end{bmatrix} + \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \right]^{-1} \left[\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} - \begin{bmatrix} Y_0 & 0 \\ 0 & Y_0 \end{bmatrix} \right]$$

$$[s] = - \begin{bmatrix} y_{11} + Y_0 & y_{12} \\ y_{21} & y_{22} + Y_0 \end{bmatrix}^{-1} \begin{bmatrix} y_{11} - Y_0 & y_{12} \\ y_{21} & y_{22} - Y_0 \end{bmatrix}$$

$$\begin{bmatrix} y_{11} + Y_0 & y_{12} \\ y_{21} & y_{22} + Y_0 \end{bmatrix}^{-1} = \frac{\begin{bmatrix} y_{22} + Y_0 & -y_{12} \\ -y_{21} & y_{11} + Y_0 \end{bmatrix}}{(y_{11} + Y_0)(y_{22} + Y_0) - y_{12}y_{21}}$$

$$\therefore [s] = - \frac{\begin{bmatrix} (y_{22} + Y_0)(y_{11} - Y_0) - y_{12}y_{21} & (y_{22} + Y_0)y_{12} - y_{12}(y_{22} - Y_0) \\ -y_{21}(y_{11} - Y_0) + y_{21}(y_{11} + Y_0) & -y_{12}y_{21} + (y_{11} + Y_0)(y_{22} - Y_0) \end{bmatrix}}{(y_{11} + Y_0)(y_{22} + Y_0) - y_{12}y_{21}}$$

$$[s] = \frac{1}{\Delta_2} \begin{bmatrix} (1 - y'_{11})(1 + y'_{22}) + y'_{12}y'_{21} & -2y'_{12} \\ -2y'_{21} & (1 + y'_{11})(1 - y'_{22}) + y'_{12}y'_{21} \end{bmatrix}$$

WHERE $\Delta_2 = (1 + y'_{11})(1 + y'_{22}) - y'_{12}y'_{21}$, $y'_{11} = y_{11}Z_0$, $y'_{12} = y_{12}Z_0$,
 $y'_{21} = y_{21}Z_0$, AND $y'_{22} = y_{22}Z_0$ ($Z_0 = 1/Z_0$).

1.26) STEP 1. CONVERT THE $[s]$ PARAMETERS OF THE BJT TO $[z]$ PARAMETERS (CALLED $[z_1]$).

STEP 2. CALCULATE THE $[z]$ PARAMETERS OF THE INDUCTOR (CALLED $[z_2]$).

STEP 3. ADD THE $[z]$ PARAMETERS (T.E., $[z_3] = [z_1] + [z_2]$)

STEP 4. CONVERT $[z_3]$ TO $[s]$ PARAMETERS. THESE ARE THE $[s]$ PARAMETERS OF THE TWO-PORT NETWORK.

1.27) CONVERT THE CE S PARAMETERS TO CE Y PARAMETERS (SEE FIG.1.8.1),

THAT IS: $y_{11,e} = 0.016 + j0.034 \quad y_{12,e} = 0.00141 - j0.0272(10^{-3})$

$y_{21,e} = 0.04 - j0.036 \quad y_{22,e} = 0.00363 + j0.0079$

USE THE RELATIONS IN FIG. 1.8.1b TO CALCULATE THE CB AND CC Y PARAMETERS. THAT IS,

$$y_{11,b} = 0.061 + j0.00587 \quad y_{12,b} = -0.00503 - j0.00787$$

$$y_{21,b} = -0.0436 + j0.0281 \quad y_{22,b} = 0.00363 + j0.0079$$

AND

$$y_{11,c} = 0.016 + j0.034 \quad y_{12,c} = -0.0174 - j0.034$$

$$y_{21,c} = -0.056 + j0.002 \quad y_{22,c} = 0.061 + j0.00587$$

CONVERT FROM CB AND CC Y PARAMETERS TO CB AND CC S PARAMETERS. THAT IS,

$$[S]_{CB} = \begin{bmatrix} 0.356[-173.6^\circ] & 0.243[35.41^\circ] \\ 1.3481[-54.81^\circ] & 1.1981[-32.7^\circ] \end{bmatrix} \text{ AND } [S]_{CC} = \begin{bmatrix} 0.893[-62.03^\circ] & 0.764[29.68^\circ] \\ 1.12[-35.26^\circ] & 0.176[98.35^\circ] \end{bmatrix}$$

1.28)(a)

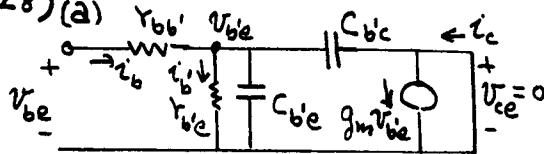


FIG. 1.11.4 WITH $V_{ce} = 0$

$$i_c = g_m V_{be} e^{(1)} \quad (1)$$

$$i_b' = i_b \frac{\frac{1}{j\omega(C_{b'e} + C_{b'c})}}{R_{b'e} + \left(\frac{1}{j\omega(C_{b'e} + C_{b'c})}\right)} \quad (2)$$

$$V_{be} = i_b' R_{b'e} \quad (3)$$

$$\text{FROM (1), (2), AND (3): } i_c = g_m R_{b'e} i_b' = \frac{g_m R_{b'e} i_b}{1 + j\omega R_{b'e} (C_{b'e} + C_{b'c})}$$

DEFINE $h_{fe}(j\omega)$ AS:

$$h_{fe}(j\omega) = \frac{i_c}{i_b} \Big|_{V_{ce}=0} = \frac{g_m R_{b'e}}{1 + j\omega R_{b'e} (C_{b'e} + C_{b'c})} = \frac{g_m R_{b'e}}{1 + j\omega / w_\beta}$$

WHERE

$$f_\beta = \frac{w_\beta}{2\pi} = \frac{1}{2\pi R_{b'e} (C_{b'e} + C_{b'c})} \approx \frac{1}{2\pi R_{b'e} C_{b'e}} \quad (\text{SINCE } C_{b'e} \gg C_{b'c})$$

f_T (THE GAIN-BANDWIDTH PRODUCT) IS THE FREQUENCY WHERE $|h_{fe}(j\omega)| = 1$, OR

$$1 = \frac{g_m R_{b'e}}{\sqrt{1 + (\omega_T/w_\beta)^2}} \approx g_m R_{b'e} \frac{w_\beta}{\omega_T} \Rightarrow f_T = g_m R_{b'e} f_\beta = \frac{g_m}{2\pi C_{b'e}}$$

(b) SIMILARLY, FOR THE FET IN FIG. 1.11.15 WE OBTAIN

$$f_T = \frac{g_m}{2\pi(C_{gd} + C_{gs})} \approx \frac{g_m}{2\pi C_{gs}} = \frac{g_m}{2\pi C_C} \quad (\text{SINCE } C_{gs} \text{ IS DENOTED BY } C_C \text{ IN FIG. 1.11.15})$$

$$2.1) (a) \text{ LET } z_1 = \frac{Z}{50} = \frac{100+j100}{50} = 2+j2$$

(z_1 IS SHOWN IN THE SMITH CHART)

$$(b) y_1 = \frac{1}{z_1} = 0.25 - j0.25$$

(y_1 IS SHOWN IN THE SMITH CHART)


(c) IN THE Z SMITH CHART THE LOCATION OF z_1 IS THE SAME AS IN (a). THE VALUE OF y_1 IS READ FROM THE GREEN CIRCLES.

$$(d) z_2 = \frac{50-j100}{50} = 1-j2$$

$$y_2 = \frac{1}{z_2} = 0.2 + j0.4$$

$$z_3 = \frac{25-j25}{50} = 0.5-j0.5$$

$$y_3 = \frac{1}{z_3} = 1+j$$

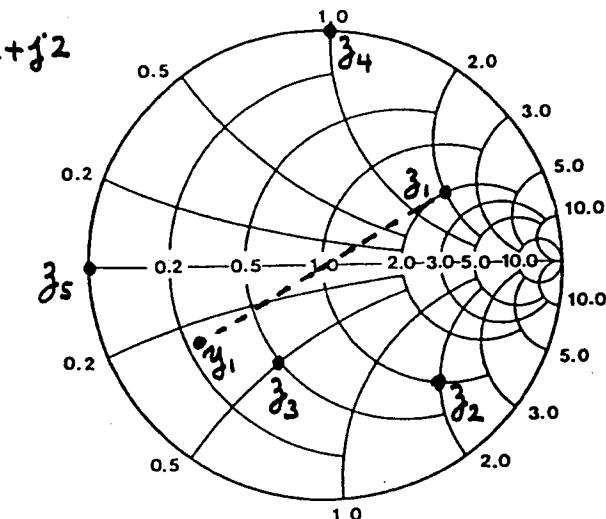

$$z_4 = \frac{j50}{50} = j1 \quad z_5 = j0$$

$$y_4 = \frac{1}{z_4} = -j1 \quad y_5 = \infty$$

(z_2, z_3, z_4 , AND z_5 ARE SHOWN IN THE SMITH CHART)

$$2.2) (a) z = -r + jx, \Gamma = \frac{z-1}{z+1} = \frac{-(r+1) + jx}{(1-r) + jx} \quad (1)$$

$$|\Gamma| = \sqrt{\frac{(r+1)^2 + x^2}{(1-r)^2 + x^2}} = \sqrt{\frac{r^2 + 2r + 1 + x^2}{r^2 - 2r + 1 + x^2}} \quad (2)$$

IN (1) THE NUMERATOR IS GREATER THAN THE DENOMINATOR, SINCE $2r > -2r$. HENCE, $|\Gamma| > 1$

$$(b) \text{ FROM (1): } \frac{1}{\Gamma^*} = \frac{(1-r) - jx}{-(r+1) - jx} = \frac{(r-1) + jx}{(r+1) + jx} \quad (3)$$

EQ. (3) IS IDENTICAL TO THE TRANSFORMATION IN (2.2.2) WHERE $z = r + jx$ WITH $r \geq 0$. HENCE, NEGATIVE RESISTANCES CAN BE HANDLED IN THE SMITH CHART BY PLOTTING $\frac{1}{\Gamma^*}$ AND INTERPRETING THE RESISTANCE CIRCLES AS BEING NEGATIVE, AND THE REACTANCE CIRCLES AS MARKED.

$$(c) \quad Z_1 = \frac{Z_1}{50} = \frac{-20+j16}{50} = -0.4+j0.32$$

FROM THE SMITH CHART WE READ:

$$\frac{1}{r^*} = 0.47 \angle 139^\circ$$


$$\text{HENCE } \Gamma = 2.1 \angle 139^\circ$$

FOR:

$$Z_2 = \frac{-200+j25}{50} = -4+j0.5$$

$$\frac{1}{r^*} = 0.61 \angle 3.75^\circ$$
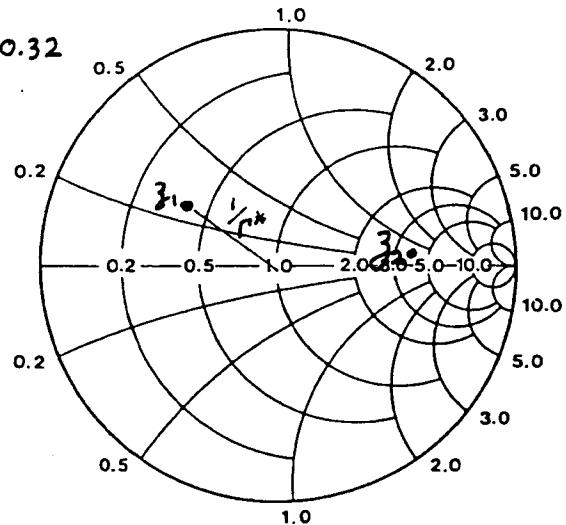
$$\text{HENCE } \Gamma = 1.6 \angle 3.75^\circ$$



(d) SEE THE COMPRESSED SMITH


CHART. FOR $Z_1 = -0.4 + j0.32$

WE READ: $|\Gamma| = 2.1$, $\angle \Gamma = 139^\circ$.

HENCE $\Gamma = 2.1 \angle 139^\circ$.

SIMILARLY, FOR Z_2 WE
OBTAIN $\Gamma = 1.6 \angle 3.75^\circ$

(e) $|\Gamma| \approx 3.2$

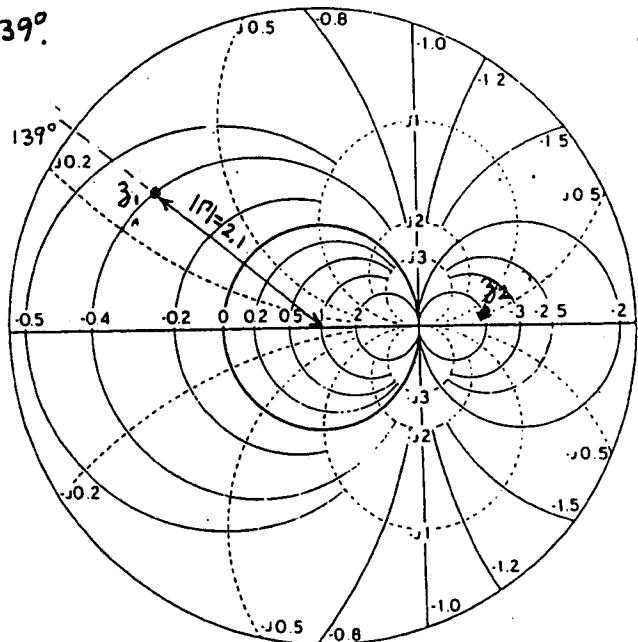

$$2.3) \quad Z(d) = Z_0 \frac{Z_L + j Z_0 \tan \beta d}{Z_0 + j Z_L \tan \beta d}$$

$$Z\left(d + \frac{n\lambda}{2}\right) = Z_0 \frac{Z_L + j Z_0 \tan(\beta d + \frac{n\beta\lambda}{2})}{Z_0 + j Z_L \tan(\beta d + \frac{n\beta\lambda}{2})} ; \quad n\beta\frac{\lambda}{2} = \frac{n_2\pi}{2} = n\pi$$

$$\tan(\beta d + n\pi) = \tan \beta d$$

HENCE,

$$Z\left(d + \frac{n\lambda}{2}\right) = Z(d)$$

2.4) From (2.2.6) AND (2.2.7): Let $\Gamma_0 = |\Gamma_0| e^{j\phi_L}$, THEN

$$\Gamma = \Gamma_0 e^{-j^2 \beta d} = |\Gamma_0| e^{j(\phi_L - 2\beta d)} = |\Gamma| e^{j\phi}; |\Gamma| = |\Gamma_0|$$

$$\phi = \phi_L - 2\beta d$$

$$Z(d) = Z_0 \left[\frac{1 + |\Gamma| e^{j\phi}}{1 - |\Gamma| e^{j\phi}} \right]$$

$$= Z_0 \left[\frac{1 + |\Gamma| \cos \phi + j|\Gamma| \sin \phi}{1 - |\Gamma| \cos \phi - j|\Gamma| \sin \phi} \right] \quad (1)$$

OR

$$Z(d) = Z_0 \left[\frac{1 - |\Gamma|^2 + j2|\Gamma| \sin \phi}{1 - 2|\Gamma| \cos \phi + |\Gamma|^2} \right] = R(d) + jX(d)$$


Hence: $R(d) = Z_0 \frac{1 - |\Gamma|^2}{1 - 2|\Gamma| \cos \phi + |\Gamma|^2}, X(d) = Z_0 \frac{2|\Gamma| \sin \phi}{1 - 2|\Gamma| \cos \phi + |\Gamma|^2}$

ALSO, FROM (1)

$$|Z(d)| = Z_0 \left[\frac{(1 + |\Gamma| \cos \phi)^2 + (|\Gamma| \sin \phi)^2}{(1 - |\Gamma| \cos \phi)^2 + (|\Gamma| \sin \phi)^2} \right]^{1/2} = Z_0 \left[\frac{1 + 2|\Gamma| \cos \phi + |\Gamma|^2}{1 - 2|\Gamma| \cos \phi + |\Gamma|^2} \right]^{1/2}$$

$$\theta_d = \tan^{-1} \frac{X(d)}{R(d)} = \tan^{-1} \left[\frac{2|\Gamma| \sin \phi}{1 - |\Gamma|^2} \right]$$

2.5)

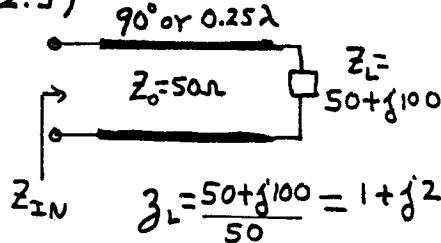

LOCATE Z_L IN THE SMITH CHART.


AT Z_L READ 0.187λ . DRAW A CONSTANT $|\Gamma|$ CIRCLE. Z_{IN} IS AT 0.25λ FROM Z_L (OR $0.187\lambda + 0.25\lambda = 0.437\lambda$).

HENCE: $Z_{IN} = 0.21 - j0.41$

$$Z_{IN} = 50 Z_{IN} = 10.5 - j20.5 \Omega$$

$$\Gamma_0 = 0.707 \angle 45^\circ$$
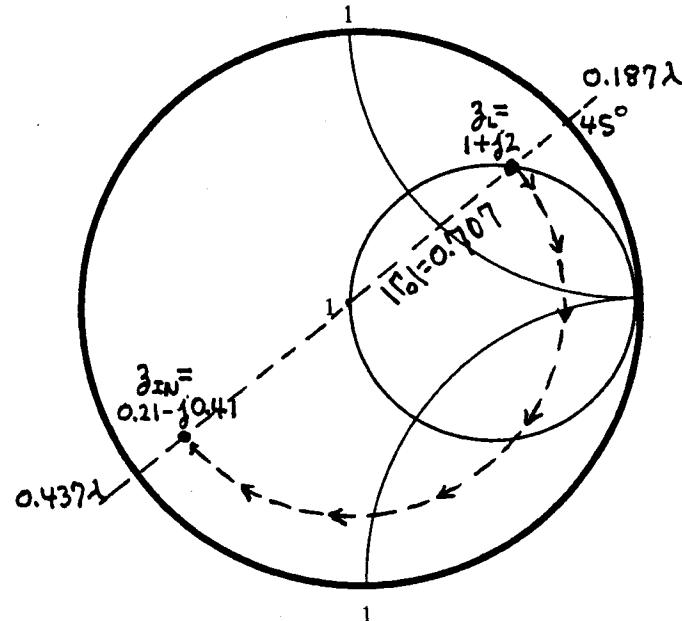
$$VSWR = \frac{1 + 0.707}{1 - 0.707} = 5.83$$



$$2.6) (a) |V(d)|_{\max} = |A_1| (1 + |\Gamma_0|) \text{ AND } |I(d)|_{\min} = \frac{|A_1|}{Z_0} (1 - |\Gamma_0|)$$

$$\text{HENCE: } R(d)_{\max} = \frac{|V(d)|_{\max}}{|I(d)|_{\min}} = Z_0 \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|}$$

$$r(d)_{\max} = \frac{R(d)_{\max}}{Z_0} = \frac{1 + |\Gamma_0|}{1 - |\Gamma_0|} = \text{VSWR}$$

$$(b) |V(d)|_{\min} = |A_1| (1 - |\Gamma_0|) \text{ AND } |I(d)|_{\max} = \frac{|A_1|}{Z_0} (1 + |\Gamma_0|)$$

$$\text{HENCE: } R(d)_{\min} = \frac{|V(d)|_{\min}}{|I(d)|_{\max}} = Z_0 \frac{1 - |\Gamma_0|}{1 + |\Gamma_0|}$$



$$r(d)_{\min} = \frac{R(d)_{\min}}{Z_0} = \frac{1 - |\Gamma_0|}{1 + |\Gamma_0|} = \frac{1}{\text{VSWR}}$$

$$2.7) (a) Z_{IN} = -j \frac{25}{50} = -j 0.5$$


FROM THE Z SMITH CHART: $\lambda = 0.426\lambda$

$$(b) Y_{IN} = j 2$$

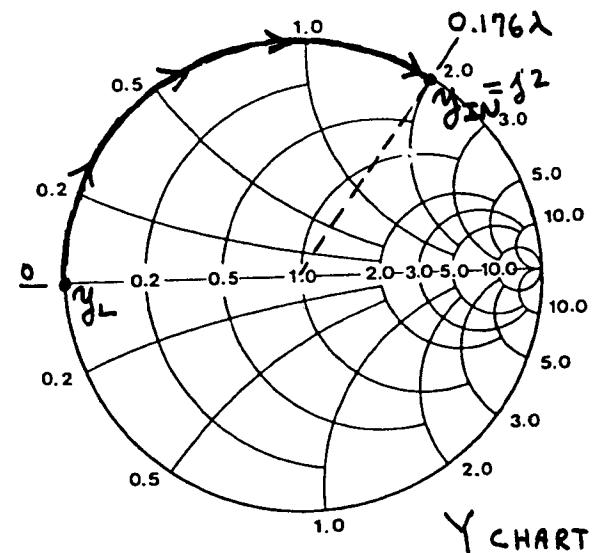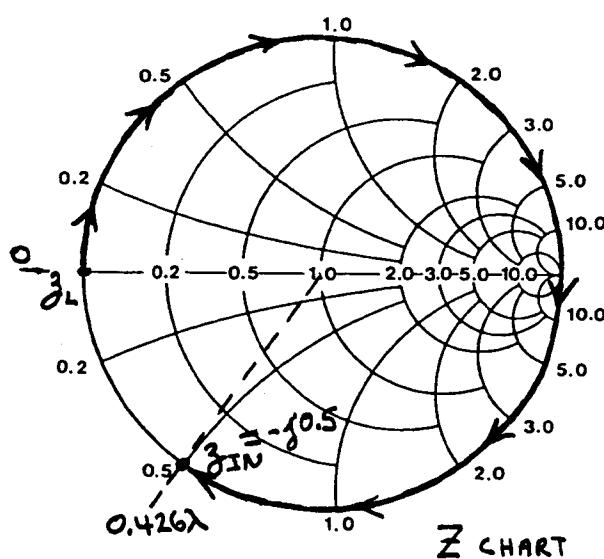FROM THE Y SMITH CHART: $\lambda = 0.176\lambda$



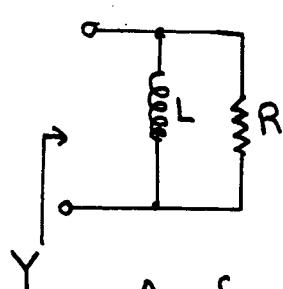2.8) THE FREQUENCY RESPONSE FOLLOWS A CONSTANT CONDUCTANCE CIRCLE WITH $g=1$. THE EQUIVALENT CIRCUIT IS (SEE FIG. 2.3.2b)



$$Y = \frac{1}{R} - j \frac{1}{\omega L}$$

$$y = \frac{Y}{Y_0} = Y Z_0 = \frac{Z_0}{R} - j \frac{Z_0}{\omega L}$$

$$g = 1 = \frac{Z_0}{R} \Rightarrow R = 50 \Omega$$

$$\text{AT } f_b = 1 \text{ GHz: } -j \frac{50}{\omega_b L} = -j 0.5, L = \frac{50}{0.5(2\pi \cdot 10^9)} = 15.9 \text{ nH}$$

$$\text{OBSERVE THAT AT } f_a = 500 \text{ MHz: } y = -j \frac{Z_0}{\omega_a L} = \frac{-j 50}{2\pi \cdot 500 \cdot 10^6 \cdot 15.9 \cdot 10^{-9}} = j 1$$

2.9) (a) $Y = 0.4, R = 50 \Omega \Rightarrow 50(0.4) = 20 \Omega$


AT f_a , THE REACTANCE IS $-j 0.6$; AND AT f_b IS $-j 0.32$.

$$Z = 20 - j \frac{1}{\omega_a C} \quad \therefore \frac{1}{\omega_a C} = 0.6(50) = 30 \quad (C = 50 \text{ pF})$$

$$\text{OR } f_a = \frac{1}{2\pi(30)50 \cdot 10^{-12}} = 106.1 \text{ MHz}$$

$$\text{AND } \frac{1}{\omega_b C} = 0.32(50) = 16 \Rightarrow f_b = \frac{1}{2\pi(16)50 \cdot 10^{-12}} = 198.9 \text{ MHz}$$

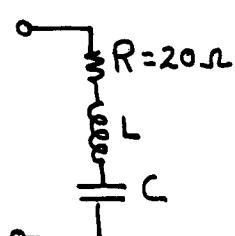(b) THE EQUIVALENT CIRCUIT IS A SERIES R, L, C CIRCUIT.



$$\text{AT } f_a = 500 \text{ MHz, } Z = 20 + j 10 \quad \therefore 20 + j 10 = R + j(\omega_a L - \frac{1}{\omega_a C}) \quad (1)$$

$$\text{AT } f_b = 1 \text{ GHz, } Z = 20 + j 30$$

$$\therefore 20 + j 30 = R + j(\omega_b L - \frac{1}{\omega_b C}) \quad (2)$$


FROM (1) AND (2) IT FOLLOWS THAT $R = 20 \Omega$ AND

$$10 = 2\pi(f_a L - \frac{1}{f_a C}) \text{ AND } 30 = 2\pi(f_b L - \frac{1}{f_b C})$$

THE SIMULTANEOUS SOLUTION OF THESE EQUATIONS IS:

$$L = 5.31 \text{ nH}$$

$$C = 47.64 \text{ pF}$$


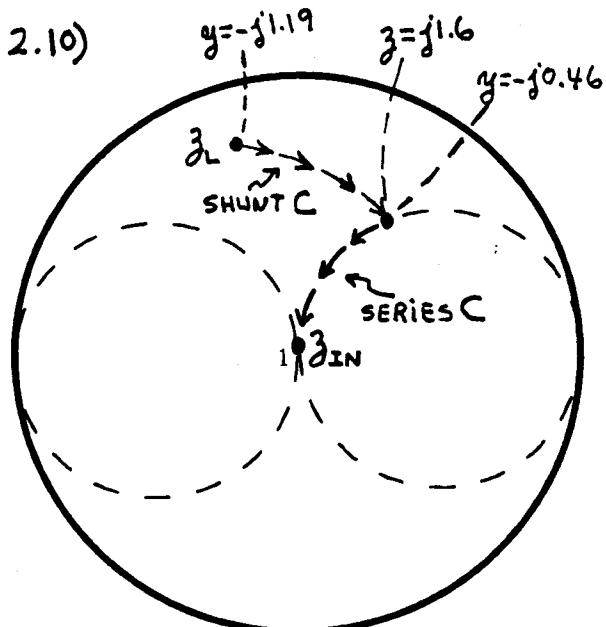


$$\text{SHUNT C: } y_c = -j0.46 - (-j1.19) = j0.73$$

$$Z_c = \frac{50}{y_c} = -j68.5 \Omega$$

$$\text{SERIES C: } z_c = 0 - j1.6 = -j1.6$$
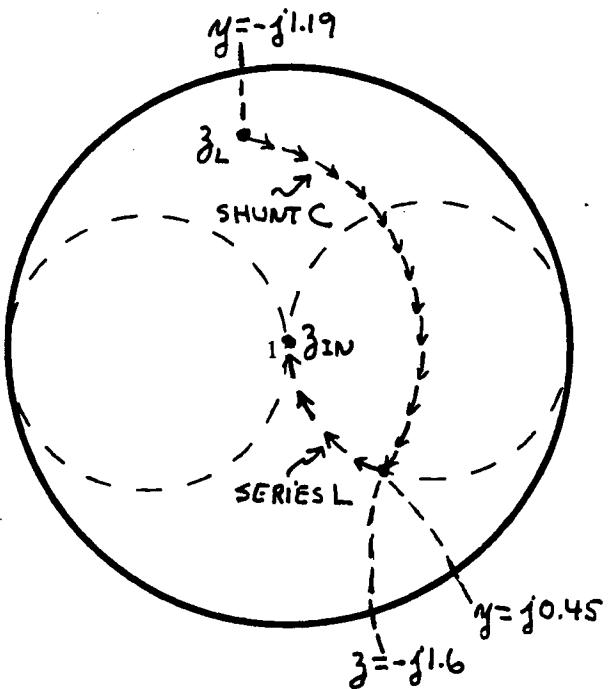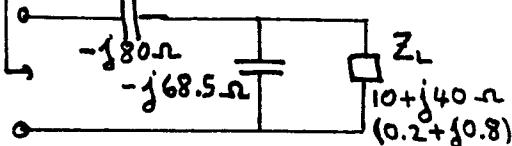
$$Z_{IN} = 50 \Omega \quad Z_c = 50 z_c = -j80 \Omega$$





$$\text{SHUNT C: } y_c = j0.46 - (-j1.19) = j1.64$$

$$Z_c = \frac{50}{j1.64} = -j30.5 \Omega$$

$$\text{SERIES L: } z_L = 0 - (-j1.6) = j1.6$$
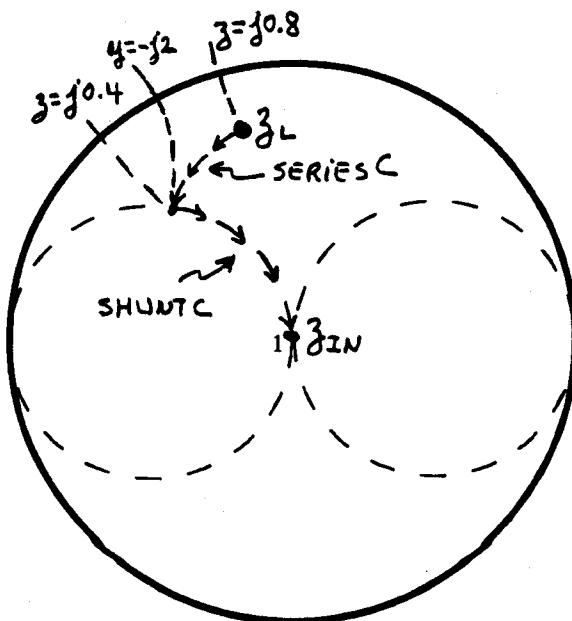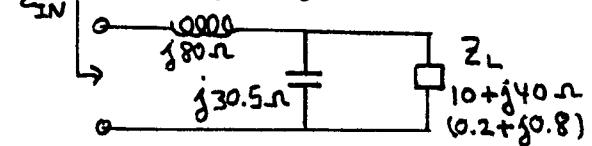
$$Z_{IN} = 50 \Omega \quad Z_L = 50 z_L = j80 \Omega$$




$$\text{SERIES C: } z_c = j0.4 - j0.8 = -j0.4$$


$$Z_c = 50 z_c = -j20 \Omega$$

$$\text{SHUNT C: } y_c = 0 - (-j2) = j2$$

$$Z_c = \frac{50}{j2} = -j25 \Omega$$

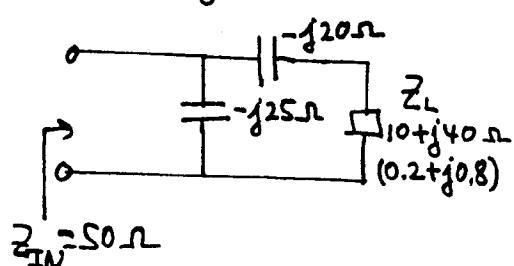

$$Z_{IN} = 50 \Omega$$

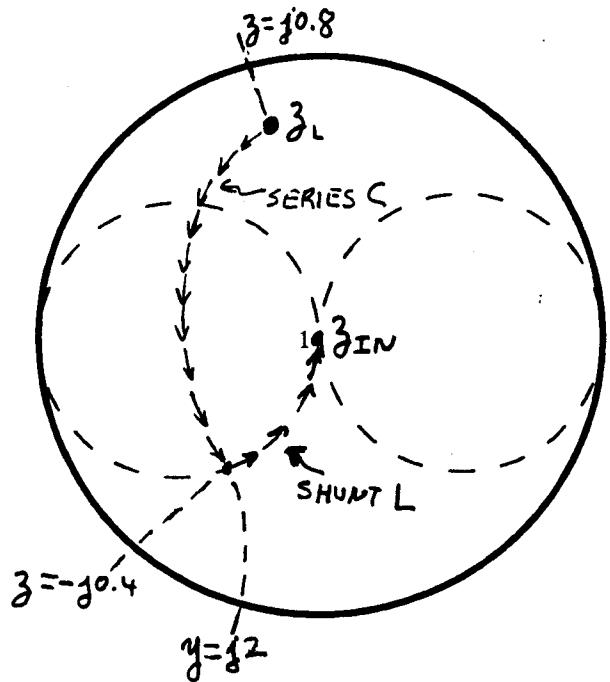


$$\text{SERIES } C: z_c = -j0.4 - j0.8 = -j1.2$$


$$Z_c = 50 z_c = -j60 \Omega$$

$$\text{SHUNT } L: y_L = 0 - j2 = -j2$$

$$Z_L = \frac{50}{y_L} = j25 \Omega$$

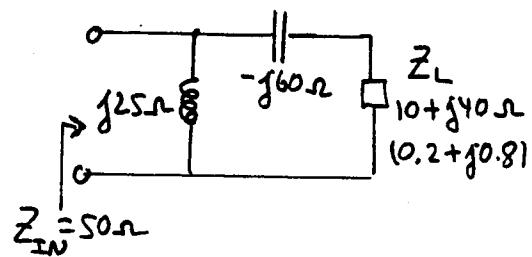
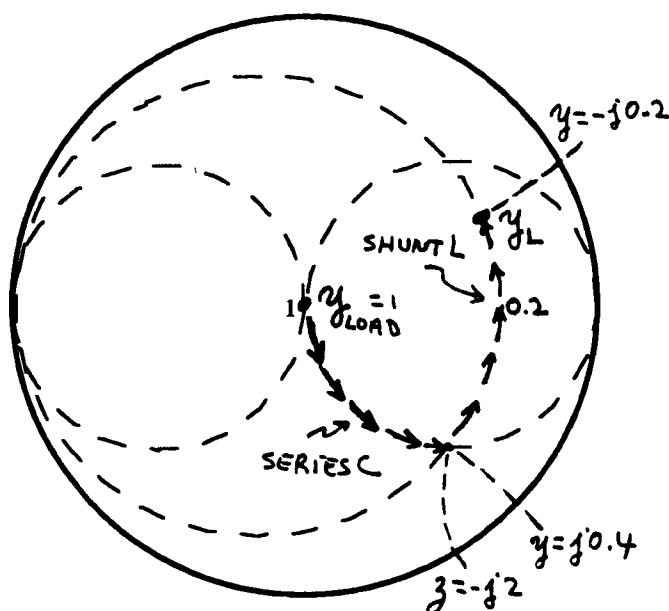
$$2.11) \quad y_L = \frac{Y_L}{Y_0} = Z_0 Y_L = 50(4 - j4)10^{-3} = 0.2 - j0.2$$



$$\text{SERIES } C: z_c = -j2 - j0 = -j2$$

$$Z_c = 50 z_c = -j100 \Omega$$

$$\text{SHUNT } L: y_L = -j0.2 - j0.4 = -j0.6$$

$$Z_L = \frac{50}{y_L} = j83.3 \Omega$$

AT $f = 700 \text{ MHz}$:


$$Z_L = j\omega L = j83.3$$

$$L = \frac{83.3}{2\pi 700 \cdot 10^6} = 18.9 \text{ nH}$$

$$Z_c = \frac{j}{\omega C} = -j100$$

$$C = \frac{1}{100(2\pi 700 \cdot 10^6)} = 2.27 \text{ pF}$$

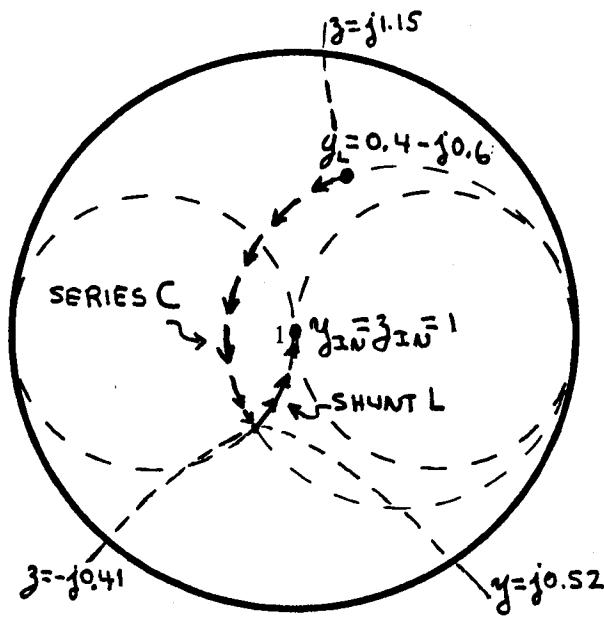2.12) ONLY CIRCUIT (b) CAN MATCH $Y_L = 8 - j12 \text{ mS}$ TO $Z_{IN} = 50 \Omega$.



$$\text{SERIES C: } \beta_c = -j0.41 - j1.15 = -j1.56$$


$$Z_c = 50 \beta_c = -j78 \Omega$$

$$C = \frac{1}{\omega(78)} = \frac{1}{2\pi 10^9 (78)} = 2.04 \text{ pF}$$

$$\text{SHUNT L: } \gamma_L = 0 - j0.52 = -j0.52$$


$$Z_L = \frac{50}{\gamma_L} = j96.15 \Omega$$
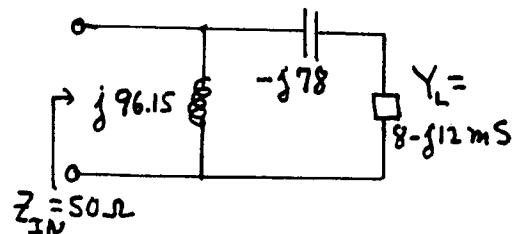
$$L = \frac{96.15}{\omega} = \frac{96.15}{2\pi 10^9} = 15.3 \text{ nH}$$




$$2.13) Z_L = j\omega L = j10^9 50 10^{-9} = j50 \quad \text{OR} \quad \beta_L = j\frac{50}{50} = j1$$
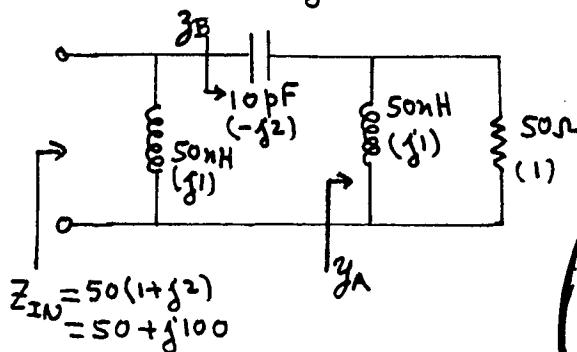
$$Z_c = \frac{1}{j\omega C} = \frac{1}{j10^9 10 10^{-12}} = -j100 \quad \text{OR} \quad \beta_c = -j\frac{100}{50} = -j2$$



$$\beta_{IN} = 1 + j2$$
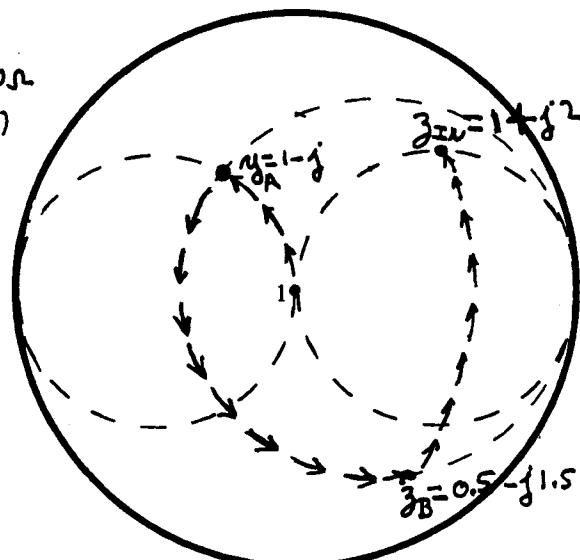
$$Z_{IN} = 50 \beta_{IN} = 50 + j100 \Omega$$



2.14) LET $Z_o = 100\Omega$.

$$\text{THEN } Z_L = \frac{Z_L}{100} = 1 - j$$


$$\text{AND } Z_{IN} = \frac{Z_{IN}}{100} = 0.25 + j0.25$$

$$\text{SHUNT C: } y_c = j1.31 - j0.5 = j1.26$$

$$Z_c = \frac{100}{y_c} = -j126\Omega$$

$$\text{SERIES L: } Z_L = j0.25 - (-j0.67) = j0.92$$

$$Z_L = 100 Z_L = j92\Omega$$

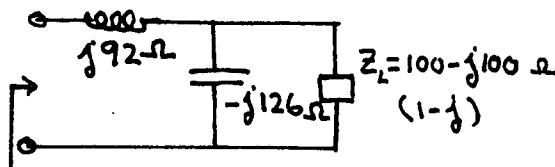

$$Z_{IN} = 25 + j25\Omega \\ (0.25 + j0.25)$$

$$2.15) (a) Z_L = \frac{50}{50} = 1$$

$$Z_{IN} = \frac{20 + j20}{50} = 0.4 + j0.4$$

DRAW THE $Q=5$ CIRCLES (SEE FIG. 2.4.16)

THE MOTION FROM A TO B -- SERIES L_1 :

$$\text{AT B: } Z_B = 1 + j3$$

$$Z_{L_1} = j3 \text{ or } Z_{L_1} = j3(50) = j150\Omega$$

THE MOTION FROM B TO C -- SHUNT C:

$$\text{AT B: } y_B = 0.1 - j0.3$$

$$\text{AT C: } y_c = 0.1 + j0.5$$

$$y_c = 0.5 - (-j0.3) = j0.8$$

$$Z_c = \frac{50}{j0.8} = -j62.5\Omega$$




THE MOTION FROM C TO D -- SERIES L_2 :

$$\text{AT C: } Z_C = 0.4 - j1.9$$

$$\text{AT D: } Z_D = 0.4 + j0.4$$

$$Z_{L_2} = j0.4 - (-j1.9) = j2.3$$

$$Z_{L_2} = 50(j2.3) = j115\Omega$$

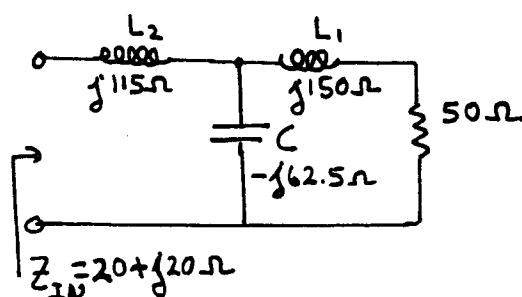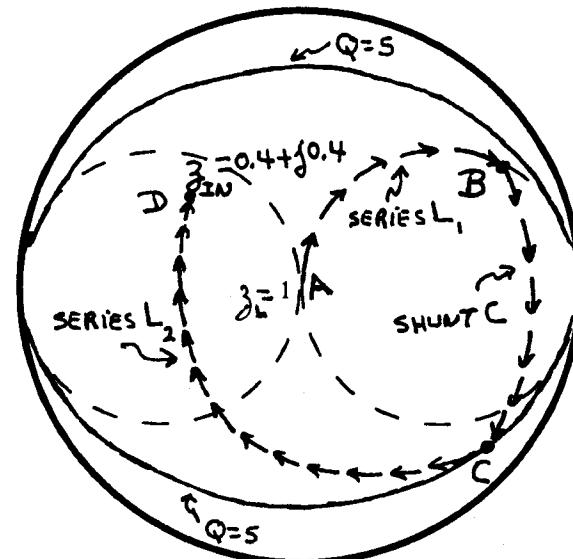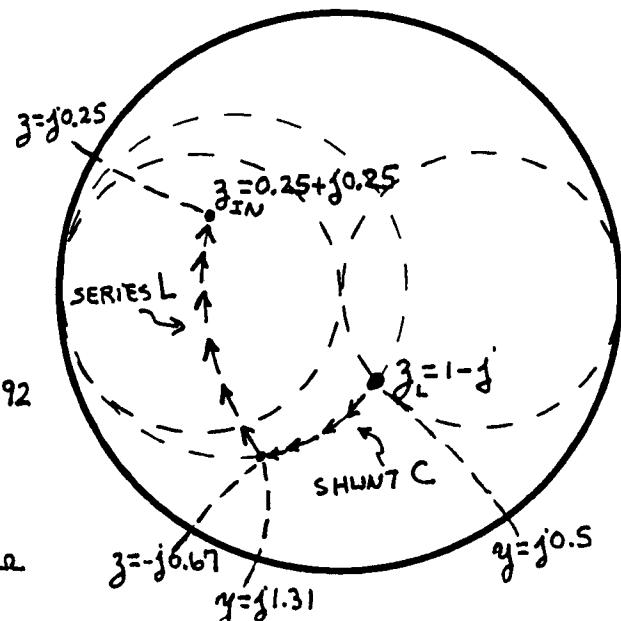

(b) $\beta_L = 1$ AND $\beta_{IN} = 0.5$

$$\text{AT } B: y_B = 1 - j2.6, \beta_B = 0.13 + j0.335$$

$$\text{AT } C: y_C = 2 - j3.4, \beta_C = 0.13 + j0.215$$

$$\text{AT } D: y_D = 2, \beta_D = \beta_{IN} = 0.5$$

$$\text{SHUNT } L: y_L = -j2.6$$



$$Z_L = \frac{50}{-j2.6} = j19.2 \Omega$$

$$\text{SERIES } C_1: \beta_{C_1} = j0.215 - j0.335 = -j0.12$$

$$Z_{C_1} = 50(-j0.12) = -j6 \Omega$$

$$\text{SHUNT } C_2: y_{C_2} = 0 - (-j3.4) = j3.4$$
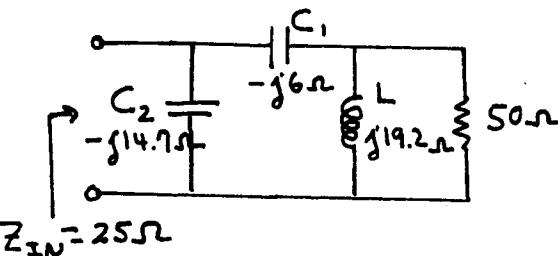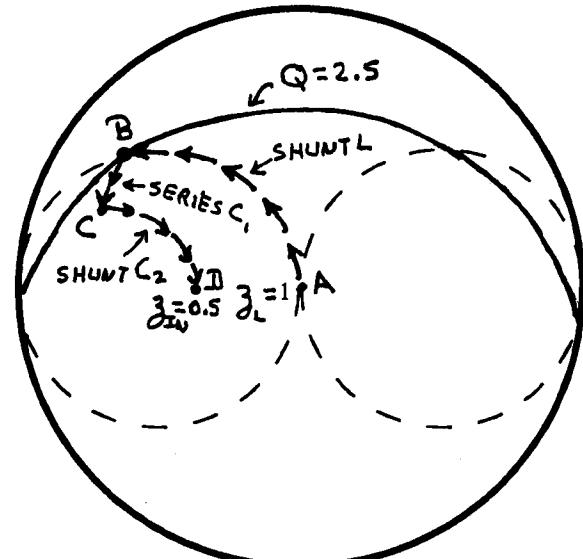
$$Z_{C_2} = \frac{50}{j3.4} = -j14.7 \Omega$$



2.16)(a) From Fig. 2.5.2 with $Z_0 = 50 \Omega$ AND $\epsilon_r = 2.23$ we obtain:

$$\frac{W}{h} \approx 3.1 \text{ OR } W = 3.1(0.7874) = 2.44 \text{ mm}$$

From Fig. 2.5.3 with $W/h = 3.1$ AND $\epsilon_r = 2.23$ we obtain:

$$\frac{\lambda}{\lambda_{TEM}} = 1.08 \text{ OR } \lambda = 1.08 \lambda_{TEM} = 1.08 \frac{\lambda_0}{\sqrt{2.23}} = 0.723 \lambda_0$$

$$\text{SINCE } \lambda = \frac{\lambda_0}{\sqrt{\epsilon_{ff}}} \text{, THEN } \frac{1}{\sqrt{\epsilon_{ff}}} = 0.723 \text{ OR } \epsilon_{ff} = 1.91$$

$$(b) \text{ FROM (2.5.11): } \frac{W}{h} = \frac{2}{\pi} \left\{ B - 1 - \ln(B-1) + \frac{2.23 - 1}{2(2.23)} \left[\ln(B-1) + 0.39 - \frac{0.61}{2.23} \right] \right\} \quad (1)$$

$$\text{WHERE } B = \frac{377\pi}{2(50)\sqrt{2.23}} = 7.931 \quad (2)$$

$$\text{SUBSTITUTE (2) INTO (1) TO OBTAIN: } \frac{W}{h} = 3.073$$

$$\text{FROM (2.5.8): } \lambda = \frac{\lambda_0}{\sqrt{2.23}} \left[\frac{2.23}{1 + 0.63(2.23-1)(3.073)^{0.1255}} \right]^{1/2} = 0.724 \lambda_0$$

$$\frac{1}{\sqrt{\epsilon_{ff}}} = 0.724 \text{ OR } \epsilon_{ff} = 1.91$$


2.17) APPROXIMATE VALUES CAN BE OBTAINED FROM FIGS. 2.5.2 AND 2.5.3.
EXACT VALUES ARE GIVEN IN FIG. 2.5.4.

$$\therefore \frac{W}{h} = 1.5 \text{ OR } W = 1.5(25) = 37.5 \text{ mils}$$

$$\text{FROM FIG. 2.5.3: } \frac{\lambda}{\lambda_{\text{TEM}}} = 1.18 \text{ OR } \lambda = 1.18 \lambda_{\text{TEM}} = \frac{1.18 \cdot 310^9}{\sqrt{6} \cdot 10^9} = 14.45 \text{ cm}$$

$$\begin{aligned} Z_L &= jWL \\ &= j2\pi/10(10/10)^{-9} = j62.8 \Omega \\ Z_L &= \frac{Z_0}{50} = \frac{j62.8}{50} = j1.256 \\ \text{HENCE: } l &= 0.393\lambda \end{aligned}$$
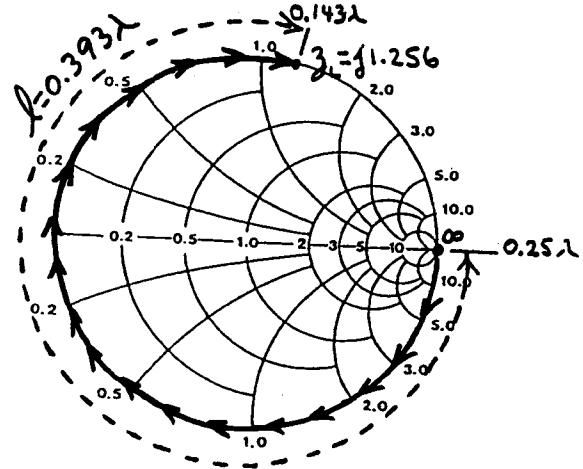
$$\begin{aligned} \text{OR} \\ l &= 0.393(14.45) = 5.68 \text{ cm} \\ \text{OR} \\ l &= 5.68 \left(\frac{1000}{2.54} \right) = 2,236.2 \text{ mils} \end{aligned}$$



2.18) At $f = 1 \text{ GHz}$, $\lambda_0 = 30 \text{ cm}$. MICROSTRIP: $\epsilon_r = 2.23$, $h = 0.7874 \text{ mm}$

$$\text{LINE WITH } Z_0 = 29.9 \Omega \text{ AND } l = \frac{\lambda}{4}: \quad B = \frac{377\pi}{2(29.9)\sqrt{2.23}} = 13.26$$

$$\frac{W}{h} = \frac{2}{\pi} \left\{ 13.26 - 1 - \ln(2(13.26) - 1) + \frac{2.23 - 1}{2(2.23)} \left[\ln(13.26 - 1) + 0.39 - \frac{0.61}{2.23} \right] \right\} = 6.203$$

$$\therefore W = 6.203 h = 6.203(0.7874) = 4.884 \text{ mm}$$

$$\lambda = \frac{\lambda_0}{\sqrt{2.23}} \left[\frac{2.23}{1 + 0.63(2.23 - 1)(6.203)^{0.1255}} \right]^{1/2} = 0.712\lambda_0$$

$$\text{NOTE: SINCE } \lambda = \frac{\lambda_0}{\sqrt{\epsilon_{ff}}} \text{ THEN } \frac{1}{\sqrt{\epsilon_{ff}}} = 0.712 \text{ OR } \epsilon_{ff} = 1.974$$

$$l = \frac{\lambda}{4} = 0.25(0.712\lambda_0) = 0.25(0.712)(30) = 5.34 \text{ cm}$$

SIMILARLY, WE OBTAINED:

$$\underline{Z_0 = 52.64 \Omega, l = 3\lambda/8}$$

$$\underline{\frac{W}{h} = 2.89 \text{ OR } W = 2.27 \text{ mm}}$$

$$\underline{\lambda = 0.726\lambda_0, \epsilon_{ff} = 1.89}$$

$$\underline{l = \frac{3\lambda}{8} = \frac{3}{8}(0.726)(30) = 8.167 \text{ cm}}$$

$$\underline{Z_0 = 95.2 \Omega, l = 3\lambda/8}$$

$$\underline{\frac{W}{h} = 0.99, W = 0.779 \text{ mm}}$$

$$\underline{\lambda = 0.747\lambda_0, \epsilon_{ff} = 1.79}$$

$$\underline{l = \frac{3\lambda}{8} = \frac{3}{8}(0.747)(30) = 8.4 \text{ cm}}$$

$$\underline{Z_0 = 79 \Omega, l = \lambda/4}$$

$$\underline{\frac{W}{h} = 1.44, W = 1.134 \text{ mm}}$$

$$\underline{\lambda = 0.74\lambda_0, \epsilon_{ff} = 1.825}$$



$$\underline{l = \frac{\lambda}{4} = 5.55 \text{ cm}}$$

$$2.19) (a) Z_{IN} = \frac{Z_{IN}}{50} = 2 - j2$$

$$y_{IN} = \frac{1}{Z_{IN}} = 0.25 + j0.25$$

$$l_1 = 0.339\lambda - 0.25\lambda = 0.089\lambda$$

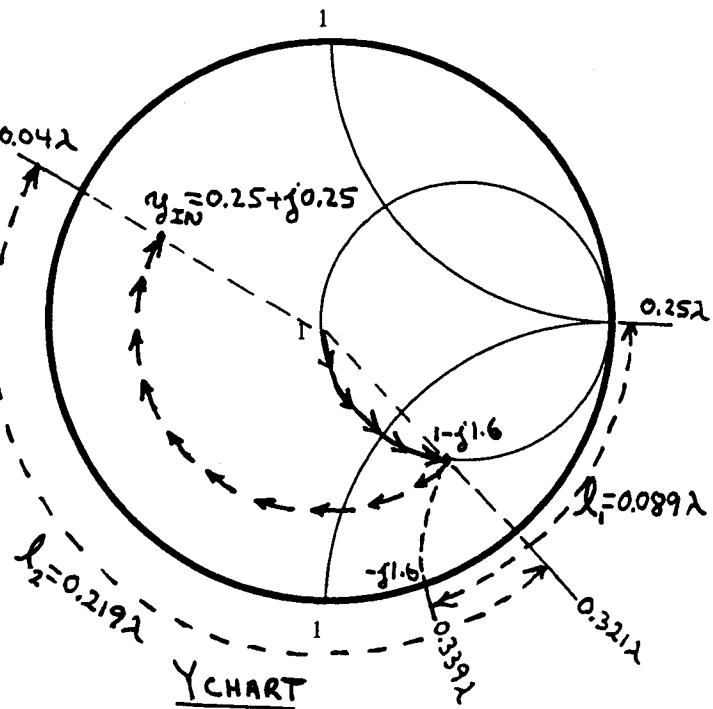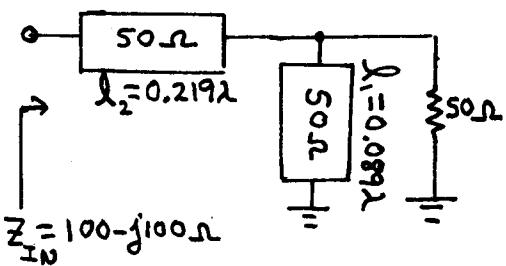
$$l_2 = 0.042 + (0.5\lambda - 0.321\lambda) = 0.219\lambda$$



(b) If l_1 is an open-circuited stub, then

$$l_1 = 0.25\lambda + 0.089\lambda = 0.339\lambda$$

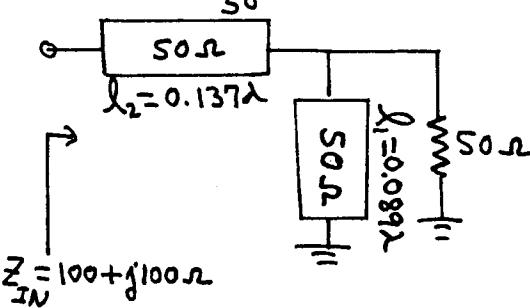(c) For $Z_{IN} = \frac{Z_{IN}}{50} = 2 + j2$, one answer is:



IF l_1 is an open-circuited stub, then

$$l_1 = 0.25\lambda + 0.089\lambda = 0.339\lambda$$


$$2.20) (a) Z_L = \frac{15 + j25}{50} = 0.3 + j0.5$$

$$y_L = \frac{1}{Z_L} = 0.882 - j1.47$$

ROTATE, ALONG A CONSTANT IMPEDANCE CIRCLE, FROM y_L UNTIL THE UNIT CONDUCTANCE CIRCLE IS REACHED AT y_x .

$$y_x = 1 + j1.55$$
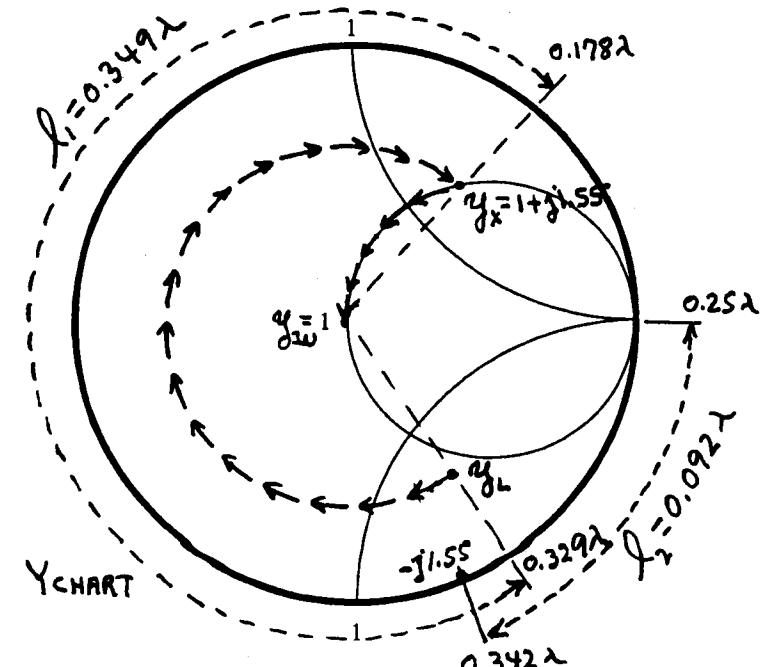
$$l_1 = 0.178\lambda + (0.5\lambda - 0.329\lambda) \\ = 0.349\lambda$$



$$y_{IN} = y_{sc} + y_x$$

$$1 = y_{sc} + (1 + j1.5S)$$


$$\text{HENCE, } y_{sc} = -j1.5S$$

The LENGTH ℓ_2 OF THE SHORT-CIRCUITED STUB MUST HAVE

$$y_{sc} = -j1.5S$$

FROM THE Y SMITH CHART:
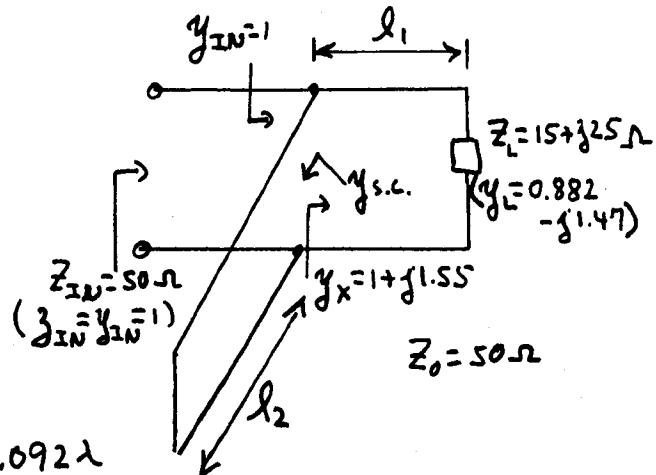
$$\ell_2 = 0.342\lambda - 0.25\lambda = 0.092\lambda$$



(b) IF THE CHARACTERISTIC IMPEDANCE OF THE STUB IS $Z_0' = 100 \Omega$.

$$Z_{sc} = \frac{50}{y_{sc}} = \frac{50}{-j1.5S} = j32.26 \Omega$$

$$\text{THEN: } j32.26 = jZ_0' \tan \beta d = j100 \tan \beta d \Rightarrow \beta d = 0.312$$

$$d \equiv \ell_2 = \frac{0.312}{2\pi/\lambda} = 0.05\lambda$$

ANOTHER WAY: NORMALIZE Z_{sc} WITH Z_0' , $\bar{Z}_{sc} = j \frac{32.26}{100} = j0.323$

THEN: $y_{sc} = \frac{1}{\bar{Z}_{sc}} = -j3.09$. LOCATE $y_{sc} = -j3.09$ IN THE

Y SMITH CHART, AND READ $\ell_2 = 0.302\lambda - 0.25\lambda = 0.052\lambda$

$$2.21) (a) Y_{IN} = G_{IN} + jB_{IN} = 50 + j40 \text{ mS} , R_{IN} = \frac{1}{G_{IN}} = \frac{1}{50 \cdot 10^{-3}} = 20 \Omega$$

$$Z_{01} = \sqrt{Z_L R_{IN}} = \sqrt{50(20)} = 31.62 \Omega$$

IN A SHORT-CIRCUITED $\frac{3\lambda}{8}$ STUB: $Y_{sc} = jY_{02}$. HENCE, $jY_{02} = jB_{IN} = j40 \text{ mS}$

$$\text{OR } Y_{02} = 40 \text{ mS} , Z_{02} = \frac{1}{Y_{02}} = 25 \Omega$$

$$(b) Y_{IN} = G_{IN} - jB_{IN} = 50 - j40 \text{ mS} , R_{IN} = \frac{1}{G_{IN}} = 20 \Omega.$$

THEN, $Z_{01} = \sqrt{50(20)} = 31.62 \Omega$. IN A SHORT-CIRCUITED $\frac{\lambda}{8}$ STUB:

$$Y_{sc} = -jY_{02} . \text{ HENCE, } Y_{02} = 40 \text{ mS OR } Z_{02} = \frac{1}{40 \cdot 10^{-3}} = 25 \Omega.$$

$$(c) Y_{IN} = G_{IN} + jB_{IN} = 10 + j20 \text{ mS} , R_{IN} = \frac{1}{G_{IN}} = \frac{1}{10 \cdot 10^{-3}} = 100 \Omega$$

THEN, $Z_{01} = \sqrt{50(100)} = 70.7 \Omega$. IN AN OPEN-CIRCUITED $\frac{\lambda}{8}$ STUB:

$$Y_{0c} = jY_{02} . \text{ HENCE, } Y_{02} = 20 \text{ mS OR } Z_{02} = \frac{1}{20 \cdot 10^{-3}} = 50 \Omega.$$

$$(d) Y_{IN} = 10 - j20 \text{ mS} . \text{ HENCE: } Z_{01} = \sqrt{50(100)} = 70.7 \Omega.$$

$$\text{IN AN OPEN-CIRCUITED } \frac{3\lambda}{8} \text{ STUB: } Y_{0c} = -jY_{02} . \text{ HENCE, } Z_{02} = \frac{1}{Y_{02}} = \frac{1}{20 \cdot 10^{-3}} = 50 \Omega.$$

$$2.22(a) \Gamma_n = 0.5 e^{j90^\circ}, y_n = 0.6 + j0.8$$

$$\therefore y_n = \frac{1}{\Gamma_n} = 0.6 - j0.8$$

FROM THE SMITH CHART:

$$l_1 = 0.136\lambda, l_2 = 0.375\lambda - 0.166\lambda \\ = 0.209\lambda$$

IN FIG. P.22(b):

$$Y = \frac{0.6 - j0.8}{50} = 12 - j16 \text{ mS}$$

$$\therefore Z_{01} = \sqrt{50 \left(\frac{1}{12-16j} \right)} = 64.5 \Omega$$

USING A $\frac{3\lambda}{8}$ OPEN-CIRCUITED STUB:

$$-jY_{02} = -j16 \text{ mS}, \text{OR } Y_{02} = 16 \text{ mS}$$

$$Z_{02} = \frac{1}{16 \cdot 10^3} = 62.5 \Omega$$

(b) BALANCED FORM OF THE STUBS.


$$\text{FOR FIG. P.22(a): } y_{bal} = j \frac{1.15}{2} = j0.575 \Rightarrow l_{1(bal)} = 0.083\lambda$$

$$\text{FOR FIG. P.22(b): } Z_{02(bal)} = 2(62.5) = 125 \Omega$$

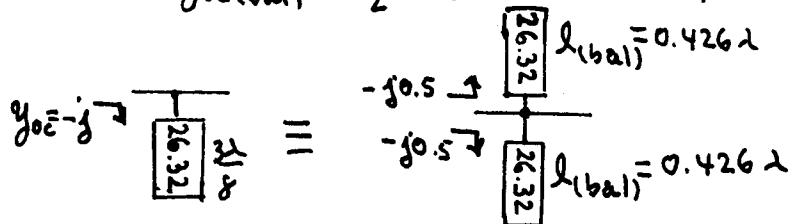2.23) THE $\frac{3\lambda}{8}$ STUB WITH $Z_0 = 26.32 \Omega$ HAS AN ADMITTANCE OF $-j0.0385$.

$$\text{IN A } Z_0 = 26.32 \Omega \text{ SYSTEM: } y_{oc} = (26.32)(-j0.038) = -j1$$

$$\text{THEN: } y_{oc(bal)} = -j \frac{1}{2} = -j0.5 \Rightarrow l_{1(bal)} = 0.426\lambda$$



THE $\frac{3\lambda}{8}$ STUB WITH $Z_0 = 47.6 \Omega$ HAS AN ADMITTANCE OF $-j0.021 \text{ S}$.

$$y_{oc} = 47.6(-j0.021) = -j1$$


$$\text{THEN: } y_{oc(bal)} = -j \frac{1}{2} = -j0.5 \Rightarrow l_{1(bal)} = 0.426\lambda$$

$$2.24) (a) \quad \Gamma_L = 0.4 \angle -120^\circ, \quad Z_L = 0.538 - j0.444, \quad Y_L = \frac{1}{Z_L} = 1.105 + j0.912$$


$$Y_L = \frac{Y_L}{50} = 22 + j18 \text{ mS}$$

$$\text{HENCE: } Z_{o1} = \sqrt{50 \left(\frac{1}{22.10^3} \right)} = 47.67 \Omega \text{ AND}$$
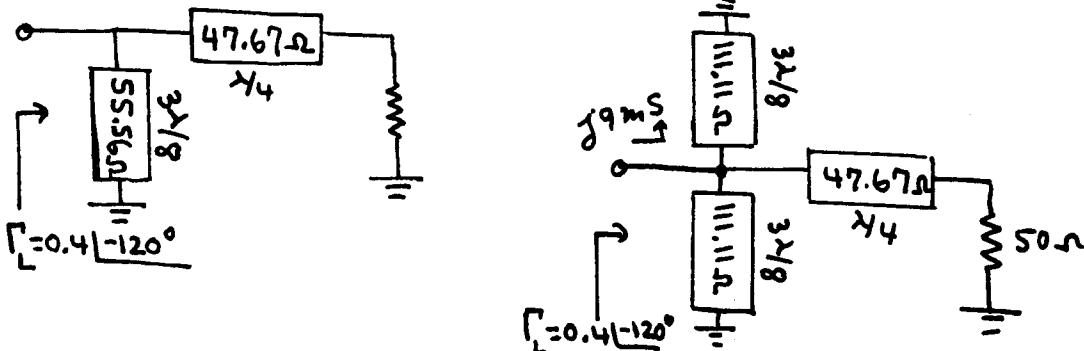
$$jY_{o2} = j18 \text{ mS} \text{ OR } Z_{o2} = \frac{1}{Y_{o2}} = \frac{1}{18.10^{-3}} = 55.56 \Omega$$



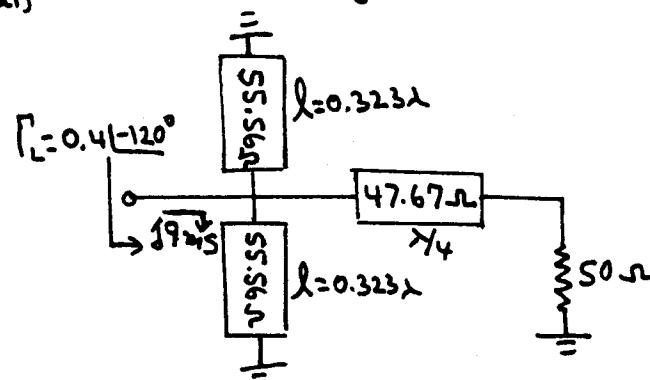(b) EACH SIDE OF THE BALANCE STUBS HAS AN ADMITTANCE OF $j9 \text{ mS}$. IF ITS CHARACTERISTIC IMPEDANCE IS $Z_o = \frac{111.11}{2} = 55.56 \Omega$, THEN $\gamma_{(bal)} = j9 \cdot 10^{-3} (55.56) = j0.5$. HENCE: $l = 0.323 \lambda$.



$$2.25) \quad \Gamma_L = 0.8 \angle 160^\circ, \quad Y_L = \frac{1}{Z_L} = 2.64 - j4$$

$$\Gamma_L = 0.7 \angle 20^\circ, \quad Y_L = \frac{1}{Z_L} = 0.182 - j0.171$$


THE DESIGN OF THE MATCHING CIRCUITS IS SHOWN IN THE Y SMITH CHARTS.

MATCHING TO Γ_n :


OPEN STUB LENGTH: $l_1 = 0.192\lambda$

SERIES TRANS. LINE: $l_2 = 0.08\lambda$

$$l_2 = 0.08\lambda$$

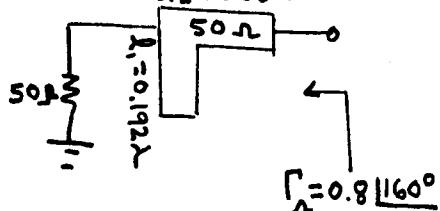

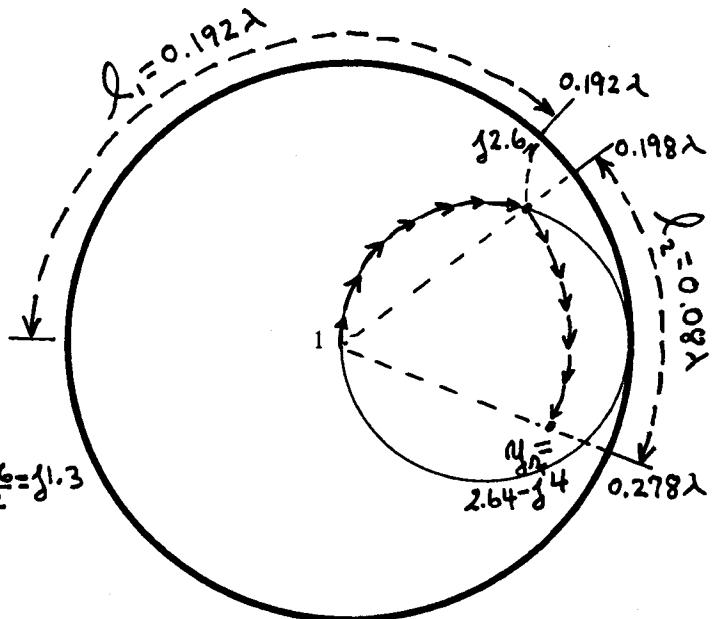
BALANCED SHUNT STUBS: $Y_{(bal)} = \frac{j2.6}{2} = j1.3$
LENGTH OF EACH SIDE: $l'_1 = 0.146\lambda$




MATCHING TO Γ_L :

SHORT-CIRCUITED STUB LENGTH: $l_1 = 0.076\lambda$


SERIES TRANS. LINE: $l_2 = 0.159\lambda$

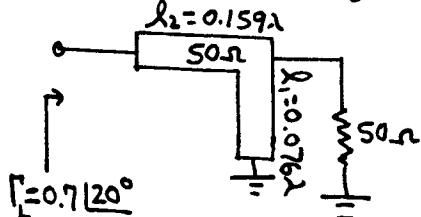

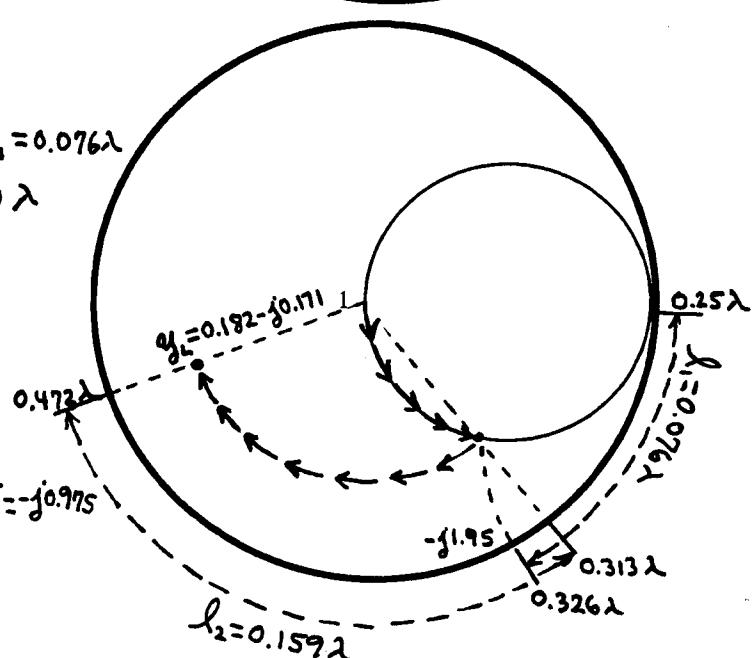
BALANCED SHUNT STUBS: $Y_{(bal)} = -j\frac{1.95}{2} = -j0.975$
LENGTH OF EACH SIDE: $l'_1 = 0.127\lambda$



AMPLIFIER DIAGRAM

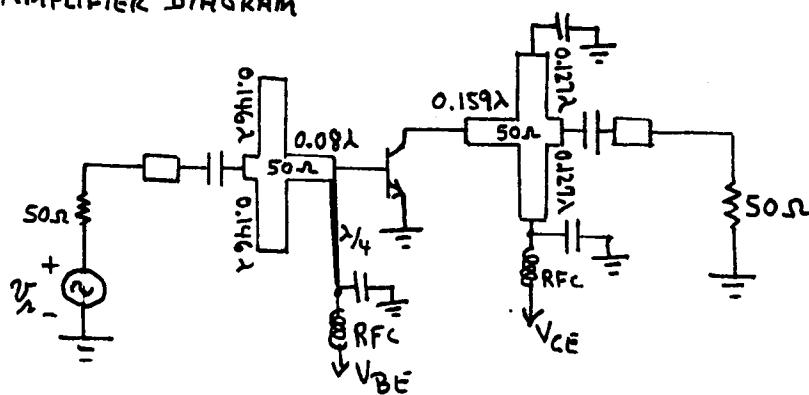


2.26) (a)

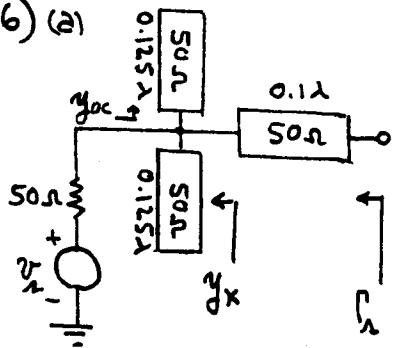

THE ADMITTANCE OF THE 0.125λ STUB
IS: $y_{oc} = j$

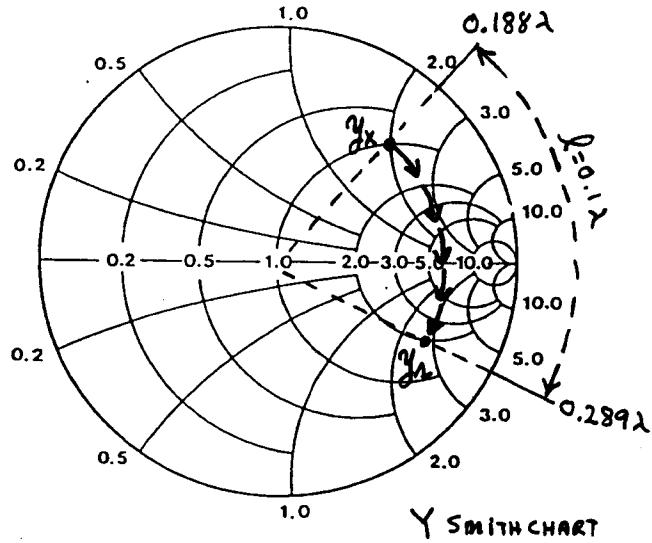
$$\text{HENCE: } y_x = 1 + j + j = 1 + 2j$$



LOCATE y_x IN THE Γ CHART, AND ROTATE 0.1λ TO FIND y_2 . HENCE

$$y_2 = 2 - j2.7 \text{ AND } \Gamma_2 = 0.71 \angle 152^\circ$$

(b)

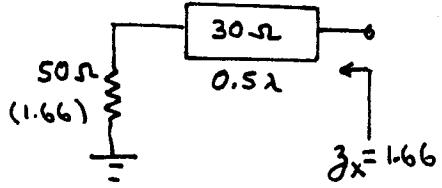

NORMALIZING WITH $Z_0 = 30\Omega$

$$j = \frac{50}{30} = 1.66$$

HENCE, THE IMPEDANCE z_x AT 0.5λ
FROM THE LOAD END IS:


$$z_x = 1.66 \text{ OR } Z_x = 30(1.66) = 50\Omega$$

$$\text{AND } Y_x = \frac{1}{Z_x} = 20 \text{ mS}$$

THE 75Ω , 0.46λ BALANCE STUB HAS: $y_{oc} = -j0.26$ OR

$$Y_{oc, total} = 2(-j0.26) = -j0.52$$
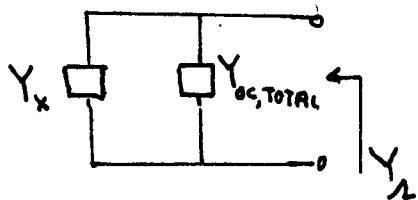
$$Y_{oc, total} = -j\frac{0.52}{75} = -j7 \text{ mS}$$



$$Y_2 = Y_x + Y_{oc, total}$$

$$Y_2 = 20 - j7 \text{ mS}$$

IN A 50Ω SYSTEM: $y_2 = 50Y_2 = 1 - j0.35$

$$z_2 = \frac{1}{y_2} = 0.891 + j0.312$$

$$\text{AND } \Gamma_2 = 0.172 \angle 99.9^\circ$$

$$2.27)(a) \lambda = \frac{3 \cdot 10^{10}}{6 \cdot 10^9} = 5 \text{ cm}, \ell_1 = 1.25 \text{ cm} = 1.25 \frac{\lambda}{5} = \frac{\lambda}{4}$$

$$\ell_2 = 1.87 \text{ cm} = 1.87 \frac{\lambda}{5} = 0.375 \lambda = \frac{3\lambda}{8}$$

FOR THE $\frac{\lambda}{4}$ LINE:

$$Z_x = \frac{Z_0^2}{Z_L} = \frac{30^2}{50} = 18 \Omega$$

$$Y_x = \frac{1}{Z_x} = 56 \text{ mS}$$

FOR THE $\frac{3\lambda}{8}$ STUB:

$$y_{oc} = -j, Y_{oc} = \frac{1}{27}(-j) = -j37 \text{ mS}$$

$$\text{HENCE: } Y_L = Y_x + Y_{oc} = 56 - j37 \text{ mS}$$

IN A 50Ω SYSTEM: $y_L = 50 Y_L = 2.8 - j1.85$ AND $\Gamma_L = 0.61 \angle 160.2^\circ$

(b) FOR BALANCE STUBS USE $Z_0 = 2(27) = 54 \Omega$ WITH LENGTHS OF $3\frac{\lambda}{8}$.

$$2.28) \Gamma_{IN} = 0.5 \angle 100^\circ, z_{IN} = 0.527 + j0.692$$

THE $50 \Omega, 0.15\lambda$ TRANSFORMS z_{IN} TO THE IMPEDANCE $z_x = 2.94 - j0.74$,

$$\text{OR } y_x = \frac{1}{z_x} = 0.32 + j0.08$$

THE ADMITTANCE OF THE $\frac{\lambda}{8}$ STUB IS: $y_{oc} = j$. HENCE, FOR THE TWO STUBS: $y_{oc, \text{TOTAL}} = j + j = 2j$

$$\text{THEN, } y_A = y_x + y_{oc, \text{TOTAL}} = 0.32 + j0.08 + j2 \\ = 0.32 + j2.08$$

$$Z_A = 50 y_A = \frac{50}{y_A} = (0.072 - j0.47)50 = 3.6 - j23.5 \Omega$$

2.29)



$$z_L = \frac{Z_L}{50} = 1 - j, z_{IN} = \frac{Z_{IN}}{50} = 0.5 + j0.5$$

$$y_L = \frac{1}{z_L} = 0.5 + j0.5, y_{IN} = \frac{1}{z_{IN}} = 1 - j$$

y_L AND y_{IN} ARE ON THE SAME CONSTANT $| \Gamma |$ CIRCLE. HENCE, A SERIES TRANSMISSION LINE OF LENGTH:

$$l = 0.338\lambda - 0.088\lambda = 0.25\lambda$$

WILL CHANGE y_L TO y_{IN} .

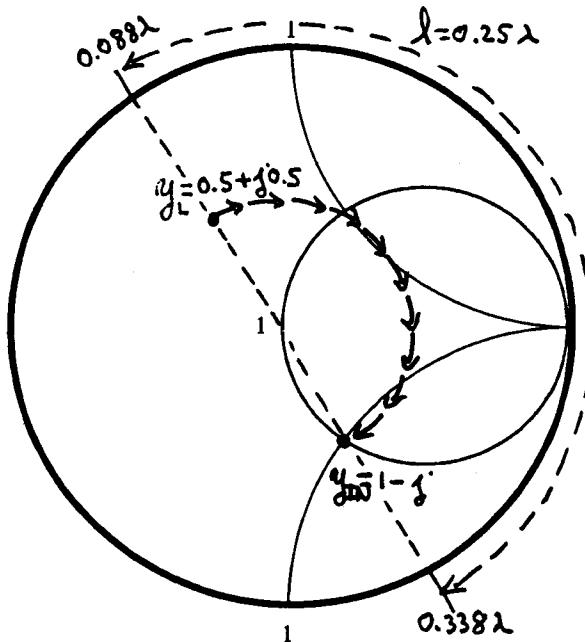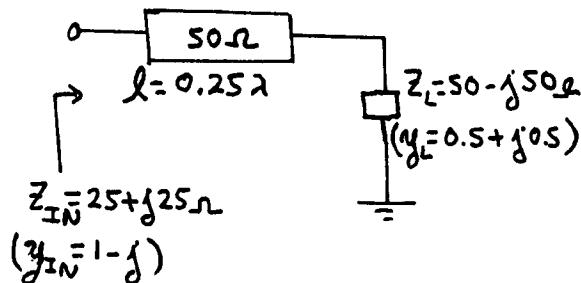

$$2.30) \quad z_L = \frac{50 + j50}{50} = 1 + j$$

THE $50\Omega, 0.125\lambda$ CHANGES $z_L = 1 + j$ TO $z_x = 2 - j$ (OR $y_x = 0.4 + j0.2$)

THE $50\Omega, 0.125\lambda$ STUB HAS: $y_{oc} = j$

$$\text{HENCE: } y_L = y_x + y_{oc} = 0.4 + j0.2 + j = 0.4 + j1.2 \text{ AND } \Gamma_L = 0.728 \angle -104^\circ$$

$$2.31) \quad \text{LOCATE } \Gamma_h = 0.57 \angle 116^\circ \text{ IN}$$

THE SMITH CHART AND READ:

$$z_x = 0.27 \text{ OR } Z_x = 50z_x = 13.5\Omega$$



THE TRANSFORMATION OF 50Ω TO $Z_x = 13.5\Omega$ CAN BE DONE WITH A $\frac{1}{4}\lambda$ LINE

$$\text{WITH: } Z_0 = \sqrt{50(13.5)} = 26\Omega$$

THEN, A SERIES TRANSMISSION LINE OF LENGTH: $l = 0.088\lambda$ TRANSFORMS


$$Z_x = 13.5\Omega \text{ TO } Z_h = 18.5 + j28\Omega$$
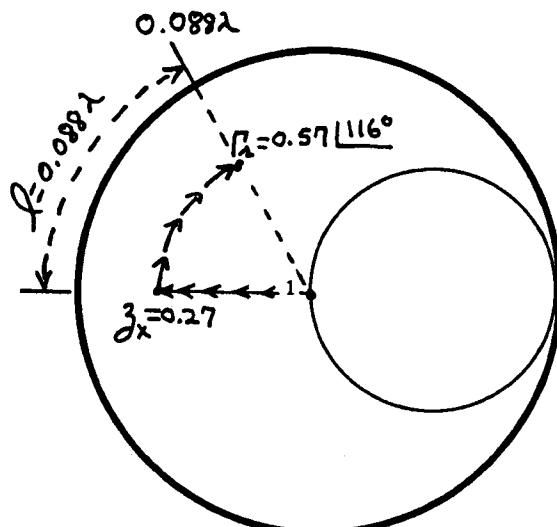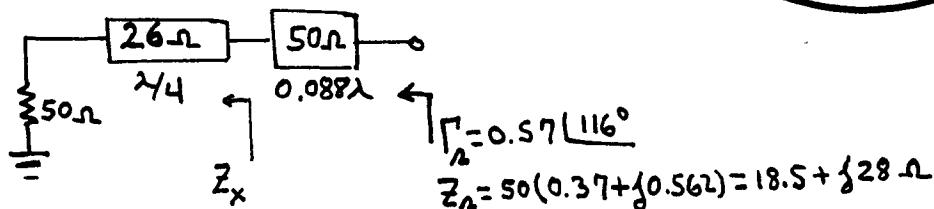
$$\text{OR } \Gamma_h = 0.57 \angle 116^\circ$$



$$2.32)(a) \quad Z_L = \frac{100 + j100}{50} = 2 + j2$$

THE TRANSMISSION LINE PRODUCES A MOTION ALONG A CONSTANT $|Y|$ CIRCLE, AND THE INDUCTOR L PRODUCES A MOTION ALONG A CONSTANT CONDUCTANCE CIRCLE.

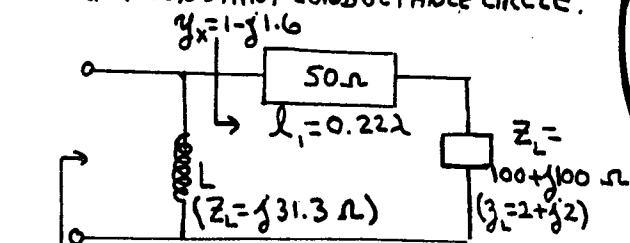

$$Z_{IN} = 50 \Omega$$


($y_{IN} = 1$)

USING A ZY SMITH CHART: ZY CHART

$$l_1 = 0.429\lambda - 0.209\lambda = 0.22\lambda$$

AT y_x : $y_x = 1 - j1.6$. THEN, $y_L = 0 - (j1.6) = -j1.6$
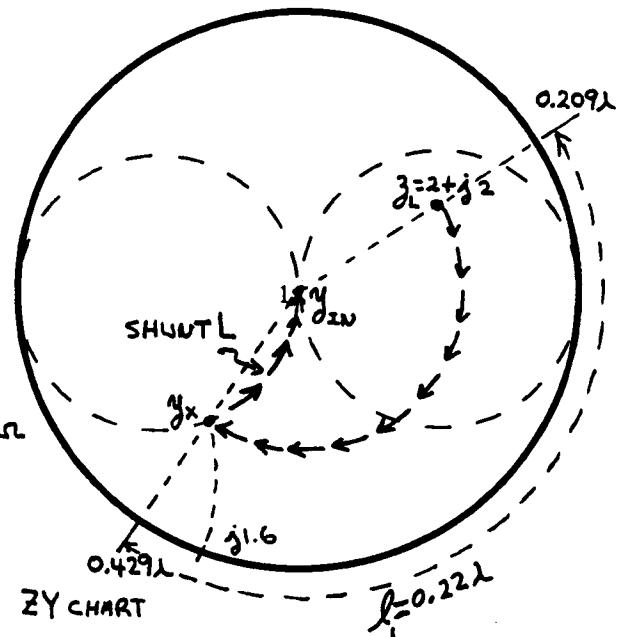
$$\text{OR } Z_L = 50y_L = \frac{50}{-j1.6} = j31.3 \Omega$$





(b) IN THIS CIRCUIT THE INDUCTOR PRODUCES A MOTION ALONG A CONSTANT RESISTANCE CIRCLE.

$$l_1 = 0.322\lambda - 0.209\lambda = 0.113\lambda$$


AT z_x : $z_x = 1 - j1.6$

$$z_L = 0 - (-j1.6) = j1.6$$

$$Z_L = 50z_L = 50(j1.6) = j80 \Omega$$

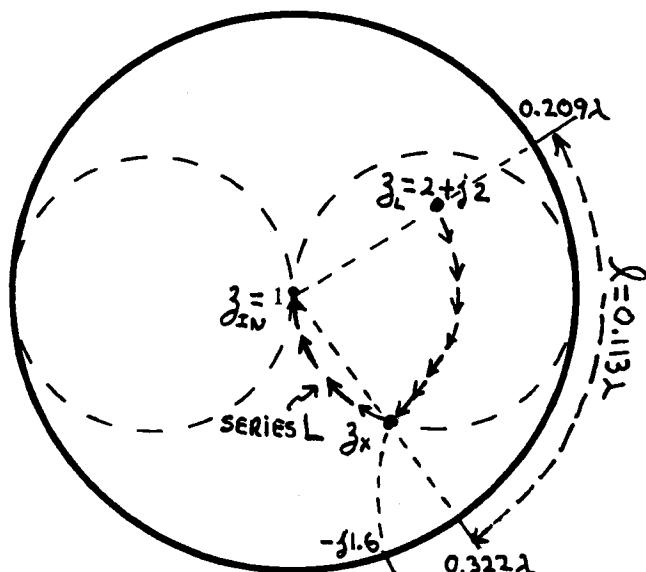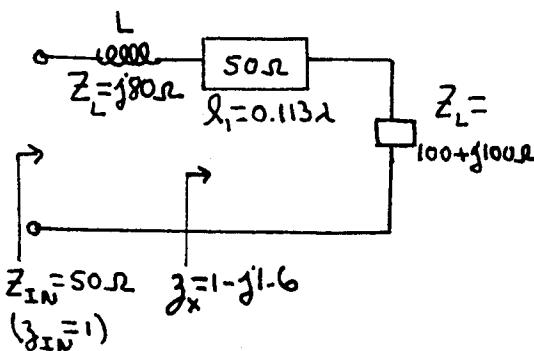
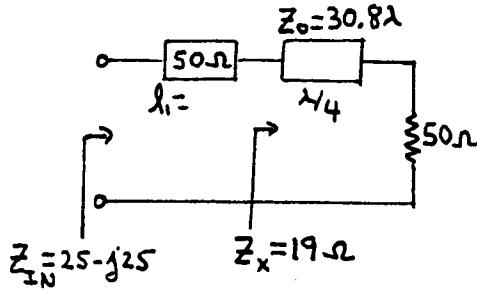
$$2.33)(a) \quad Z_{IN} = \frac{25-j25}{50} = 0.5-j0.5$$



Z_x AND Z_{IN} MUST BE ON THE SAME CONSTANT $|Y|$ CIRCLE. ONE SOLUTION IS SHOWN ON THE SMITH CHART.


$$Z_x = 50 \beta_x = 50(0.38) = 19 \Omega$$

$$\text{THEN: } Z_0 = \sqrt{Z_L Z_x} = \sqrt{50(19)} = 30.8 \Omega$$

$$\text{AND } l_1 = 0.412 \lambda$$

$$(b) \quad Z_{IN} = 0.5 - j0.5, \quad Y_{IN} = \frac{1}{Z_{IN}} = 1 + j$$

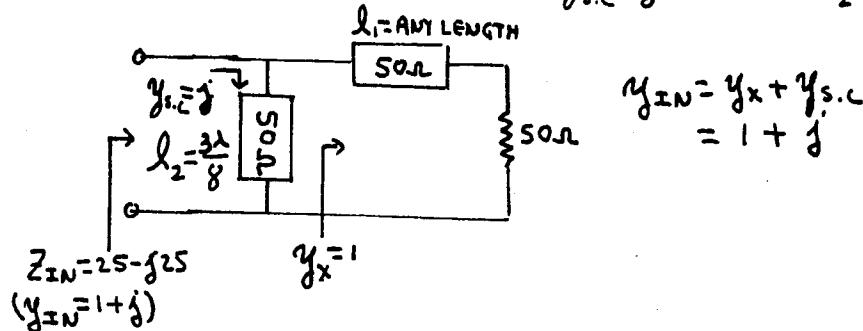
LETTING $Z_0 = 50 \Omega$ AND $l_1 = \text{ANY LENGTH}$, THE ADMITTANCE $y_x = 1$. THEN, THE SHUNT STUB MUST PROVIDE: $y_{s.c.} = j$. HENCE: $l_2 = \frac{3\lambda}{8}$.



$$(c) \quad Z_{IN} = \frac{50 + j50}{50} = 1 + j, \quad Y_{IN} = 0.5 - j0.5, \quad Y_{IN} = 10 - j10 \text{ mS}$$

$$\therefore Z_0 = \sqrt{Z_L Z_x} = \sqrt{50 \left(\frac{1}{10 \cdot 10^{-3}} \right)} = 70.7 \Omega. \text{ THE STUB ADMITTANCE MUST}$$
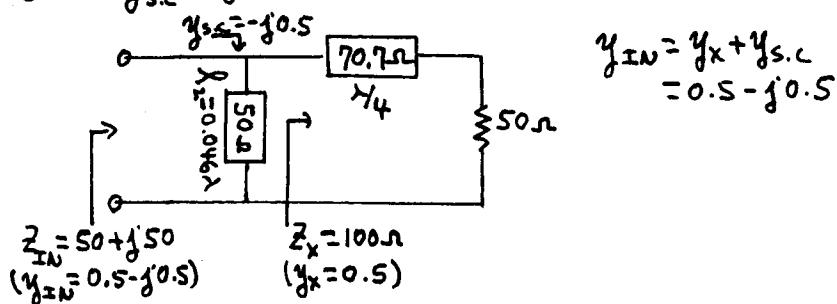
$$\text{BE: } y_{s.c.} = -j0.5. \text{ HENCE: } l_2 = 0.426 \lambda$$



2.34) STARTING WITH (2.6.13):

$$G_T = \frac{(1-|\Gamma_L|^2) |S_{21}|^2 (1-|\Gamma_L|^2)}{|(1-S_{11}\Gamma_L)(1-S_{22}\Gamma_L) - S_{12}S_{21}\Gamma_L\Gamma_L|^2} \quad (1)$$

THE DENOMINATOR CAN BE EXPRESSED AS

$$\begin{aligned} & |1-S_{22}\Gamma_L|^2 \left| 1-S_{11}\Gamma_L - \frac{S_{12}S_{21}\Gamma_L\Gamma_L}{1-S_{22}\Gamma_L} \right|^2 = \\ & |1-S_{22}\Gamma_L|^2 \left| 1-\Gamma_L \left(S_{11} - \frac{S_{12}S_{21}\Gamma_L}{1-S_{22}\Gamma_L} \right) \right|^2 = |1-S_{22}\Gamma_L|^2 |1-\Gamma_L\Gamma_{IN}|^2 \end{aligned}$$

HENCE, (1) CAN BE EXPRESSED IN THE FORM

$$G_T = \frac{1-|\Gamma_L|^2}{|1-\Gamma_L\Gamma_{IN}|^2} |S_{21}|^2 \frac{1-|\Gamma_L|^2}{|1-S_{22}\Gamma_L|^2} \quad (2.6.14)$$

ANOTHER WAY OF WRITING THE DENOMINATOR IS:

$$\begin{aligned} & |1-S_{11}\Gamma_L|^2 \left| 1-S_{22}\Gamma_L - \frac{S_{12}S_{21}\Gamma_L\Gamma_L}{1-S_{11}\Gamma_L} \right|^2 = \\ & |1-S_{11}\Gamma_L|^2 \left| 1-\Gamma_L \left(S_{22} - \frac{S_{12}S_{21}\Gamma_L}{1-S_{11}\Gamma_L} \right) \right|^2 = |1-S_{11}\Gamma_L|^2 |1-\Gamma_L\Gamma_{OUT}|^2 \end{aligned}$$

HENCE, (1) CAN ALSO BE EXPRESSED AS:

$$G_T = \frac{1-|\Gamma_L|^2}{|1-S_{11}\Gamma_L|^2} |S_{21}|^2 \frac{1-|\Gamma_L|^2}{|1-\Gamma_L\Gamma_{OUT}|^2} \quad (2.6.15)$$

$$2.35) \frac{b_1}{b_2} = \frac{S_{11}(1-\Gamma_L S_{22}) + S_{21}\Gamma_L S_{12}}{D}, \quad \frac{b_2}{b_1} = \frac{S_{21}}{D}$$

$$\frac{a_1}{b_2} = \frac{1-S_{22}\Gamma_L}{D}, \quad \frac{a_2}{b_1} = \frac{S_{21}\Gamma_L}{D},$$

$$D = 1 - (S_{11}\Gamma_L + S_{22}\Gamma_L + S_{21}\Gamma_L S_{12}\Gamma_L) + S_{11}\Gamma_L S_{22}\Gamma_L$$

$$\text{Hence: } A_V = \frac{\frac{a_2}{b_2} + \frac{b_2}{b_1}}{\frac{a_1}{b_2} + \frac{b_1}{b_1}} = \frac{S_{21}\Gamma_L + S_{21}}{S_{11}(1-\Gamma_L S_{22}) + S_{21}\Gamma_L S_{12} + 1-S_{22}\Gamma_L}$$

OR

$$A_V = \frac{S_{21}(\Gamma_L + 1)}{1-S_{22}\Gamma_L + S_{11}(1-\Gamma_L S_{22}) + S_{21}\Gamma_L S_{12}}$$

2.36) (a) From (2.8.6), with $\Gamma_L = \Gamma_{out}^* = 0.682 \angle 97^\circ$, we obtain $|\Gamma_b| = 0$.

Then, using (2.8.4), $(VSWR)_{out} = 1$.

(b) When $\Gamma_L = \Gamma_{out}^*$ we have $|\Gamma_b| = 0$ or $\Gamma_b = 0$. Hence,
 $Z_b = Z_o = 50 \Omega$.

(c) $|\Gamma_b| = \left| \frac{\Gamma_{out} - \Gamma_L^*}{1 - \Gamma_{out} \Gamma_L} \right| = \left| \frac{0.5 \angle -60^\circ - 0.682 \angle 97^\circ}{1 - 0.5 \angle -60^\circ (0.682 \angle 97^\circ)} \right| = 0.546$

$$(VSWR)_{out} = \frac{1+0.546}{1-0.546} = 3.41$$

2.37) (a) From (2.8.3), with $\Gamma_a = \Gamma_{in}^* = 0.545 \angle 77.7^\circ$, we obtain $|\Gamma_a| = 0$.

Then, using (2.8.1), $(VSWR)_{in} = 1$.

(b) When $\Gamma_a = \Gamma_{in}^*$ we have $|\Gamma_a| = 0$ or $\Gamma_a = 0$. Hence,
 $Z_a = Z_o = 50 \Omega$

(c) $|\Gamma_a| = \left| \frac{\Gamma_{in} - \Gamma_a^*}{1 - \Gamma_{in} \Gamma_a} \right| = \left| \frac{0.4 \angle 45^\circ - 0.545 \angle -77.7^\circ}{1 - 0.4 \angle 45^\circ (0.545 \angle -77.7^\circ)} \right| = 0.735$

$$(VSWR)_{in} = \frac{1+0.735}{1-0.735} = 6.54$$

3.1) (a) $G_T = \frac{P_L}{P_{AVN}}$, $G_p = \frac{P_L}{P_{IN}}$, $G_A = \frac{P_{AVN}}{P_{AVS}}$, $P_{IN} = P_{AVS} M_2$ ($M_2 \leq 1$),
AND $P_L = P_{AVN} M_L$ ($M_L \leq 1$).

HENCE, [SEE (2.7.29)]: $G_T = G_p M_2$ OR $G_T \leq G_p$, AND
 $G_T = G_A M_L$ OR $G_T \leq G_A$.

$G_T = G_p$ WHEN $\Gamma_2 = \Gamma_{IN}^*$ (OR WHEN $M_2 = 1$)

$G_T = G_A$ WHEN $\Gamma_L = \Gamma_{OUT}^*$ (OR WHEN $M_L = 1$)

(b) G_T IN (3.2.1) AND G_p IN (3.2.3) SHOULD BE IDENTICAL WHEN $\Gamma_2 = \Gamma_{IN}^*$
(i.e., $P_{IN} = P_{AVS}$ WHEN $\Gamma_2 = \Gamma_{IN}^*$). FROM (3.2.1) WITH $\Gamma_2 = \Gamma_{IN}^*$:

$$G_T = \frac{1 - |\Gamma_{IN}|^2}{|1 - \Gamma_{IN} \Gamma_{IN}^*|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2} - \frac{1 - |\Gamma_{IN}|^2}{|1 - \Gamma_{IN}^*|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

HENCE:

$$G_T = G_p = \frac{1}{|1 - \Gamma_{IN}|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

G_T IN (3.2.2) AND G_A IN (3.2.4) SHOULD BE IDENTICAL WHEN $\Gamma_L = \Gamma_{OUT}^*$
(i.e., $P_L = P_{AVN}$ WHEN $\Gamma_L = \Gamma_{OUT}^*$). FROM (3.2.2) WITH $\Gamma_L = \Gamma_{OUT}^*$:

$$G_T = \frac{1 - |\Gamma_L|^2}{|1 - S_{11} \Gamma_L|^2} |S_{21}|^2 \frac{1 - |\Gamma_{OUT}|^2}{|1 - \Gamma_{OUT} \Gamma_{OUT}^*|^2} = \frac{1 - |\Gamma_L|^2}{|1 - S_{11} \Gamma_L|^2} |S_{21}|^2 \frac{1 - |\Gamma_{OUT}|^2}{(1 - |\Gamma_{OUT}|^2)^2}$$

HENCE:

$$G_T = G_A = \frac{1 - |\Gamma_L|^2}{|1 - S_{11} \Gamma_L|^2} |S_{21}|^2 \frac{1}{|1 - \Gamma_{OUT}|^2}$$

3.2) (a) WITH $Z_2 = Z_L = Z_o$ THEN $\Gamma_2 = \Gamma_L = 0$, AND FROM (3.2.1):

$$G_T = |S_{21}|^2$$

(b) FROM (3.2.5): $\Gamma_{IN} = S_{11}$ WHEN $\Gamma_L = 0$. THEREFORE, FROM (3.2.3):

$$G_p = \frac{|S_{21}|^2}{|1 - \Gamma_{IN}|^2} = \frac{|S_{21}|^2}{|1 - |S_{11}|^2|^2}$$

(c) FROM (3.2.6): $\Gamma_{OUT} = S_{22}$ WHEN $\Gamma_L = 0$. THEREFORE, FROM (3.2.4):

$$G_A = \frac{|S_{21}|^2}{|1 - \Gamma_{OUT}|^2} = \frac{|S_{21}|^2}{|1 - |S_{22}|^2|^2}$$

3.3)(a) WITH THE VALUES GIVEN IN THE PROBLEM IT FOLLOWS THAT:

$$\text{FROM (3.2.5): } \Gamma_{IN} = 0.671 \angle 160.72^\circ$$

$$\text{FROM (3.2.6): } \Gamma_{OUT} = 0.615 \angle -82.8^\circ$$

$$\text{FROM (3.2.1): } G_T = 8.575 \text{ OR } 9.33 \text{ dB}$$

$$\text{FROM (3.2.3): } G_p = 9.487 \text{ OR } 9.77 \text{ dB}$$

$$\text{FROM (3.2.4): } G_A = 8.745 \text{ OR } 9.42 \text{ dB}$$

$$(b) P_{AVS} = \frac{|E_1|^2}{8 \operatorname{Re}[Z_1]} = \frac{10^2}{8(50)} = 0.25 \text{ W}, M_\lambda = \frac{G_T}{G_p} = \frac{8.575}{9.487} = 0.904$$

$$P_{IN} = P_{AVS} M_\lambda = 0.25(0.904) = 0.226 \text{ W}$$

$$P_L = G_p P_{IN} = 9.487(0.226) = 2.144 \text{ W}$$

$$P_{AVN} = G_A P_{AVS} = 8.745(0.25) = 2.186 \text{ W}$$

3.4) $\Gamma_\lambda = 0$ AND $\Gamma_L = 0.5 \angle 90^\circ$. HENCE:


$$G_T = G_{TL} = 11.294 \text{ OR } 10.53 \text{ dB}$$


$$G_p = 22.145 \text{ OR } 13.45 \text{ dB}$$

$$G_A = 21.33 \text{ OR } 13.29 \text{ dB}$$


3.5) OBSERVE THAT $\Gamma_{OUT} = S_{22}$ WHEN $\Gamma_\lambda = 0$. THEREFORE, THE ORIGIN (i.e., $\Gamma_\lambda = 0$) IS A STABLE POINT WHEN $|S_{22}| < 1$.

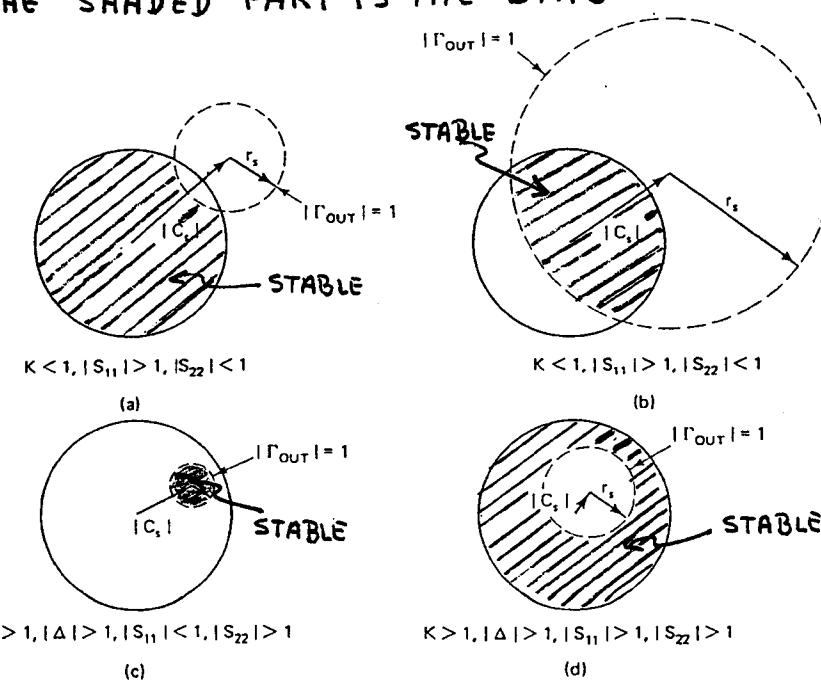THE "SHADED" PART IS THE "STABLE REGION".



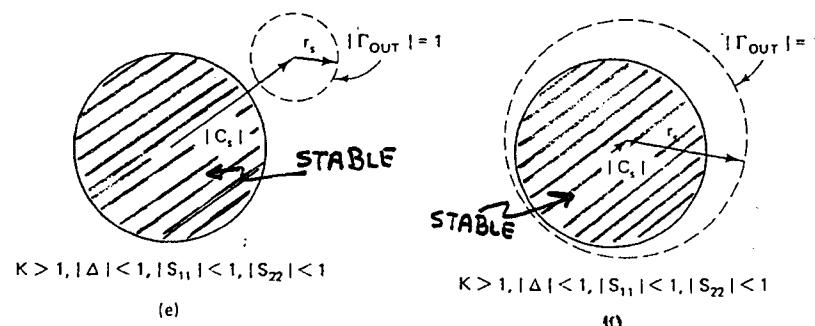


3.6) OBSERVE THAT $\Gamma_{IN} = S_{11}$ WHEN $\Gamma_L = 0$. THEREFORE, THE ORIGIN (i.e., $\Gamma_L = 0$) IS A STABLE POINT WHEN $|S_{11}| < 1$.
 THE "SHADED" PART IS THE "STABLE REGION".

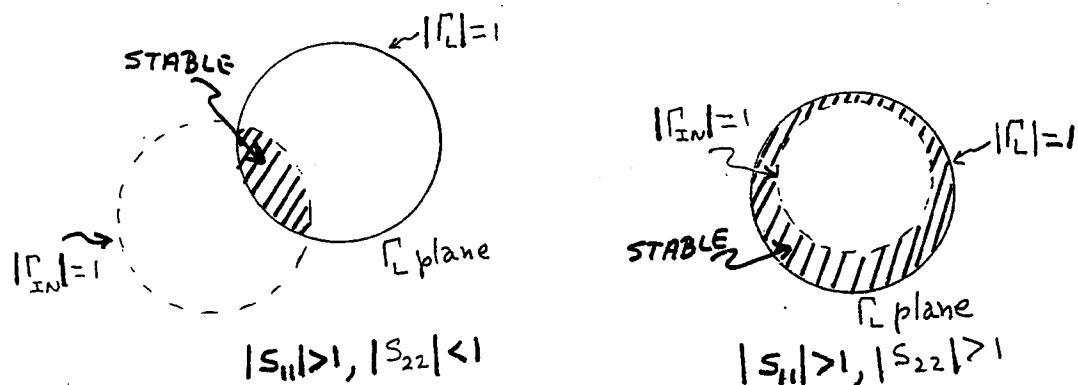

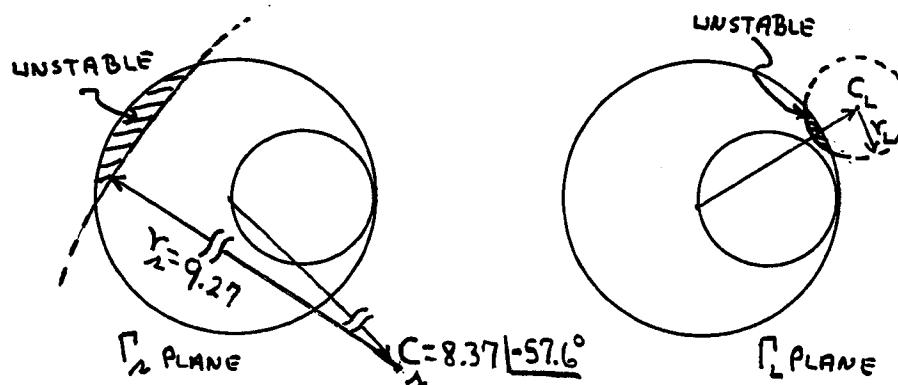3.7) (a) $K = 1.284, \Delta = 0.386$ 134.2° \therefore UNCONDITIONALLY STABLE.
 (b) $K = 0.909, \Delta = 0.402$ -65.04° \therefore POTENTIALLY UNSTABLE.

$$\begin{array}{l} \text{INPUT} \\ \text{STABILITY} \\ \text{CIRCLE} \end{array} \quad \left\{ \begin{array}{l} Y_2 = 9.27 \\ C_2 = 8.37 \angle -57.6^\circ \end{array} \right.$$



$$\begin{array}{l} \text{OUTPUT} \\ \text{STABILITY} \\ \text{CIRCLE} \end{array} \left\{ \begin{array}{l} r_L = 0.19 \\ C_L = 1.18 \quad [29.8^\circ] \end{array} \right.$$



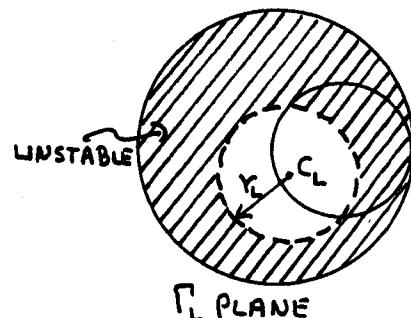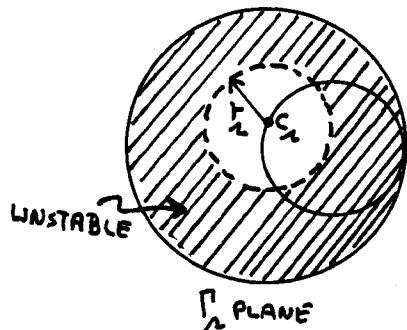
(c) $K = 1.202$, $\Delta = 1.76 \angle 18.5^\circ \therefore$ POTENTIALLY UNSTABLE

$$\begin{array}{l} \text{INPUT} \\ \text{STABILITY} \\ \text{CIRCLE} \end{array} \left\{ \begin{array}{l} Y_L = 0.518 \\ C_L = 0.152 \angle 82.1^\circ \end{array} \right.$$

$$\begin{array}{l} \text{OUTPUT} \\ \text{STABILITY} \\ \text{CIRCLE} \end{array} \left\{ \begin{array}{l} Y_L = 0.494 \\ C_L = 0.239 \angle -58^\circ \end{array} \right.$$




f (GHz)	K	Δ	STABILITY CIRCLE	STABILITY CIRCLE
4	0.412	$0.65 \angle -90.3^\circ$	$Y_L = 0.444, C_L = 1.25 \angle 80.9^\circ$	$Y_L = 3.79, C_L = 4.3 \angle 91.4^\circ$
6	0.56	$0.57 \angle -131.1^\circ$	$Y_L = 0.604, C_L = 1.43 \angle 111.6^\circ$	$Y_L = 6.316, C_L = 6.93 \angle 107.8^\circ$
8	0.78	$0.43 \angle 174.9^\circ$	$Y_L = 0.789, C_L = 1.69 \angle 152.6^\circ$	$Y_L = 7.39, C_L = 8.2 \angle 126.1^\circ$
10	0.89	$0.32 \angle 114^\circ$	$Y_L = 0.759, C_L = 1.72 \angle 171.8^\circ$	$Y_L = 3.49, C_L = 4.41 \angle 150.1^\circ$
14	1.33	$0.17 \angle -2.4^\circ$	$Y_L = 0.513, C_L = 1.62 \angle -110.2^\circ$	$Y_L = 1.87, C_L = 3.08 \angle -171.7^\circ$

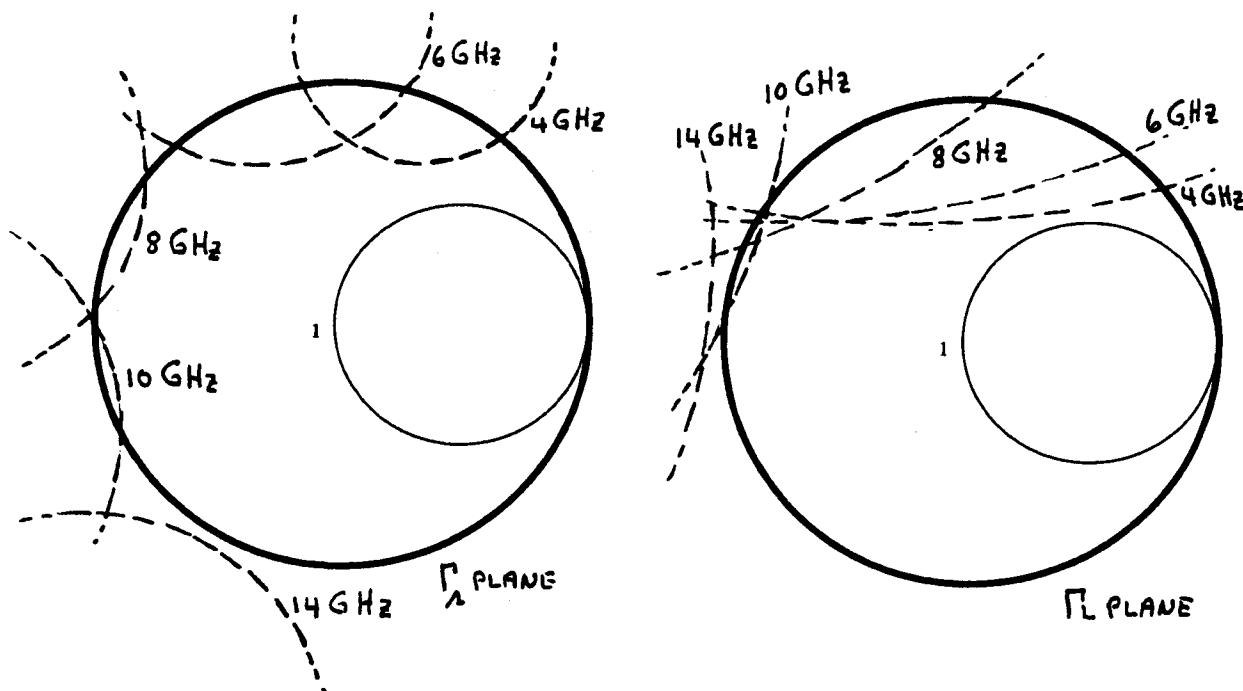


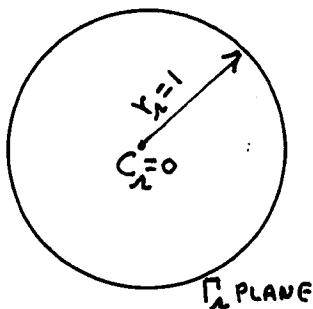3.9) (a) $K=1, \Delta=1$

INPUT
STABILITY
CIRCLE:
 $\begin{cases} Y_2 = 1 \\ C_2 = 0 \end{cases}$




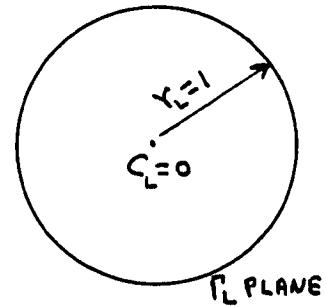OUTPUT
STABILITY
CIRCLE:
 $\begin{cases} Y_L = 1 \\ C_L = 0 \end{cases}$




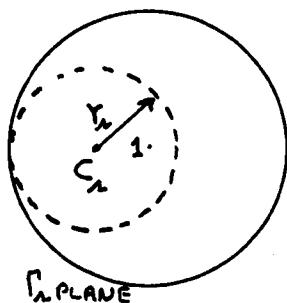(b) $K=1, \Delta=-2.414$

$$\begin{cases} Y_n = 0.55 \\ C_n = 0.45 \angle 180^\circ \end{cases}$$



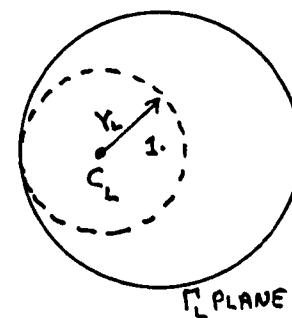
$$\begin{cases} Y_L = 0.55 \\ C_L = 0.45 \angle 180^\circ \end{cases}$$




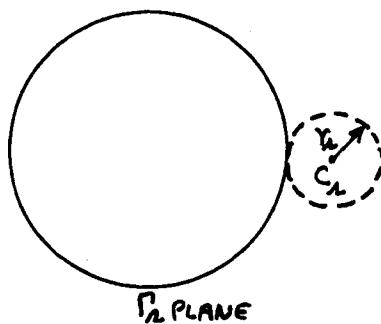(c) $K=1, \Delta=0.415$

$$\begin{cases} Y_n = 0.26 \\ C_n = 1.26 \end{cases}$$



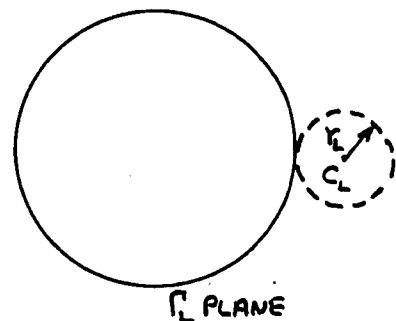
$$\begin{cases} Y_L = 0.26 \\ C_L = 1.26 \end{cases}$$




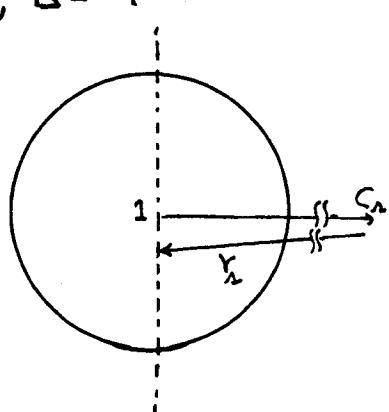(d) $K=0, \Delta=-1$

$$\begin{cases} Y_n = \infty \\ C_n = \infty \end{cases}$$


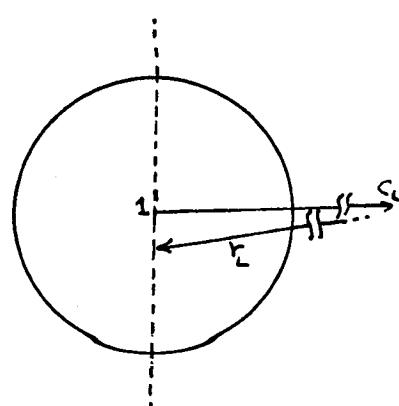
$$\begin{cases} Y_L = \infty \\ C_L = \infty \end{cases}$$



3.10) (a) FROM (3.3.7) AND (3.3.8) : $\lim_{S_{12} \rightarrow 0} \Delta = S_{11} S_{22}$. THEN,

$$\lim_{S_{12} \rightarrow 0} \gamma_L = 0$$



AND $\lim_{S_{12} \rightarrow 0} C_L = \frac{(S_{22} - S_{11} S_{21} S_{11})^*}{|S_{22}|^2 - |S_{11} S_{21}|^2} = \frac{S_{22}^* (1 - |S_{11}|^2)}{|S_{22}|^2 (1 - |S_{11}|^2)} = \frac{S_{22}^*}{|S_{22}|^2} = \frac{1}{|S_{22}|}$

SIMILARLY: $\lim_{S_{12} \rightarrow 0} \gamma_R = 0$ AND $\lim_{S_{12} \rightarrow 0} C_R = \frac{1}{|S_{11}|}$

(b)

$$\begin{cases} \gamma_L = 0 \\ C_L = \frac{1}{|S_{11}|} = 0.5 \angle -90^\circ \end{cases}$$

$$\begin{cases} \gamma_R = 0 \\ C_R = \frac{1}{|S_{22}|} = 10 \angle -45^\circ \end{cases}$$

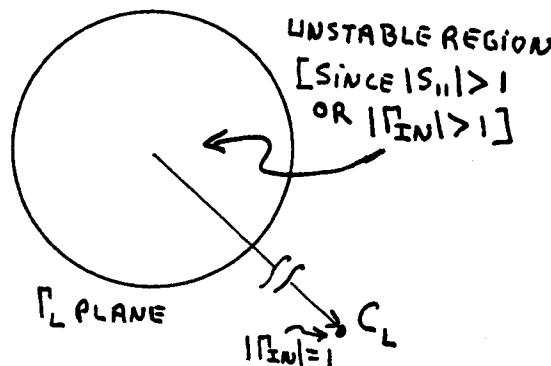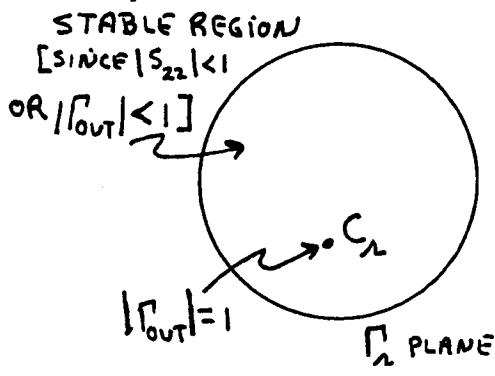

3.11) THE SOURCE STABILITY CIRCLE DOES NOT ENCLOSE THE CENTER OF THE SMITH CHART WHEN: $|C_R| > \gamma_R$. FROM (3.3.9) AND (3.3.10) WE OBTAIN: $|S_{11} - \Delta S_{22}^*| > |S_{12} S_{21}|$

FROM PROBLEM 3.20: $|S_{11} - \Delta S_{22}^*|^2 = |S_{12} S_{21}|^2 + (1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2)$

HENCE: $|S_{12} S_{21}|^2 + (1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2) > |S_{12} S_{21}|^2$

OR $(1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2) > 0 \quad (1)$

FROM (1): $\begin{cases} \text{If } |S_{22}| < 1 \text{ then } |\Delta| < |S_{11}| \\ \text{If } |S_{22}| > 1 \text{ then } |\Delta| > |S_{11}| \end{cases}$

SIMILARLY: $|C_L| > \gamma_L \Rightarrow |S_{22} - \Delta S_{11}^*| > |S_{12} S_{21}| \text{ OR}$
 $(1 - |S_{11}|^2)(|S_{22}|^2 - |\Delta|^2) > 0 \quad (2)$

FROM (2): $\begin{cases} \text{If } |S_{11}| < 1 \text{ then } |\Delta| < |S_{22}| \\ \text{If } |S_{11}| > 1 \text{ then } |\Delta| > |S_{22}| \end{cases}$

3.12) THE ANSWER TO THIS PROBLEM FOLLOWS FROM THE RESULTS IN APPENDIX J. THAT IS, WITH $C_{ii}=0$ AND $\gamma_{ii}=1$ WE OBTAIN:

$$C_{\text{OUT}} = \frac{S_{22} - \Delta S_{11}^*}{1 - |S_{11}|^2} \quad \text{AND} \quad \gamma_{\text{OUT}} = \frac{|S_{12} S_{21}|}{1 - |S_{11}|^2}$$

ALSO, WITH $C_{00}=0$ AND $\gamma_{00}=1$ WE OBTAIN:

$$C_{\text{IN}} = \frac{S_{11} - \Delta S_{22}^*}{1 - |S_{22}|^2} \quad \text{AND} \quad \gamma_{\text{IN}} = \frac{|S_{12} S_{21}|}{1 - |S_{22}|^2}$$

3.13) (a) $\Delta = S_{11} S_{22} - S_{12} S_{21}$ AND $|S_{11} S_{22}| = |\Delta + S_{12} S_{21}|$

$$\therefore |\Delta| = |S_{11} S_{22} - S_{12} S_{21}| \quad \text{AND} \quad |S_{11} S_{22}| = |\Delta + S_{12} S_{21}|$$

HENCE: $|\Delta| \leq |S_{11} S_{22}| + |S_{12} S_{21}| \quad (1) \quad |S_{11} S_{22}| \leq |\Delta| + |S_{12} S_{21}| \quad (2)$

FROM (3.3.13): $k > 1$ OR $1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2 > 2|S_{12} S_{21}| \quad (3)$

(1) INTO (3): $1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2 > 2|\Delta| - 2|S_{11} S_{22}| \quad (4)$

(2) INTO (3): $1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2 > 2|S_{11} S_{22}| - 2|\Delta| \quad (5)$

FROM (4): $(1 - |\Delta|)^2 > (|S_{11}| - |S_{22}|)^2 \quad (6)$

FROM (5): $(1 + |\Delta|)^2 > (|S_{11}| + |S_{22}|)^2 \quad (7)$

FROM (6) AND (7): $(1 - |\Delta|)^2 (1 + |\Delta|)^2 > (|S_{11}| - |S_{22}|)^2 (|S_{11}| + |S_{22}|)^2$
 $(1 - |\Delta|^2)^2 > (|S_{11}|^2 - |S_{22}|^2)^2 \quad (8)$

SINCE: $B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2$ AND $B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$

THEN: $B_1 B_2 = (1 - |\Delta|^2)^2 - (|S_{11}|^2 - |S_{22}|^2)^2 \quad (9), \quad B_1 + B_2 = 2(1 - |\Delta|^2) \quad (10)$

FROM (8) AND (9) WE HAVE: $B_1 B_2 > 0 \quad (11)$

(b) THE RELATION $B_1 B_2 > 0$ SHOWS THAT IF $B_1 > 0$ THEN $B_2 > 0$.

THEREFORE, THE CONDITIONS $k > 1$ AND $B_1 > 0$ ARE SIMILAR TO $k > 1$ AND $B_2 > 0$.

(c) If $B_1 > 0$ THEN $B_2 > 0$. HENCE, FROM (10):

$$2(1 - |\Delta|^2) > 0$$

OR $|\Delta| < 1$

3.14) FOR THIS TRANSISTOR: $K = 0.532$, $\Delta = 0.617 \angle -85.4^\circ$

$$r_n = 1.96$$


$$C_n = 2.64 \angle 116.7^\circ$$

$$r_L = 0.576$$

$$C_L = 1.4 \angle 41.5^\circ$$


AT POINT A: $r = 0.25$

$$\therefore R = 0.25(50) = 12.5\Omega$$

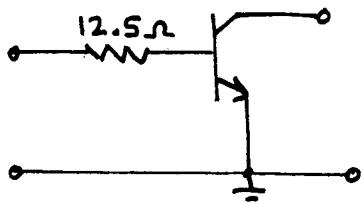


AT POINT B: $g = 1$
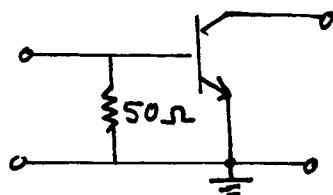
$$\therefore G = \frac{1}{50} = 20\text{mS} (\text{OR } 50\Omega)$$




AT POINT C : $r = 1$

$$\therefore R = 1(50) = 50\Omega$$

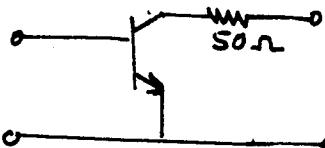

AT POINT D: $g = 0.12$
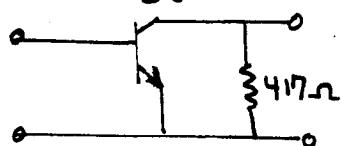
$$G = \frac{0.12}{50} = 2.4\text{mS} (\text{OR } 417\Omega)$$





FOR THIS CIRCUIT IT FOLLOWS
THAT: $S_{11} = 0.695 \angle 77.3^\circ$, $S_{12} = 0.03 \angle 42.5^\circ$,

$$S_{21} = 5.13 \angle 124.1^\circ \text{ AND } S_{22} = 0.665 \angle 25.8^\circ$$

HENCE, $K = 1.02$ AND $\Delta = 0.488 \angle -84.7^\circ$

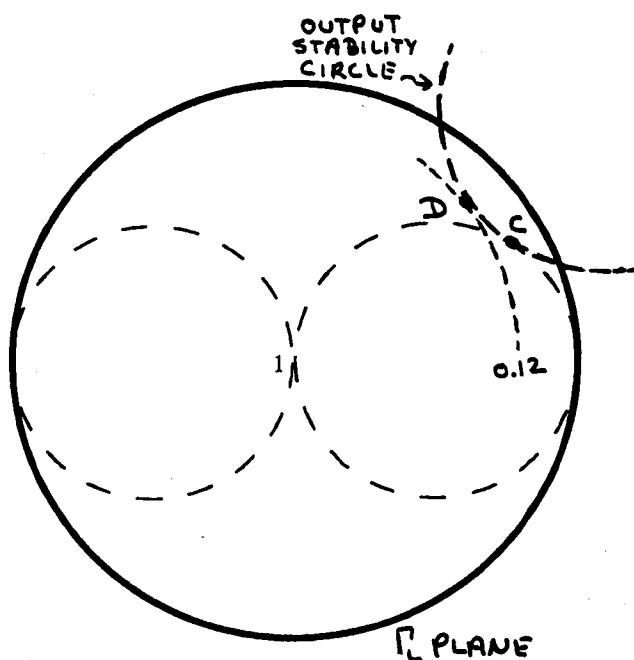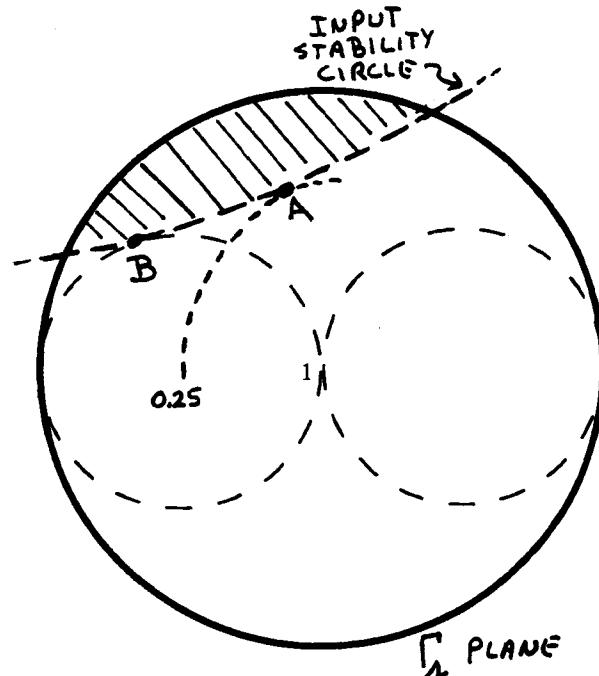AND THE CIRCUIT IS UNCONDITIONALLY
STABLE.



3.15) THE MAXIMUM VALUE OF $G_i = \frac{1 - |\Gamma_i|^2}{|1 - S_{ii}\Gamma_i|^2}$ IS OBTAINED AS FOLLOWS:

LET $\Gamma_i = x + jy$ AND $S_{ii} = a + jb$, THEN

$$G_i = \frac{1 - x^2 - y^2}{(1 - xa + yb)^2 + (xb + ya)^2} = \frac{1 - x^2 - y^2}{D}; D = (1 - xa + yb)^2 + (xb + ya)^2$$

$$\begin{cases} \frac{\partial G_i}{\partial x} = \frac{-2x}{D} - \frac{(1-x^2-y^2)[-2a(1-xa+yb)+2b(xb+ya)]}{D^2} = 0 \\ \frac{\partial G_i}{\partial y} = \frac{-2y}{D} - \frac{(1-x^2-y^2)[2b(1-xa+yb)+2a(xb+ya)]}{D^2} = 0 \end{cases}$$

OR $\begin{cases} 2xD = -(1-x^2-y^2)[-2a(1-xa+yb)+2b(xb+ya)] \quad (1) \\ 2yD = -(1-x^2-y^2)[2b(1-xa+yb)+2a(xb+ya)] \quad (2) \end{cases}$

DIVIDING (1) BY (2) GIVES:

$$\frac{x}{y} = \frac{-a(1-xa+yb)+b(xb+ya)}{b(1-xa+yb)+a(xb+ya)} = \frac{-a+x^2+y^2}{b+yb^2+ya^2}$$

OR $xb + yb^2 x + ya^2 x = -ay + x^2 y + xb^2 y \Rightarrow x = -\frac{ay}{b} \quad (3)$

(3) INTO (1): $-2\frac{ay}{b}(1 + \frac{a^2 y}{b} + yb)^2 = -(1 - \frac{a^2 y^2}{b} - y^2)(-2a(1 + \frac{a^2 y}{b} + yb))$

OR $-\frac{y}{b}(1 + \frac{a^2 y}{b} + yb) = 1 - \frac{a^2 y^2}{b} - y^2 \Rightarrow y = -b \quad (4)$

(4) INTO (3): $x = -\frac{a}{b}(-b)$ OR $x = a \quad (5)$

FROM (4) AND 5: $\Gamma_i = x + jy = a - jb$ OR $\Gamma_i = S_{ii}^*$.

3.16) (a) FOR $G_{TH,max}$: $\Gamma_L = S_{11}^* = 0.706 \angle 160^\circ$ AND


$$\Gamma_L = S_{22}^* = 0.508 \angle 20^\circ.$$


$$G_{TH,max} = \frac{1}{1 - |S_{11}|^2} = \frac{1}{1 - (0.706)^2} = 1.99 \text{ OR } 3 \text{ dB}$$

$$G_o = |S_{21}|^2 = (5.01)^2 = 25.1 \text{ OR } 14 \text{ dB}$$


$$G_{L,max} = \frac{1}{1 - |S_{22}|^2} = \frac{1}{1 - (0.508)^2} = 1.35 \text{ OR } 1.3 \text{ dB}$$
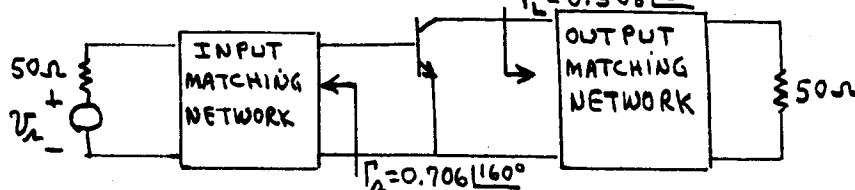
$$G_{TH,max} = 3 + 14 + 1.3 = 18.3 \text{ dB}$$




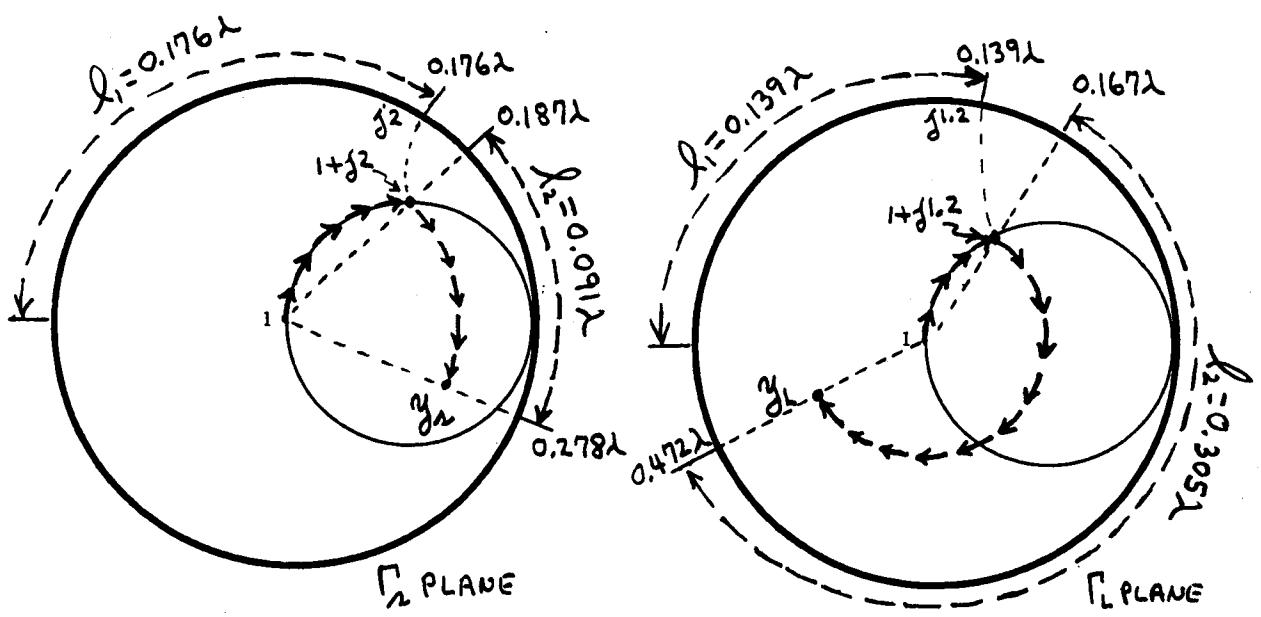

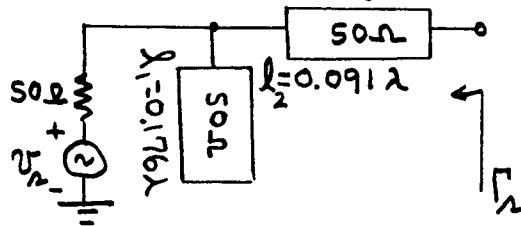
$$\Gamma_\lambda = 0.706 \angle 160^\circ, y_\lambda = \frac{1}{3} - 2.9 - j2.8$$


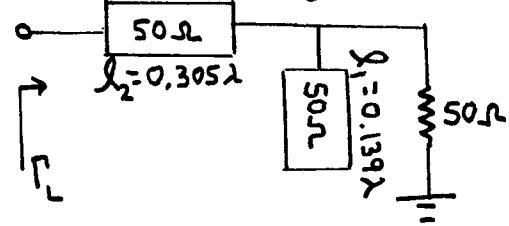
$$\Gamma_L = 0.508 \angle 20^\circ, y_L = \frac{1}{3} - 0.335 - j0.157$$



(b)

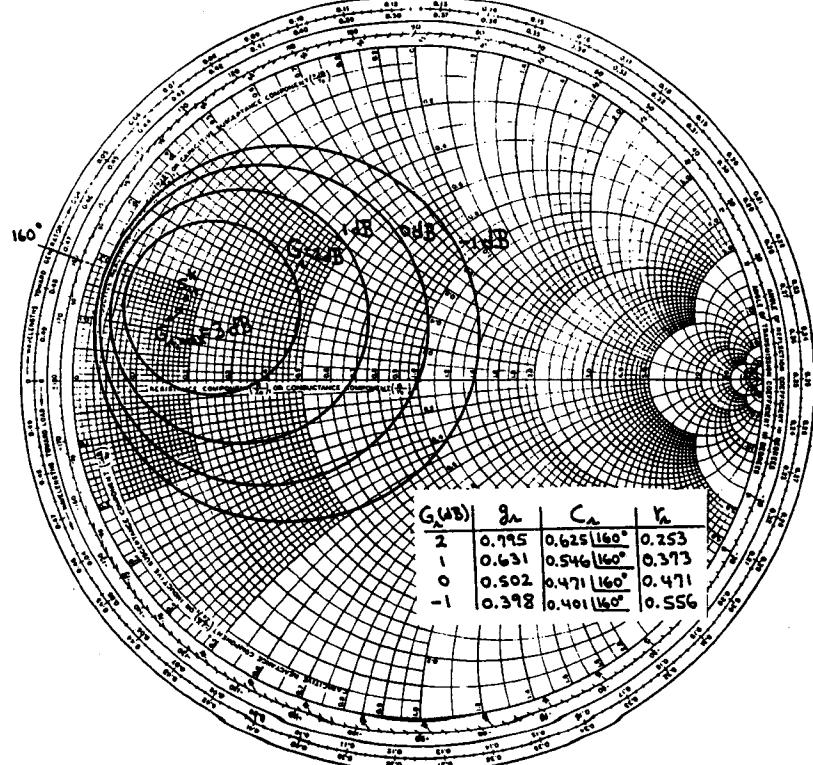

3.17) (a) THE INPUT RESISTANCE IS CALCULATED AS FOLLOWS:

$$\Gamma_{IN} = S_{11} = 2.3 \angle -135^\circ, Z_{IN} = 50(-0.45 - j0.34) = -22.48 - j17.04 \Omega.$$

Z_{IN} CAN ALSO BE CALCULATED USING THE SMITH CHART.


PLOT $\frac{1}{S_{11}} = 0.435 \angle -135^\circ$ AND READ $Z_{IN} = 50(-0.45 - j0.34) = -22.5 - j17 \Omega$

$$\text{FOR } G_L = 4 \text{ dB}, g_L = 2.512 [1 - (2.3)^2] = -10.78$$


$$\text{FROM (3.4.11) AND (3.4.12)}: G_L = 0.404 \angle 135^\circ \text{ AND } Y_L = 0.24$$

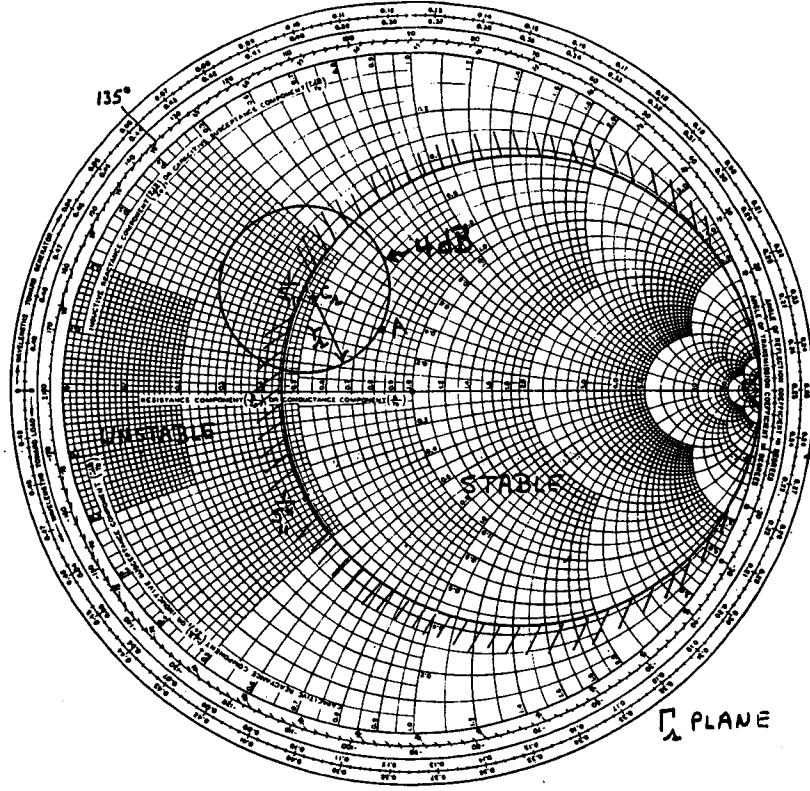(b) AT POINT A, Γ_L HAS
THE LARGEST REAL
PART ON THE $G_L = 4 \text{ dB}$
CIRCLE. THAT IS,
 $\Gamma_L = 0.2 \angle 115^\circ$

THE INPUT MATCHING
CIRCUIT MUST TRANSFORM
 50Ω TO $\Gamma_L = 0.2 \angle 115^\circ$.





(c) DESIGN FOR $\Gamma_L = 0.2 \angle 115^\circ$ AND $\Gamma_L = S_{22}^* = 0.8 \angle 66^\circ$. THEN,
 $G_L = 4 \text{ dB}, G_o = |S_{21}|^2 = 16$ (OR 12.04 dB), $G_{L,\max} = \frac{1}{1 - (0.8)^2} = 2.78$ (OR 4.4 dB)
 $\therefore G_{TW}(\text{dB}) = G_L + G_o + G_{L,\max} = 4 + 12.04 + 4.4 = 20.4 \text{ dB}$

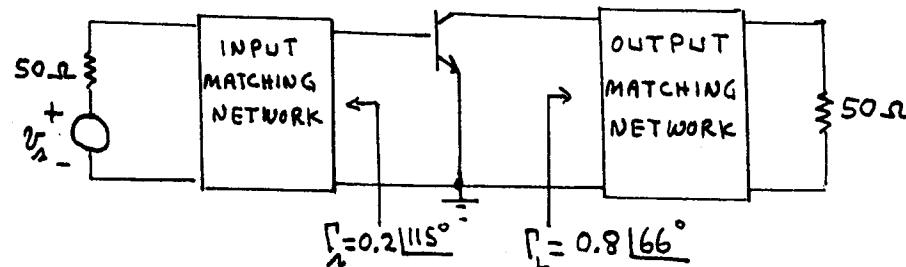

$$3.18)(a) G_{L_{max}} = \frac{1}{1-(0.5)^2} = 1.33 \text{ OR } 1.25 \text{ dB}, G_{L_{max}} = \frac{1}{1-(0.6)^2} = 1.563 \text{ OR } 1.94 \text{ dB}$$

$$G_o = |S_{21}|^2 = 25 \text{ OR } 13.98 \text{ dB}, \therefore G_{TU_{max}} = 1.25 + 13.98 + 1.94 = 17.2 \text{ dB}$$

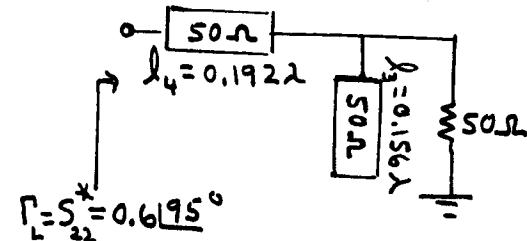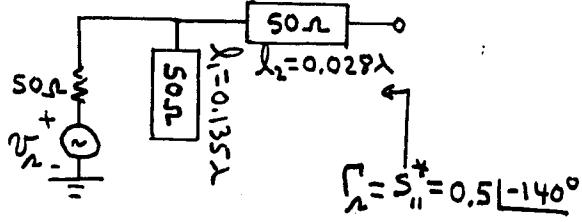(b) A MATCHING NETWORK DESIGN AT 900 MHz IS:



$$\text{AT } 900 \text{ MHz: } \lambda = \frac{310}{910^8} = 33.3 \text{ cm, } l_1 = 0.135\lambda = 4.496 \text{ cm,}$$

$$l_2 = 0.028\lambda = 0.932 \text{ cm, } l_3 = 0.156\lambda = 5.195 \text{ cm, } l_4 = 0.1922\lambda = 6.394 \text{ cm}$$

$$(c) g_L = \frac{G_L}{G_{L_{max}}} = \frac{1.259}{1.563} = 0.805$$

FROM (3.4.11) AND (3.4.12):

$$C_L = 0.519 \angle 95^\circ$$

$$Y_L = 0.304$$



(d) LET $\lambda' = \frac{c}{f'}$ WHERE $f' = 1 \text{ GHz}$,

AND $\lambda = \frac{c}{f}$ WHERE $f = 900 \text{ MHz}$.

$$\therefore \frac{\lambda}{\lambda'} = \frac{f'}{f} \text{ OR } \lambda = \frac{f}{f'} \lambda' = \frac{10^9}{910^8} \lambda' = 1.11\lambda'$$

$$l_1 = 0.135\lambda = 0.135(1.11\lambda') = 0.15\lambda', l_2 = 0.028(1.11\lambda') = 0.031\lambda',$$
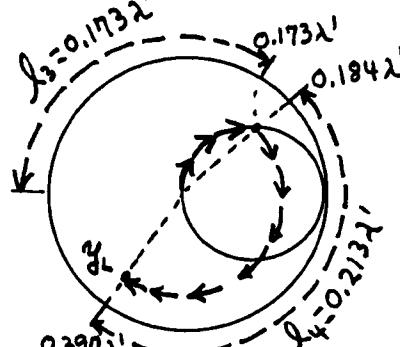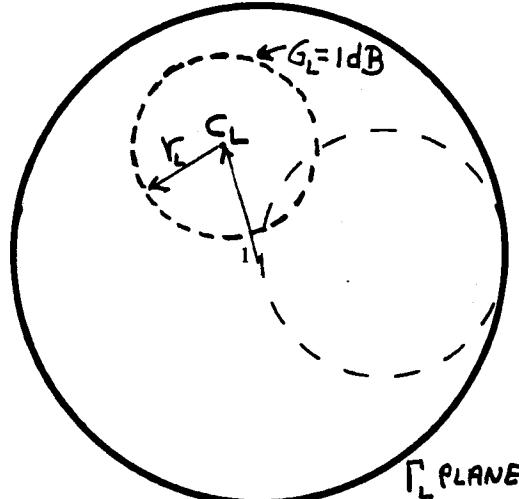
$$l_3 = 0.156(1.11\lambda') = 0.173\lambda', l_4 = 0.192(1.11\lambda') = 0.213\lambda'$$



$$\beta_\lambda = \frac{1}{y_\lambda}$$

$$y_\lambda = 1.79 + j1.58, \Gamma_\lambda = 0.55 \angle -146^\circ$$

$$\beta_L = \frac{1}{y_L}$$

$$y_L = 0.28 - j0.72, \Gamma_L = 0.693 \angle 74.4^\circ$$

$$\therefore G_{TU} = \frac{1 - (0.55)^2}{|1 - 0.48 \angle 137^\circ (0.55 \angle -146^\circ)|^2} \frac{(4.6)^2}{|1 - (0.693)^2|^2} \frac{1}{|1 - 0.57 \angle -99^\circ (0.693 \angle 74.4^\circ)|^2} = 31.97 \text{ OR } 15.05 \text{ dB}$$

$$3.19) (a) \Gamma_{ML}^* = S_{11} + \frac{S_{12}S_{21}\Gamma_{ML}}{1-S_{22}\Gamma_{ML}} = \frac{S_{11}-\Delta\Gamma_{ML}}{1-S_{22}\Gamma_{ML}} \quad (1)$$

$$\Gamma_{ML}^* = S_{22} + \frac{S_{12}S_{21}\Gamma_{ML}}{1-S_{11}\Gamma_{ML}} = \frac{S_{22}-\Delta\Gamma_{ML}}{1-S_{11}\Gamma_{ML}} \quad (2)$$

SOLVING (2) FOR Γ_{ML} GIVES: $\Gamma_{ML} = \frac{\Gamma_{ML}^* - S_{22}}{S_{11}\Gamma_{ML}^* - \Delta} \quad (3)$

EQUATING (1) AND (3): $\frac{S_{11}-\Delta\Gamma_{ML}}{1-S_{22}\Gamma_{ML}} = \frac{\Gamma_{ML}^* - S_{22}}{S_{11}\Gamma_{ML}^* - \Delta}$

$$|S_{11}|^2\Gamma_{ML} - S_{11}\Delta^* - \Delta S_{11}^*\Gamma_{ML}^2 + |\Delta|^2\Gamma_{ML} = \Gamma_{ML}^* - S_{22}^* - S_{22}\Gamma_{ML}^2 + |S_{22}|^2\Gamma_{ML}$$

$$\Gamma_{ML}^2(S_{22} - \Delta S_{11}^*) - \Gamma_{ML}(1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2) + S_{22}^* - S_{11}\Delta^* = 0$$

OR $\Gamma_{ML}^2 - \Gamma_{ML} \frac{B_2}{C_2} + \frac{C_2^*}{C_2} = 0$ WHERE $\begin{cases} B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \\ C_2 = S_{22} - \Delta S_{11}^* \end{cases}$

THE SOLUTIONS ARE:

$$\Gamma_{ML} = \frac{B_2 \pm \sqrt{(B_2)^2 - 4C_2^*}}{2C_2} = \frac{B_2 \pm \sqrt{B_2 - 4|C_2|^2}}{2C_2}$$

SIMILARLY, SOLVING (1) FOR Γ_{ML} AND EQUATING THE RESULT TO (2) GIVES: $\Gamma_{ML} = \frac{B_1 \pm \sqrt{B_1 - 4|C_1|^2}}{2C_1}$ WHERE $\begin{cases} B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \\ C_1 = S_{11} - \Delta S_{22}^* \end{cases}$

(b) FOR $S_{12} \rightarrow 0$ IT FOLLOWS FROM (3.6.3) AND (3.6.4) THAT

$$\Gamma_{ML} = (S_{11} + \frac{S_{12}S_{21}\Gamma_{ML}}{1-S_{22}\Gamma_{ML}})^* \approx S_{11}^*$$

AND

$$\Gamma_{ML} = (S_{22} + \frac{S_{12}S_{21}\Gamma_{ML}}{1-S_{11}\Gamma_{ML}})^* \approx S_{22}^*$$

$$3.20) (a) |C_1|^2 = |S_{11} - \Delta S_{22}^*|^2 = (S_{11} - \Delta S_{22}^*)(S_{11}^* - \Delta^* S_{22}) \\ = |S_{11}|^2 - S_{11}S_{22}^* \Delta^* - S_{11}^*S_{22}^* \Delta + |\Delta S_{22}|^2 \\ = |S_{11}|^2 - |S_{11}S_{22}|^2 + S_{11}S_{22}^*S_{22}^* - |S_{11}S_{22}|^2 + S_{11}^*S_{22}^*S_{11}S_{22} + |\Delta S_{22}|^2 \quad (1)$$

$$\text{SINCE } |\Delta|^2 = (S_{11}S_{22} - S_{12}S_{21})(S_{11}^*S_{22}^* - S_{12}^*S_{21}^*)$$

$$= |S_{11}S_{22}|^2 - S_{11}S_{22}S_{12}^*S_{21}^* - S_{11}^*S_{22}^*S_{12}S_{21} + |S_{12}S_{21}|^2$$

$$\text{THEN: } |S_{11}S_{22}|^2 - S_{11}S_{22}S_{12}^*S_{21}^* - S_{11}^*S_{22}^*S_{12}S_{21} = |\Delta|^2 - |S_{12}S_{21}|^2 \quad (2)$$

$$(2) \text{ INTO (1): } |C_1|^2 = |S_{11}|^2 - |\Delta|^2 + |S_{12}S_{21}|^2 - |S_{11}S_{22}|^2 + |\Delta|^2|S_{22}|^2 \\ = |S_{12}S_{21}|^2 + |S_{11}|^2(1 - |S_{22}|^2) - |\Delta|^2(1 - |S_{22}|^2) \\ = |S_{12}S_{21}|^2 + (1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2)$$

$$\text{SIMILARLY: } |C_2|^2 = |S_{12}S_{21}|^2 + (1 - |S_{11}|^2)(|S_{22}|^2 - |\Delta|^2)$$


3.21) $K = 1.03$ AND $\Delta = 0.324 \angle -64.8^\circ \therefore$ UNCONDITIONALLY STABLE

FROM (3.6.5) : $\Gamma_{M_A} = 0.73 \angle 135^\circ$


FROM (3.6.6) : $\Gamma_{M_L} = 0.95 \angle 33.8^\circ$

FROM (3.6.10) : $G_{T,\max} = 19.08 \text{ OR } 12.8 \text{ dB}$

A DESIGN USING LUMPED ELEMENTS IS :

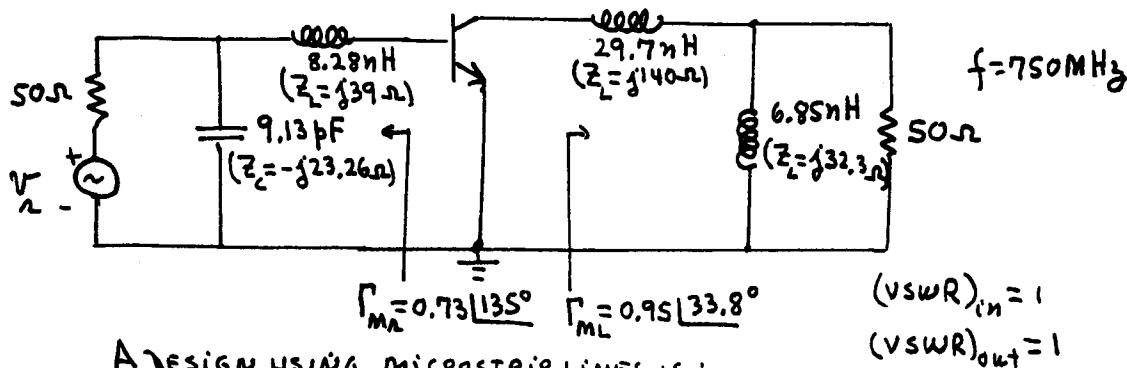

A DESIGN USING MICROSTRIP LINES IS :

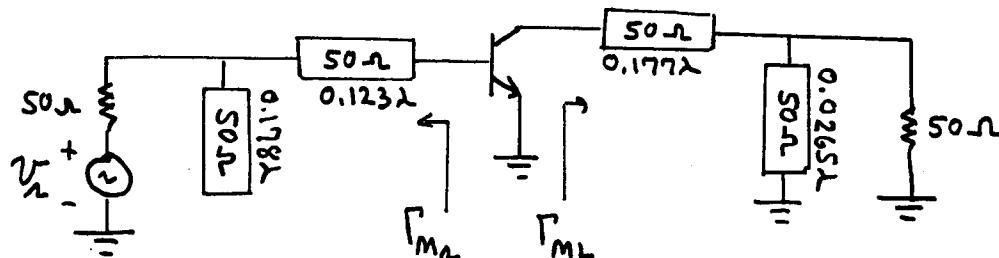

3.22) (a) THE ADMITTANCE OF THE 70Ω STUB IS : $y_{oc} = j$ OR $Y_{oc} = \frac{j}{70}$

THE ADMITTANCE OF THE TWO PARALLEL STUBS IS :

$$Y_{oc, \text{TOTAL}} = \frac{1}{70} + \frac{1}{70} = \frac{2}{70} = \frac{1}{35} = j'29 \text{ mS}$$

THE ADMITTANCE OF THE 50Ω LOAD PLUS $Y_{oc, \text{TOTAL}}$ IS (CALLED Y_x) :

$$Y_x = \frac{1}{50} + \frac{1}{35} = 20 + j'29 \text{ mS}$$

NORMALIZING Y_x WITH $Y_0 = \frac{1}{Z_0} = \frac{1}{40}$ ($y_x = 0.8 + j1.16$)

AND ROTATING IN THE SMITH CHART


A DISTANCE $l = 0.25\lambda$ GIVES

$$j_L = \frac{1}{y_L} = 0.8 + j1.16 \therefore \Gamma_L = \Gamma_{ML} = 0.55 \angle 67^\circ$$

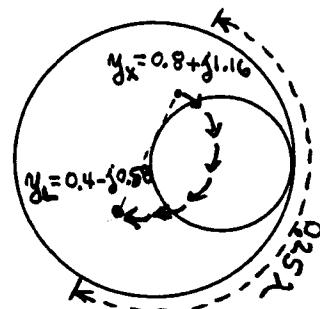(b) FROM FIG. 2.5.4 (WITH $\epsilon_r = 10$ AND $h = 30 \text{ mils}$):

$$W = 28.5 \text{ mils} \text{ AND } \epsilon_{eff} = 6.68, \lambda_0 = \frac{310^0}{210^0} = 15 \text{ cm.}$$

$$\therefore l_1 = 0.25\lambda = \frac{0.25\lambda_0}{\sqrt{\epsilon_{eff}}} = \frac{0.25(15)}{\sqrt{6.68}} = 1.45 \text{ cm.}$$



3.23) THE OUTPUT IS MATCHED WITH $\Gamma_{ML} = \Gamma_{out}^* = 0.718 \angle 103.9^\circ$.
 THEREFORE, $\Gamma_x = 0$ (OR $Z_x = 50\Omega$) AND $(VSWR)_{out} = 1$.


NOTE: THIS IS THE OUTPUT MATCHING NETWORK IN FIG. 3.6.4 (SEE FIG. 3.6.3b).
 IT IS SIMPLE TO VERIFY THAT $\Gamma_x = 0$ USING FIG. 3.6.3b. THAT IS,
 PLOT $y_{out} = y_{ML}^* = 0.414 + j1.19$ IN THE SMITH CHART AND FIND y_x ,
 WHICH WILL BE $y_x = 1$ ($Z_x = 50\Omega$ OR $\Gamma_x = 0$).

3.24) (a) SINCE $K = 1.19$ AND $\Delta = 0.399 \angle 126.5^\circ$ (i.e., $|\Delta| < 1$) THE
 BJT IS UNCONDITIONALLY STABLE AT 3.5 GHz. THEREFORE,
 IT CAN BE DESIGNED FOR A SIMULTANEOUS CONJUGATE MATCH.

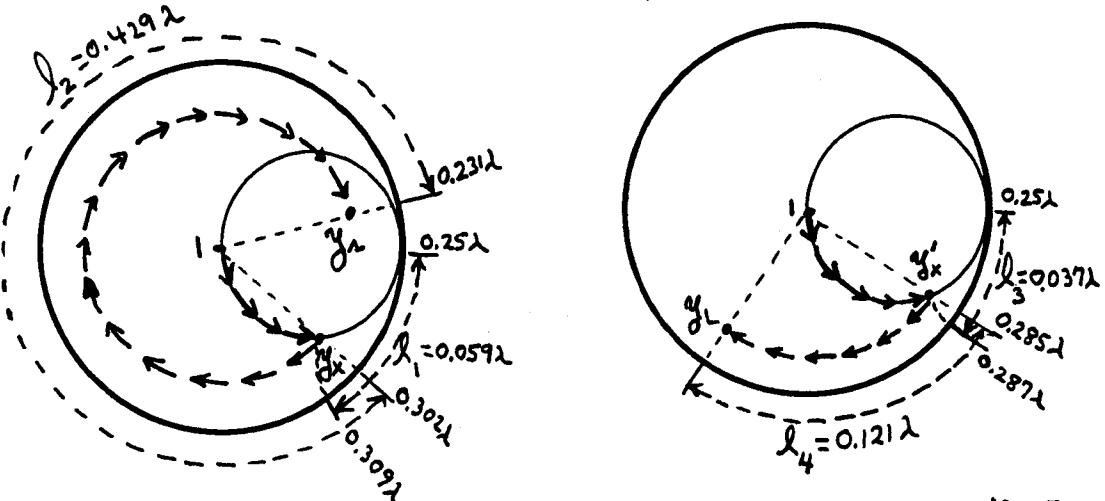
(b) FROM (3.6.5) AND (3.6.6): $\Gamma_{ML} = 0.798 \angle -166.9^\circ$, $\Gamma_{in} = 0.904 \angle 68^\circ$

FROM (3.6.10): $G_{T,max} = 23.06$ OR 13.63 dB.

A DESIGN FOR THE AMPLIFIER AT 3.5 GHz IS:


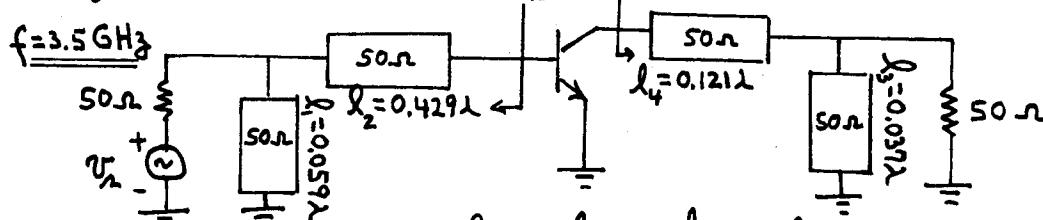
$$y_x = 1 - j2.6, y_s = 4.4 + j4.4 \quad \Gamma_{ML}, \Gamma_{in} \quad y'_x = 1 - j4.2, y_L = 0.073 - j0.67$$



f (GHz)	λ	l_1	l_2	l_3	l_4
$f_1 = 3$	$\lambda_1 = \frac{c}{f_1}$	$\lambda_2 = \frac{f_1}{f_2} \lambda_1 = 0.857 \lambda_1$	$0.051 \lambda_1$	$0.368 \lambda_1$	$0.032 \lambda_1$
$f_2 = 3.5$	$\lambda_2 = \frac{c}{f_2}$	λ_2	$0.059 \lambda_2$	$0.429 \lambda_2$	$0.037 \lambda_2$
$f_3 = 4$	$\lambda_3 = \frac{c}{f_3}$	$\lambda_2 = \frac{f_3}{f_2} \lambda_2 = 1.143 \lambda_3$	$0.067 \lambda_3$	$0.49 \lambda_3$	$0.042 \lambda_3$

USING THE SMITH CHART IT IS SIMPLE TO FIND THE VALUES OF Γ_a AND Γ_L AT f_1 AND f_3 . THE VALUES OF G_T ARE CALCULATED USING (3.2.1). THE RESULTS ARE:

f (GHz)	Γ_a	Γ_L	G_T
3	$0.833 \angle -118.5^\circ$	$0.934 \angle 82.2^\circ$	0.944 OR -0.25 dB
3.5	$0.798 \angle -166.9^\circ$	$0.904 \angle 68^\circ$	23.06 OR 13.63 dB
4	$0.749 \angle 145.6^\circ$	$0.878 \angle 51.5^\circ$	2.257 OR 3.54 dB

3.25(a) THE TRANSISTOR IS UNCONDITIONALLY STABLE ($K=1.033$, $\Delta=0.324 \angle -64.8^\circ$)

WITH $g_p = \frac{G_p}{|S_{21}|^2} = \frac{10}{(1.92)^2} = 2.713$, WE OBTAIN FROM (3.7.4) AND (3.7.5):

$$C_p = 0.781 \angle 33.85^\circ \text{ AND } Y_p = 0.214$$

THE $G_p=10 \text{ dB}$ GRIN CIRCLE IS DRAWN IN THE SMITH CHART. SELECTING Γ_L AT POINT "A": $\Gamma_L = 0.567 \angle 33.85^\circ$, GIVES

$$\Gamma_a = \Gamma_{in}^* = 0.276 \angle 93.33^\circ$$

AND $\Gamma_{out} = 0.86 \angle -33.85^\circ$


FROM (2.8.3): $|\Gamma_a|=0$ (since $\Gamma_a = \Gamma_{in}^*$)

$$\text{HENCE: } (\text{VSWR})_{in} = 1$$

FROM (2.8.6): $|\Gamma_b|=0.572$

$$\text{HENCE: } (\text{VSWR})_{out} = \frac{1+0.572}{1-0.572} = 3.67$$

A DESIGN IS:

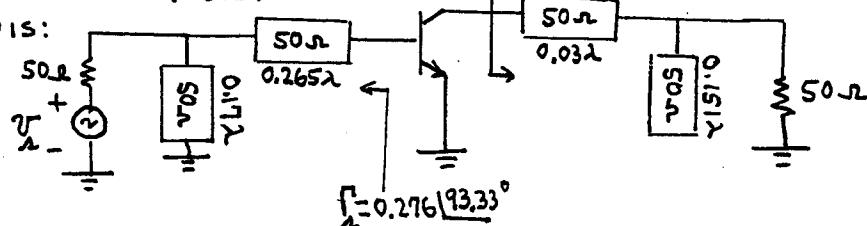


(b) $G_{p,max} = G_{T,max} = 19.08 \text{ OR } 12.8 \text{ dB}$

THE $G_{p,max}$ GRIN CIRCLE (i.e., a point) occurs AT:

$$g_{p,max} = \frac{G_{p,max}}{|S_{21}|^2} = \frac{19.08}{(1.92)^2} = 5.176, C_{p,max} = 0.95 \angle 33.8^\circ, Y_{p,max} = 0.$$

OBSERVE (SEE PROBLEM 3.21) THAT: $\Gamma_{ML} = C_{p,max} = 0.95 \angle 33.8^\circ$

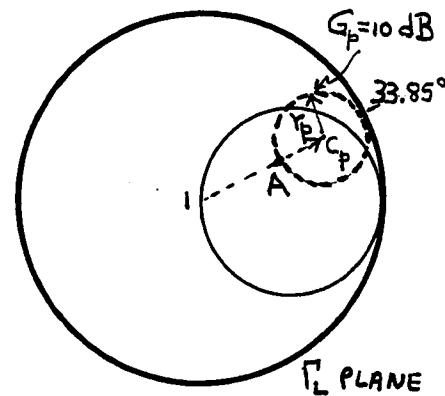AND $\Gamma_a = \Gamma_{in}^* = 0.73 \angle 135^\circ$ IS IDENTICAL TO Γ_{ML} .



3.26) FOR THIS TRANSISTOR: $K = 1.053$ AND $\Delta = 0.576 \angle -85.4^\circ$.
THEREFORE, IT IS UNCONDITIONALLY STABLE.


$$G_{p,\max} = G_{T,\max} = 77.12 \text{ OR } 18.87 \text{ dB}$$

$$G_p = 10 \text{ dB CIRCLE: } g_p = 0.977, C_p = 0.306 \angle 39.45^\circ, r_p = 0.693$$

THE $G_p = 10 \text{ dB}$ CONSTANT-GAIN CIRCLE
IS SHOWN IN THE SMITH CHART. THE Γ_L
SELECTED IS SHOWN AS "A": $\Gamma_L = 0.85 \angle 89^\circ$.
THEN: $\Gamma_L = \Gamma_{IN}^* = 0.793 \angle 64.2^\circ, \Gamma_{OUT} = 0.798 \angle -42.3^\circ$

$$|\Gamma_a| = 0, (\text{VSWR})_{in} = 1$$

$$|\Gamma_b| = 0.9, (\text{VSWR})_{out} = 18.9$$

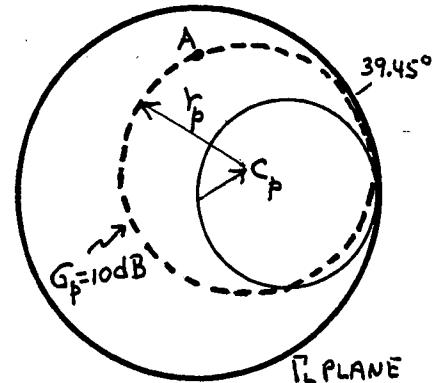

3.27) (a) $K = 0.53, \Delta = 0.524 \angle -142.9^\circ$; IT IS POTENTIALLY UNSTABLE.

OUTPUT STABILITY CIRCLE [(3.3.7) AND (3.3.8)]:

$$C_L = 1.47 \angle 76.6^\circ \text{ AND } Y_L = 0.668$$

$G_p = 10 \text{ dB}$ CONSTANT-GAIN CIRCLE [(3.7.4) AND (3.7.5)]: $g_p = \frac{10}{(2.43)^2} = 1.694,$
 $C_p = 0.41 \angle 76.6^\circ \text{ AND } r_p = 0.641$

(b) THE $G_p = 10 \text{ dB}$ GAIN CIRCLE IS DRAWN ON THE SMITH CHART. THREE
VALUES OF Γ_L ARE DENOTED BY "a", "b", AND "c". THEN,

Γ_L	$\Gamma_a = \Gamma_{IN}^*$	Γ_{out}	$ \Gamma_b $	$(\text{VSWR})_{in}$	$(\text{VSWR})_{out}$
"a" $0.59 \angle 0^\circ$	$0.687 \angle 106.11^\circ$	$0.84 \angle 70.73^\circ$	0.889	1	17
"b" $0.24 \angle -90^\circ$	$0.757 \angle 100.35^\circ$	$0.83 \angle -76.22^\circ$	0.891	1	17.3
"c" $0.67 \angle 45^\circ$	$0.851 \angle 97.7^\circ$	$0.84 \angle -83.74^\circ$	0.889	1	17


THE 3 VALUES OF Γ_L ARE IN THE STABLE REGION, SINCE $C_L = 1.3 \angle 115.7^\circ$ AND $r_L = 0.46$.

(c) FOR $G_p = 15 \text{ dB}$: $g_p = \frac{10^{1.5}}{(2.43)^2} = 5.355, C_p = 0.81 \angle 76.6^\circ, r_p = 0.402$

FOR $G_p = 20 \text{ dB}$: $g_p = \frac{10^2}{(2.43)^2} = 16.94, C_p = 1.17 \angle 76.6^\circ, r_p = 0.457$

FOR $G_p = 40 \text{ dB}$: $g_p = \frac{10^4}{(2.43)^2} = 1.694, C_p = 1.46 \angle 76.6^\circ, r_p = 0.665$

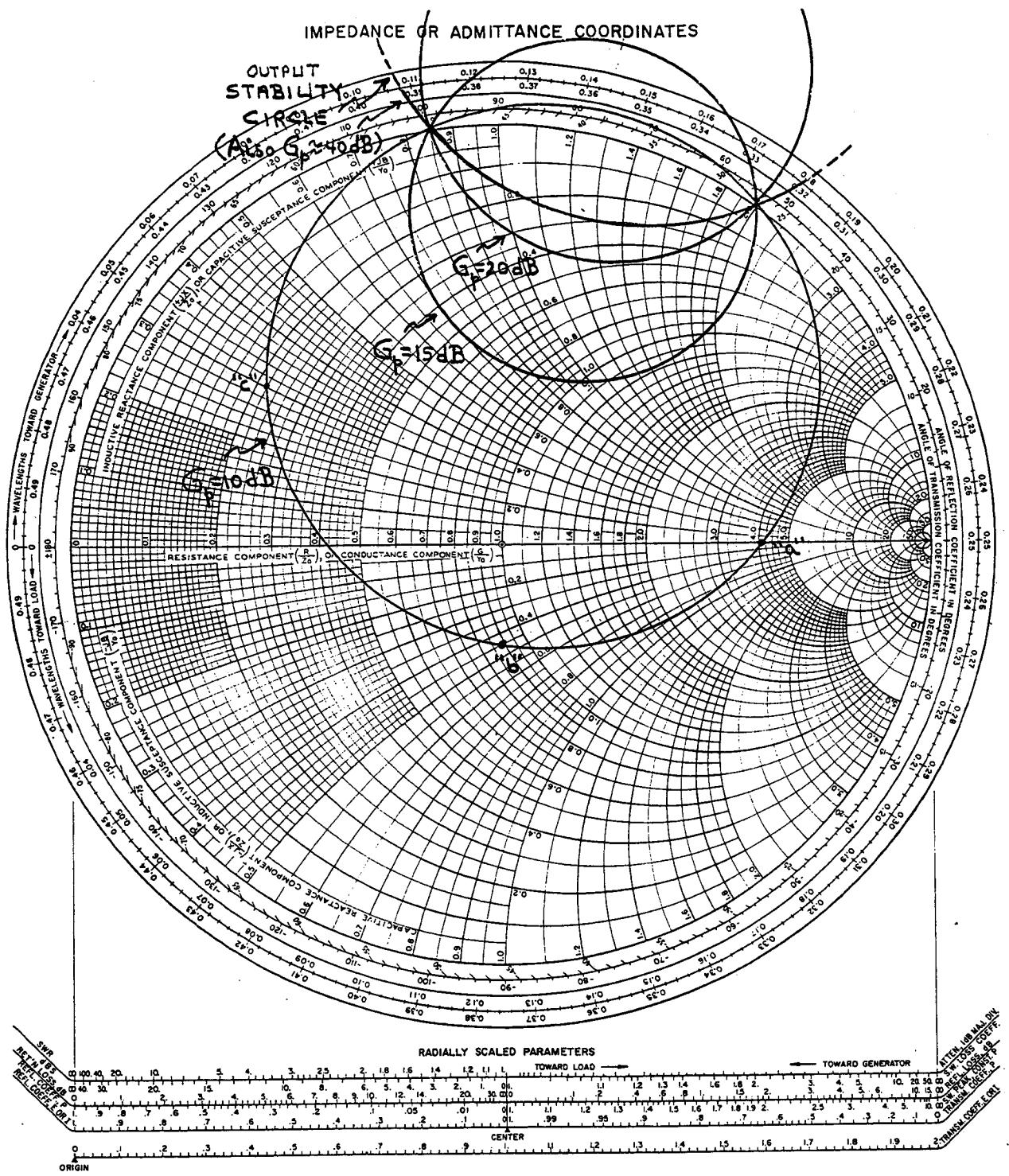THE $G_p = 15 \text{ dB}, 20 \text{ dB}$, AND 40 dB GAIN CIRCLES ARE ALSO DRAWN
ON THE SMITH CHART. THE $G_p = 40 \text{ dB}$ CIRCLE ALMOST COINCIDES WITH
THE OUTPUT STABILITY CIRCLE.



3.28) OUTPUT STABILITY CIRCLE: $|\Gamma_L - C_L|^2 = Y_L^2$

$$\text{OR} \quad |\Gamma_L|^2 - \Gamma_L C_L^* - \Gamma_L^* C_L + |C_L|^2 = Y_L^2 \quad (1)$$

(1) INTERSECTS THE SMITH CHART WHEN $|\Gamma_L| = 1$; THEN

$$1 - \Gamma_L C_L^* - \Gamma_L^* C_L + |C_L|^2 = Y_L^2$$

LET $\Gamma_L = U_L + jV_L$ AND $C_L = \operatorname{Re}[C_L] + j\operatorname{Im}[C_L]$:

$$-(U_L + jV_L)(\operatorname{Re}[C_L] - j\operatorname{Im}[C_L]) - (U_L - jV_L)(\operatorname{Re}[C_L] + j\operatorname{Im}[C_L]) = Y_L^2 - |C_L|^2 - 1$$

$$2U_L \operatorname{Re}[C_L] + 2V_L \operatorname{Im}[C_L] = 1 + |C_L|^2 - Y_L^2$$

OR

$$V_L = -\frac{\operatorname{Re}[C_L]}{\operatorname{Im}[C_L]} U_L + \frac{1 + |C_L|^2 - Y_L^2}{2 \operatorname{Im}[C_L]} \quad (2)$$

(2) IS THE EQUATION OF A STRAIGHT LINE WITH SLOPE $m_L = -\frac{\operatorname{Re}[C_L]}{\operatorname{Im}[C_L]}$ AND
INTERCEPT $b_L = \frac{1 + |C_L|^2 - Y_L^2}{2 \operatorname{Im}[C_L]}$. THIS LINE INTERSECTS THE SMITH CHART
(T.E., $|\Gamma_L| = 1$) AT TWO POINTS.

SIMILARLY, THE POWER GAIN CIRCLE INTERSECTS $|\Gamma_L| = 1$
AT TWO POINTS DETERMINED BY: (LET $C_p = \operatorname{Re}[C_p] + j\operatorname{Im}[C_p]$)

$$V_L = -\frac{\operatorname{Re}[C_p]}{\operatorname{Im}[C_p]} U_L + \frac{1 + |C_p|^2 - Y_p^2}{2 \operatorname{Im}[C_p]} = -m_p U_L + b_p$$

THE POINTS OF INTERSECTION DETERMINED BY (2) AND (3) ARE
EQUAL IF $m_L = m_p$ AND $b_L = b_p$.

$$m_L = -\frac{\operatorname{Re}[C_L]}{\operatorname{Im}[C_L]} = -\frac{\operatorname{Re}[S_{22}^* - \Delta^* S_{11}]}{\operatorname{Im}[S_{22}^* - \Delta^* S_{11}]}$$

$$m_p = -\frac{\operatorname{Re}[C_p]}{\operatorname{Im}[C_p]} = -\frac{\operatorname{Re}[C_2^*]}{\operatorname{Im}[C_2^*]} = -\frac{\operatorname{Re}[S_{22}^* - \Delta^* S_{11}]}{\operatorname{Im}[S_{22}^* - \Delta^* S_{11}]}$$


$$\therefore m_L = m_p$$

IT ALSO FOLLOWS THAT $b_L = b_p$.

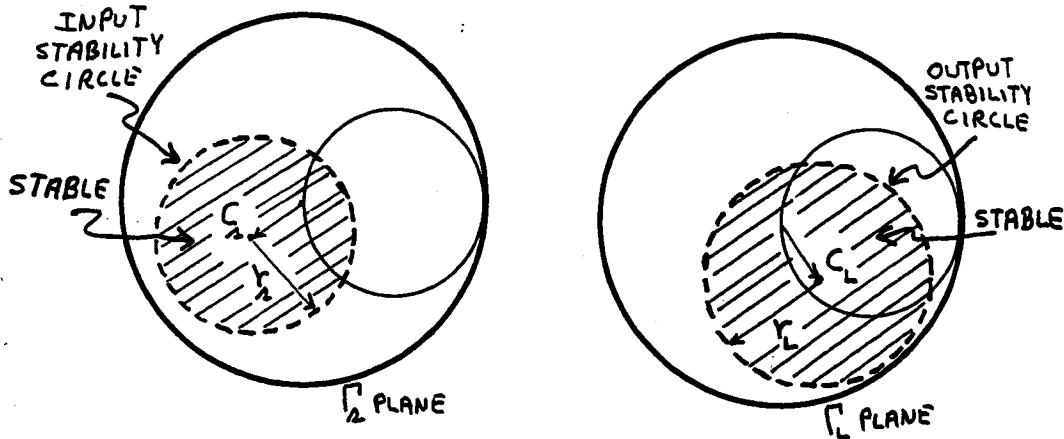3.29) (a) $K = 1.032$, $\Delta = 1.65 \angle 78.1^\circ$ \therefore POTENTIALLY UNSTABLE

FROM (3.3.7) TO (3.3.10):

$$\text{INPUT STAB. CIRCLE} \left\{ \begin{array}{l} C_a = 0.285 \angle -161.1^\circ \\ r_a = 0.65 \end{array} \right. \quad \text{OUTPUT STAB. CIRCLE} \left\{ \begin{array}{l} C_L = 0.315 \angle -61.5^\circ \\ r_L = 0.627 \end{array} \right.$$



(b) FROM (3.2.3) WITH $\Gamma_L = 0$: (AND $\Gamma_{IN} = S_{11}$ WHEN $\Gamma_L = 0$)

$$G_p = \frac{|S_{21}|^2}{1 - |S_{11}|^2} = \frac{4^2}{1 - (0.5)^2} = 21.33 \text{ OR } 13.3 \text{ dB}$$

(c) G_p CAN BE INFINITE, BECAUSE IT IS POTENTIALLY UNSTABLE.
As Γ_L APPROACHES THE STABILITY CIRCLE, $G_p \rightarrow \infty$.

3.30) FROM EXAMPLE 3.8.1: $G_{A,\max} = 9.66 \text{ dB}$, $G_A = 9.66 - 2 = 7.66 \text{ dB}$.

FROM (3.7.15) AND (3.7.16), FOR THE $G_A = 7.66 \text{ dB}$ GAIN CIRCLE:

$$g_a = \frac{10^{0.766}}{(2.3)^2} = 1.103, \quad C_a = 0.503 \angle -40.45^\circ, \quad r_a = 0.436$$

THE VALUES OF Γ_L ON THE 7.6 dB CIRCLE ARE GIVEN BY:

$$\Gamma_L = C_a + r_a e^{j\theta_1} = 0.503 \angle -40.45^\circ + 0.436 e^{j\theta_1}$$

LETTING $\theta_1 = 0, \frac{\pi}{2}, \pi, \text{ AND } \frac{3\pi}{2}$ WE OBTAIN THE VALUES OF Γ_L SHOWN IN THE TABLE. THE ASSOCIATED VALUES OF Γ_{OUT} ARE ALSO SHOWN.

FOR $(VSWR)_{out} = 1.5$ (OR $|\Gamma_b| = 0.2$), USING (3.8.7) AND (3.8.8), THE CENTER AND RADIUS OF THE $(VSWR)_{out} = 1.5$ CIRCLE ARE CALCULATED.


THE VALUES OF Γ_L ON THE $(VSWR)_{out} = 1.5$ CIRCLE ARE GIVEN BY:

$$\Gamma_L = C_{V_o} + r_{V_o} e^{j\theta_2}. \text{ LETTING } \theta_2 = 0, \frac{\pi}{2}, \pi, \text{ AND } \frac{3\pi}{2}, \text{ FOUR VALUES OF } \Gamma_L \text{ ON THE } (VSWR)_{out} = 1.5 \text{ CIRCLE ARE CALCULATED, AS SHOWN IN THE TABLE.}$$

THE ASSOCIATED VALUES OF Γ_{IN} , $|\Gamma_a|$, AND $(VSWR)_{in}$ ARE ALSO SHOWN.

Γ_L	Γ_{OUT}	$(VSWR)_{\text{out}} = 1.5$ CIRCLE	Γ_L	Γ_{IN}	$ I_a $	$(VSWR)_{\text{in}}$
$(\theta_1=0^\circ)$ $0.881 \angle -21.73^\circ$	$0.451 \angle 176.74^\circ$	$C_V = 0.437 \angle -176.74^\circ$ $R_V = 0.161$	$0.276 \angle -174.8^\circ (\theta_2=0)$ $0.457 \angle 162.7^\circ (\theta_2=\frac{\pi}{2})$ $0.598 \angle -177.6^\circ (\theta_2=\pi)$ $0.474 \angle -156.9^\circ (\theta_2=\frac{3\pi}{2})$	$0.683 \angle 33.8^\circ$ $0.712 \angle 28.8^\circ$ $0.771 \angle 30.9^\circ$ $0.748 \angle 35.7^\circ$	0.596 0.507 0.495 0.604	3.95 3.05 2.96 4.05
$(\theta_1=\pi/2)$ $0.398 \angle 15.99^\circ$	$0.005 \angle 95.36^\circ$	$C_V = 0.005 \angle -95.36^\circ$ $R_V = 0.2$	$0.2 \angle -1.4^\circ (\theta_2=0)$ $0.195 \angle 90.1^\circ (\theta_2=\frac{\pi}{2})$ $0.2 \angle -178.6^\circ (\theta_2=\pi)$ $0.2 \angle -90.1^\circ (\theta_2=\frac{3\pi}{2})$	$0.539 \angle 38.5^\circ$ $0.582 \angle 30.3^\circ$ $0.659 \angle 34^\circ$ $0.628 \angle 41.5^\circ$	0.501 0.491 0.591 0.598	3.00 2.93 3.89 3.98
$(\theta_1=\pi)$ $0.331 \angle -99.26^\circ$	$0.249 \angle 62.12^\circ$	$C_V = 0.241 \angle -62.12^\circ$ $R_V = 0.188$	$0.368 \angle -35.2^\circ (\theta_2=0)$ $0.115 \angle -12.1^\circ (\theta_2=\frac{\pi}{2})$ $0.225 \angle -109.6^\circ (\theta_2=\pi)$ $0.416 \angle -74.3^\circ (\theta_2=\frac{3\pi}{2})$	$0.539 \angle 47^\circ$ $0.569 \angle 38^\circ$ $0.652 \angle 40.8^\circ$ $0.633 \angle 48.8^\circ$	0.473 0.543 0.613 0.56	2.79 3.38 4.17 3.54
$(\theta_1=3\pi/2)$ $0.853 \angle -63.34^\circ$	$0.547 \angle 94.15^\circ$	$C_V = 0.531 \angle -94.15^\circ$ $R_V = 0.142$	$0.54 \angle -78.9^\circ (\theta_2=0)$ $0.39 \angle -95.6^\circ (\theta_2=\frac{\pi}{2})$ $0.559 \angle -108.8^\circ (\theta_2=\pi)$ $0.673 \angle -93.3^\circ (\theta_2=\frac{3\pi}{2})$	$0.666 \angle 51.8^\circ$ $0.673 \angle 45.7^\circ$ $0.742 \angle 46.3^\circ$ $0.741 \angle 51.9^\circ$	0.526 0.606 0.597 0.485	3.22 4.07 3.97 2.88

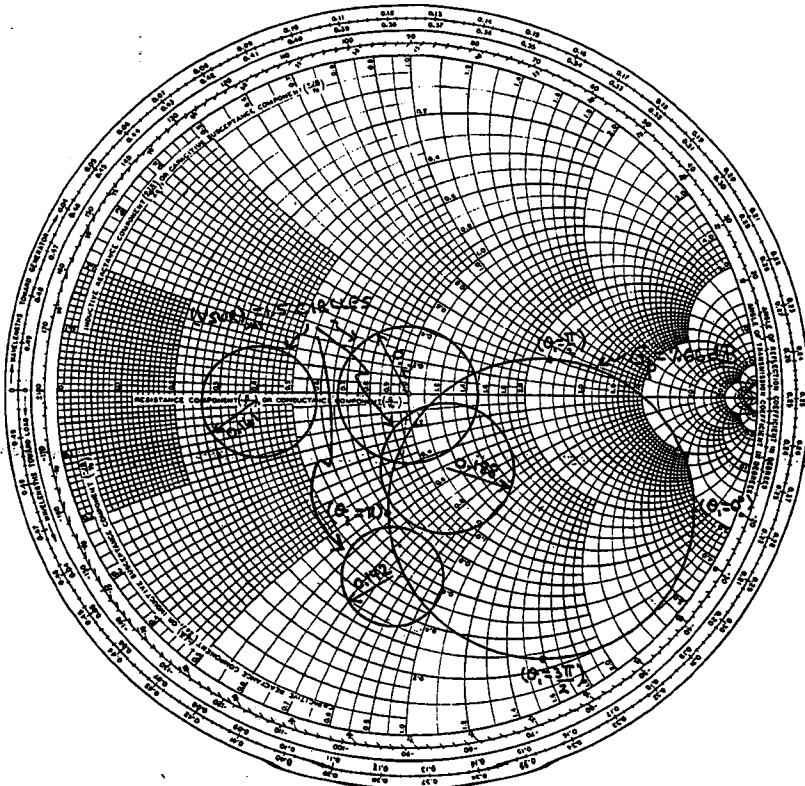FROM THESE CALCULATIONS IT IS SEEN THAT A DESIGN WITH
 $\Gamma_L = 0.331 \angle -99.26^\circ$ AND $\Gamma_L = 0.368 \angle -35.2^\circ$ RESULTS IN $(VSWR)_{\text{in}} = 2.79$ AND $(VSWR)_{\text{out}} = 1.5$.



3.31) (a) $K = 1.344$, $\Delta = 2.156 \angle -16.6^\circ \therefore$ POTENTIALLY UNSTABLE

(b) OUTPUT STABILITY CIRCLE: $C_L = 0.261 \angle -36.3^\circ$, $r_L = 0.409$


(c) FROM (3.6.6) (USING THE + SIGN): $\Gamma_{ML} = 0.319 \angle -36.3^\circ$

(d) $G_{p,\min} = G_{T,\min} = 44.82$ OR 16.51 dB

(e)

G_p	CENTER AND RADIUS
18 dB	$\{C_p = 0.31 \angle -36.3^\circ$ $r_p = 0.234$
21 dB	$\{C_p = 0.28 \angle -36.3^\circ$ $r_p = 0.34$
26 dB	$\{C_p = 0.266 \angle -36.3^\circ$ $r_p = 0.39$
36 dB	$\{C_p = 0.261 \angle -36.3^\circ$ $r_p = 0.409$

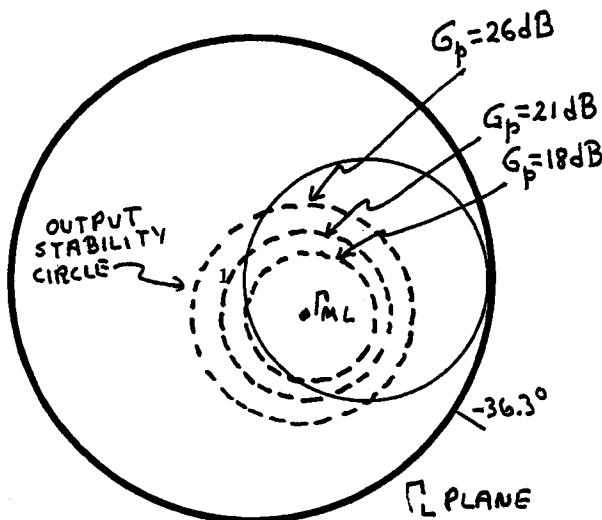THE 26 dB GAIN CIRCLE, THE
36 dB GAIN CIRCLE, AND THE
OUTPUT STABILITY CIRCLE
ALMOST COINCIDE.



(f) INPUT STABILITY CIRCLE: $C_{in} = 0.102 \angle 107.4^\circ$, $r_{in} = 0.44$

FROM (3.6.5) (USING THE + SIGN): $\Gamma_{ML} = 0.127 \angle 107.4^\circ$

(g) $(VSWR)_{in} = (VSWR)_{out} = 1$.

3.32) (a) $K = 1.17$, $\Delta = 0.368 \angle 27.91^\circ$ UNCONDITIONALLY STABLE

$$G_{p,\max} = 9.24 \text{ OR } 9.66 \text{ dB}, G_p = 9.66 - 1 = 8.66 \text{ dB}$$


FOR THE $G_p = 8.66$ dB CIRCLE: $g_p = 1.388$, $C_p = 0.292 \angle -129.4^\circ$, $r_p = 0.466$

(b) THE VALUES OF Γ_L ON THE 8.66 dB CIRCLE ARE:

$$\Gamma_L = C_p + r_p e^{j\theta_i} = 0.292 \angle -129.4^\circ + 0.466 e^{j\theta_i}$$

LETTING $\theta_i = 0, \frac{\pi}{2}, \pi$, AND $\frac{3\pi}{2}$ WE OBTAIN
THE VALUES OF Γ_L SHOWN IN THE TABLE.
THE ASSOCIATED VALUES OF Γ_{in} ARE ALSO
SHOWN.

FOR $(VSWR)_{in} = 1.5$ (OR $|\Gamma_{in}| = 0.2$),
USING (3.8.3) AND (3.8.4), THE CENTER AND
RADIUS OF THE $(VSWR)_{in} = 1.5$ CIRCLE ARE
CALCULATED.

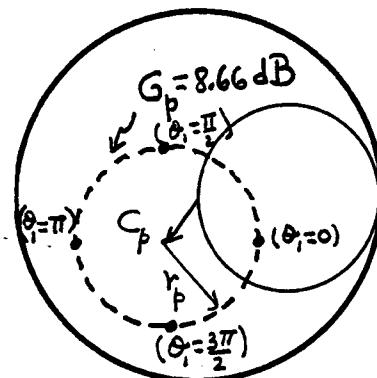

(c) THE VALUES OF Γ_L ON THE $(VSWR)_{in} = 1.5$ CIRCLE ARE GIVEN BY $\Gamma_L = C_{V_L} + r_L e^{j\theta_L}$. LETTING $\theta_L = 0$ AND π , TWO VALUES OF Γ_L ON THE $(VSWR)_{in} = 1.5$ CIRCLE ARE CALCULATED (SEE THE TABLE). THE ASSOCIATED VALUES OF Γ_{out} , $|r_L|$, AND $(VSWR)_{out}$ ARE ALSO SHOWN

Γ_L	Γ_{in}	$(VSWR)_{in} = 1.5$ CIRCLE	Γ_L	Γ_{out}	$ r_L $	$(VSWR)_{out}$
$(\theta_L=0)$ $0.36 \angle -38.8^\circ$	$0.548 \angle 47.1^\circ$	$C_{V_L} = 0.532 \angle -47.1^\circ$ $r_{V_L} = 0.142$	$0.637 \angle -37.7^\circ (\theta_L=0)$ $0.448 \angle -60.5^\circ (\theta_L=\pi)$	$0.311 \angle 129.5^\circ$ $0.259 \angle 91.2^\circ$	0.475 0.304	2.8 1.875
$(\theta_L=\pi/2)$ $0.304 \angle 127.6^\circ$	$0.634 \angle 27.9^\circ$	$C_{V_L} = 0.619 \angle -27.9^\circ$ $r_{V_L} = 0.122$	$0.729 \angle -23.4^\circ (\theta_L=0)$ $0.514 \angle -34.3^\circ (\theta_L=\pi)$	$0.314 \angle 161.7^\circ$ $0.219 \angle 123.5^\circ$	0.368 0.419	2.16 2.44
$(\theta_L=\pi)$ $0.689 \angle -160.9^\circ$	$0.81 \angle 34.2^\circ$	$C_{V_L} = 0.799 \angle -34.2^\circ$ $r_{V_L} = 0.071$	$0.859 \angle -31.5^\circ (\theta_L=0)$ $0.741 \angle -37.3^\circ (\theta_L=\pi)$	$0.501 \angle 153.7^\circ$ $0.399 \angle 136.2^\circ$	0.306 0.483	1.88 2.87
$(\theta_L=3\pi/2)$ $0.716 \angle -105^\circ$	$0.782 \angle 49.4^\circ$	$C_{V_L} = 0.77 \angle -49.4^\circ$ $r_{V_L} = 0.08$	$0.824 \angle -45.2^\circ (\theta_L=0)$ $0.721 \angle -54.2^\circ (\theta_L=\pi)$	$0.518 \angle 124.3^\circ$ $0.429 \angle 107.5^\circ$	0.430 0.415	2.51 2.42

FROM THESE CALCULATIONS IT IS SEEN THAT A DESIGN WITH $\Gamma_L = 0.689 \angle -160.9^\circ$ AND $\Gamma_L = 0.859 \angle -31.5^\circ$ GIVES: $G_p = 8.66 \text{dB}$, $(VSWR)_{in} = 1.88$, $(VSWR)_{out} = 1.5$.

3.33) (a) FROM EXAMPLE 3.7.2, FOR THE $G_p = 10 \text{dB}$ CIRCLE, $C_p = 0.572 \angle 97.2^\circ$, $r_p = 0.473$

FROM (3.8.9) AND (3.8.10), WITH $C_{in} = C_p$ AND $r_{in} = r_p$, WE OBTAIN:

$$C_i = 1.131 \angle 170.6^\circ \text{ AND } r_i = 0.622$$

(b) FOR $\Gamma_L = 0.1 \angle 97^\circ$, $\Gamma_{in} = 0.52 \angle 179.32^\circ$,


$$\Gamma_L = \Gamma_{in}^* = 0.52 \angle -179.32^\circ$$

THEN $(VSWR)_{in} = 1$

FOR $(VSWR)_{in} = 2$ (OR $|r_L| = 0.333$),

WE OBTAIN FROM (3.8.3) AND (3.8.4):
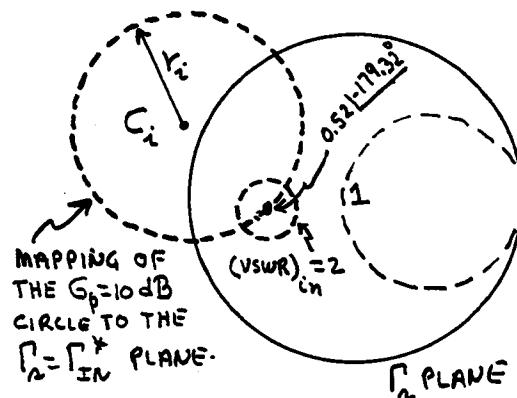
$$C_{V_L} = 0.477 \angle 179.32^\circ, r_{V_L} = 0.251$$



3.34) $K = 0.924, \Delta = 0.137 \angle -139^\circ \therefore$ POTENTIALLY UNSTABLE

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|} = \frac{8}{0.03} = 266.6 \text{ OR } 24.3 \text{ dB}$$

DESIGN FOR $G_p = 20 \text{ dB}$ (i.e., 4.3 dB LESS THAN G_{MSG}).

OUTPUT STABILITY CIRCLE:

$$C_L = 2.26 \angle 40.1^\circ, Y_L = 1.307$$

$G_p = 20 \text{ dB}$ CONSTANT-GAIN CIRCLE: ($\gamma_p = 1.563$)

$$C_p = 0.505 \angle 40.1^\circ, Y_p = 0.519$$

VALUES OF Γ_L ON $G_p = 20 \text{ dB}$ CIRCLE:

$$\Gamma_L = C_p + Y_p e^{j\theta} = 0.505 \angle 40.1^\circ + 0.519 e^{j\theta}$$

THE TABLE SHOWS TWO VALUES OF Γ_L (i.e., for $\theta_i = \pi$ AND $\theta_i = \frac{3\pi}{2}$), THE ASSOCIATED VALUES OF $\Gamma_2 = \Gamma_{IN}^+$, Γ_{OUT} , $|\Gamma_b|$, AND $(VSWR)_{OUT}$.



Γ_L	$\Gamma_2 = \Gamma_{IN}^+$	$(VSWR)_{IN}$	Γ_{OUT}	$ \Gamma_b $	$(VSWR)_{OUT}$
$(\theta_i = \pi)$ $0.352 \angle 112.2^\circ$	$0.655 \angle 163.4^\circ$	1	$0.668 \angle -44.8^\circ$	0.667	30.25
$(\theta_i = \frac{3\pi}{2})$ $0.432 \angle -26.6^\circ$	$0.607 \angle -79.2^\circ$	1	$0.674 \angle -34.3^\circ$	0.668	30.25

MAPPING OF THE $G_p = 20 \text{ dB}$ CIRCLE TO THE $\Gamma_2 = \Gamma_{IN}^+$ PLANE:

$$C_i = 0.823 \angle 175.3^\circ, Y_i = 0.227$$

INPUT STABILITY CIRCLE: $C_i = 1.65 \angle 175.3^\circ, Y_i = 0.679$

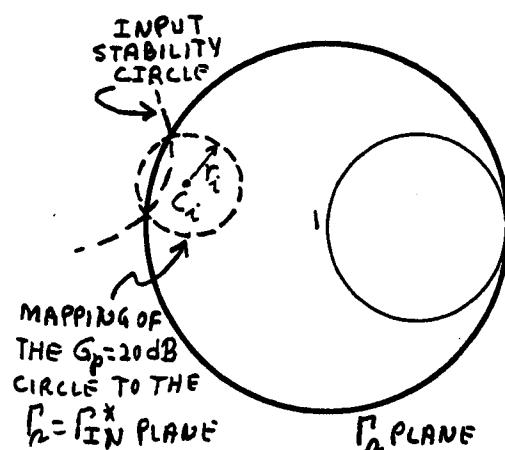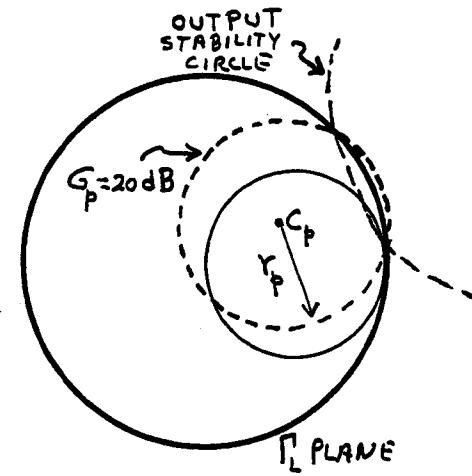THE VALUES OF $(VSWR)_{OUT} = 30.25$ SHOW THAT THE OUTPUT HAS TO BE MISMATCHED IN ORDER TO REDUCE THE GAIN TO 20 dB. THE DESIGNER CAN TRY TO REDUCE $(VSWR)_{OUT}$ BY RELAXING THE INPUT VSWR VALUE (SAY, LET $(VSWR)_{IN} \leq 1.5$), AS DISCUSSED IN EXAMPLE 3.8.2.



$$3.35) \quad K = 0.875, \Delta = 0.445 \underline{[160.4^\circ]} \quad \therefore \text{POTENTIALLY UNSTABLE}$$

$$G_{MSG} = \frac{|S_{21}|}{|S_{12}|} = \frac{3.1}{0.125} = 24.8 \text{ OR } 13.9 \text{ dB}$$

DESIGN FOR $G_A = 10 \text{ dB}$ (i.e., 3.9 dB LESS THAN G_{MSG})

INPUT STABILITY CIRCLE:


$$C_a = 3.303 \underline{[-173.2^\circ]}, Y_a = 2.392$$

$G_A = 10 \text{ dB}$ CONSTANT-GAIN CIRCLE: ($\rho_a = 1.041$)

$$C_a = 0.296 \underline{[-173.2^\circ]}, Y_a = 0.73$$

VALUES OF Γ_L ON THE $G_A = 10 \text{ dB}$ CIRCLE:
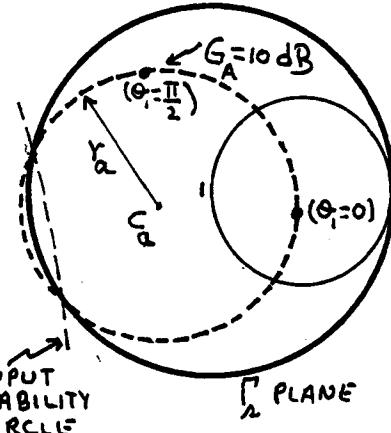
$$\Gamma_L = C_a + Y_a e^{j\theta_i} = 0.296 \underline{[-173.2^\circ]} + 0.73 e^{j0^\circ}$$



THE TABLE SHOWS TWO VALUES OF Γ_L (i.e., for $\theta_i = 0$ AND $\theta_i = \frac{\pi}{2}$), THE ASSOCIATED VALUES OF $\Gamma_L = \Gamma_{out}^*$, Γ_{in} , $|\Gamma_{al}|$, AND $(VSWR)_{in}$.

Γ_L	$\Gamma_L = \Gamma_{out}^*$	$(VSWR)_{out}$	Γ_{in}	$ \Gamma_{al} $	$(VSWR)_{in}$
$(\theta_i = 0)$ $0.437 \underline{[-4.6^\circ]}$	$0.405 \underline{[70.8^\circ]}$	1	$0.565 \underline{[172^\circ]}$	0.802	9.1
$(\theta_i = \pi/2)$ $0.755 \underline{[112.9^\circ]}$	$0.08 \underline{[133.5^\circ]}$	1	$0.624 \underline{[-171.9^\circ]}$	0.802	9.1


MAPPING OF THE $G_A = 10 \text{ dB}$ CIRCLE TO THE $\Gamma_L = \Gamma_{out}^*$ PLANE:

$$C_o = 0.646 \underline{[130.9^\circ]} \text{ AND } Y_o = 0.566$$

OUTPUT STABILITY CIRCLE:

$$C_o = 9.33 \underline{[-49.1^\circ]}, Y_o = 10.19$$

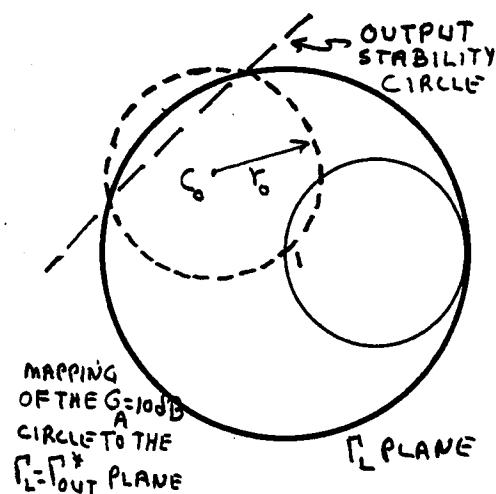THE VALUES OF $(VSWR)_{in} = 9.1$ SHOW THAT THE INPUT HAS TO BE MISMATCHED IN ORDER TO REDUCE THE GAIN TO 10 dB . (i.e., $G_A = 10 \text{ dB}$). THE DESIGNER CAN TRY TO REDUCE $(VSWR)_{in}$ BY RELAXING THE OUTPUT VSWR.



3.36) (a) dc model

$$(b) V_{TH} = \frac{24(4k)}{4k+16k} = 4.8V$$


$$R_{TH} = 4k//16k = 3.2k\Omega$$

$$V_{TH} = I_B R_{TH} + 0.7 + I_c R_E \quad (I_c \approx I_E)$$

$$\therefore I_B = \frac{V_{TH} - 0.7}{R_{TH} + \beta R_E} = 40\mu A$$

$$I_c = \beta I_B = 4mA$$
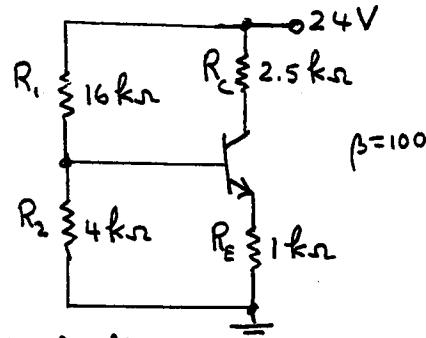
$$V_{CE} = V_{CC} - I_c (R_C + R_E) = 24 - 4m(2.5k + 1k) = 10V$$



(c) AT 500MHz THE $0.1\mu F$ ($Z_c = -j0.003\Omega$) ACT AS SHORT CIRCUITS TO THE AC SIGNAL. THUS, RFCs ARE NOT NEEDED IN SERIES WITH THE $16k\Omega$ AND $2.5k\Omega$ RESISTORS.


THE $100nH$ INDUCTOR ($Z_L = j314\Omega$) IMPEDANCE IS ABOUT 10% OF THE RESISTANCE OF $R_2 = 4k\Omega$. THUS, A RFC SHOULD BE USED IN SERIES WITH THE $4k\Omega$ RESISTOR.

(d) ac model

$$(e) Z = \frac{1}{50pF j2\pi 500 \cdot 10^6 \cdot 50 \cdot 10^{-12}} = -j6.37\Omega \quad 50\Omega$$

$$Z_{100nH} = j2\pi 500 \cdot 10^6 \cdot 100 \cdot 10^{-9} = j314.2\Omega$$

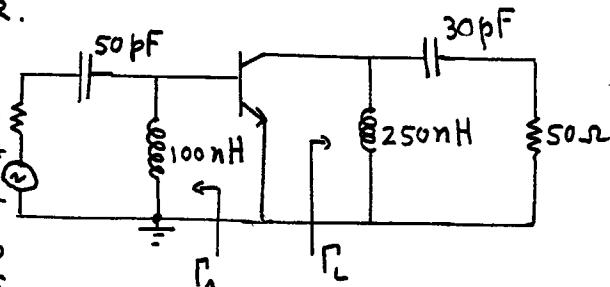USING THE ZY CHART IT IS SIMPLE TO CALCULATE: $Z_n = 1.05 + j0.035$
AND $\Gamma_n = 0.02 \angle 65.8^\circ$



SIMILARLY: $Z_L = 1.05 - j0.11$
AND $\Gamma_L = 0.06 \angle -61^\circ$

3.37) (a) dc model


$$(b) 20 = I_c R_c + V_{CE}$$

$$\text{OR } R_c = \frac{20 - 10}{5m} = 2k\Omega$$

$$V_{CE} = I_B R_B + 0.7$$

$$R_B = \frac{10 - 0.7}{(\frac{5m}{100})} = 186k\Omega$$

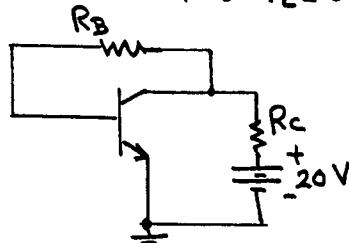THIS TYPE OF DC BIAS RESULTS IN A LARGE VALUE FOR R_B .



(c) ac model

$$\text{AT } f=300\text{MHz}: Z_{30pF} = -j17.68\Omega$$


$$Z_{40nH} = -j7.58\Omega, Z_{70nH} = j75.4\Omega$$

$$Z_{70nH} = j131.9\Omega$$

USING THE ZY SMITH CHART OR

SIMPLE CALCULATIONS, WE OBTAIN:
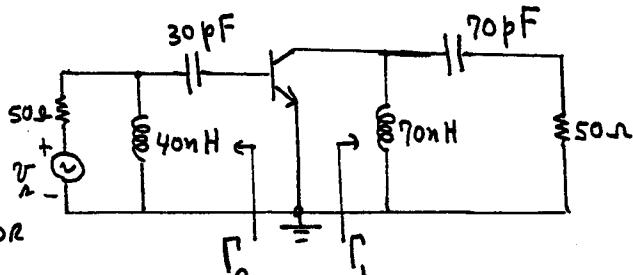
$$Z_n = 35.1 + j5.2\Omega \text{ OR } \Gamma_n = 0.185 \angle 157.3^\circ; Z_L = 49.9 + j1.25\Omega \text{ OR } \Gamma_L = 0.96 \angle 0^\circ$$



$$3.38) \text{ LET } V_{CC} = 20V, R_E = \frac{10\% V_{CC}}{I_c} = \frac{0.1(20)}{10m} = 200\Omega$$

$$V_{CC} = V_{CE} + I_c(R_C + R_E) \Rightarrow R_C + 200 = \frac{20 - 10}{4m} = 2.5k, \text{ OR } R_C = 2.3k\Omega$$

$$\text{FOR GOOD } \beta \text{ STABILITY LET } R_{TH} = \left(\frac{\beta R_E}{10} - \frac{100(200)}{10} \right) = 2k\Omega$$

$$V_{TH} = I_B R_{TH} + 0.75 + I_c R_E = \frac{4m}{100} (2k) + 0.75 + 4m(200) = 1.63V$$

$$R_1 = R_{TH} \frac{V_{CC}}{V_{TH}} = 2.3k \frac{20}{1.63} = 28.22k\Omega$$

$$R_2 = \frac{R_{TH}}{1 - V_{TH}/V_{CC}} = \frac{2.3k}{1 - \left(\frac{1.63}{20}\right)} = 2.5k\Omega$$

$$3.39) \quad I_{C2} = 10mA. \quad \text{LET } I_3 = 20mA, \text{ THEN } I_{C1} = I_3 - I_{C2} = 20m - 10m = 10mA$$

$$\therefore R_4 = \frac{0.75}{I_{C1}} = \frac{0.75}{10m} = 75\Omega. \quad \text{LET } V_{CC} = 20V$$

$$R_3 = \frac{V_{CC} - V_{CE,2}}{I_3} = \frac{20 - 10}{20m} = 500\Omega$$

$$\text{FOR GOOD } \beta \text{ STABILITY LET } I_{R_1} \approx I_{R_2} = 20 I_{B1} = 20 \frac{10m}{100} = 2mA,$$

$$V_{B,1} = V_{CE,2} - 0.75 = 9.25V$$

$$R_1 = \frac{V_{CC} - V_{B,1}}{I_{R_1}} = \frac{20 - 9.25}{2m} = 5.37k\Omega$$

$$R_2 = \frac{V_{B,1}}{I_{R_2}} = \frac{9.25}{2m} = 4.63k\Omega$$

$$3.40) (a) \text{ IN FIG. 3.9.2a: } V_{CC} = (I_B + I_c) R_C + I_B R_B + V_{BE} \quad (1)$$

$$\text{AND } I_c = h_{FE} I_B + (h_{FE} + 1) I_{CBO} \quad (2)$$

SUBSTITUTING (2) INTO (1) GIVES:

$$V_{CC} - V_{BE} = \left(\frac{I_c}{h_{FE}} - I_{CBO} \frac{(h_{FE} + 1)}{h_{FE}} \right) (R_C + R_B) + I_c R_C$$

$$\text{OR } I_c = \frac{h_{FE}(V_{CC} - V_{BE})}{R_B + R_C(h_{FE} + 1)} + \frac{I_{CBO}(h_{FE} + 1)(R_C + R_B)}{R_B + R_C(h_{FE} + 1)}$$

$$S_i = \frac{\partial I_c}{\partial I_{CBO}} = \frac{(h_{FE} + 1)(R_C + R_B)}{R_B + R_C(h_{FE} + 1)}$$

$$S_{V_{BE}} = \frac{\partial I_c}{\partial V_{BE}} = \frac{-h_{FE}}{R_B + R_C(h_{FE} + 1)}$$

IN THE DERIVATION OF $S_{h_{FE}}$ WE NEGLECT THE CONTRIBUTION FROM I_{CBO} . HENCE,

$$I_{C2} = \frac{h_{FE,2}(V_{CC} - V_{BE})}{R_B + R_C(h_{FE,2}-1)} \quad \text{AND} \quad I_{C1} = \frac{h_{FE}(V_{CC} - V_{BE})}{R_B + R_C(h_{FE}-1)}$$

$$\frac{I_{C2}}{I_{C1}} - 1 = \frac{h_{FE,2}[R_B + R_C(h_{FE}-1)]}{h_{FE}[R_B + R_C(h_{FE,2}-1)]} - 1 = \frac{(h_{FE,2} - h_{FE}) S_{i2}}{h_{FE} h_{FE,2}}$$

$$\text{OR } S_{h_{FE}} = \frac{\Delta I_C}{\Delta h_{FE}} = \frac{I_{C2} - I_{C1}}{h_{FE,2} - h_{FE}} = \frac{I_{C1} S_{i2}}{h_{FE} h_{FE,2}}$$

$$(b) I_B = \frac{I_C}{h_{FE}} = \frac{10 \cdot 10^{-3}}{50} = 0.2 \text{ mA}, R_B = \frac{V_{CE} - 0.7}{I_B} = \frac{10 - 0.7}{0.2 \cdot 10^{-3}} = 46.5 \text{ k}\Omega$$

$$R_C = \frac{V_{CC} - V_{CE}}{I_C + I_B} = \frac{20 - 10}{10.2 \cdot 10^{-3}} = 980 \Omega$$

(c) IF $h_{FE} = 100$, I_{C1} INCREASES FROM 10 mA TO:

$$I_{C2} = \frac{h_{FE,2}(V_{CC} - 0.7)}{R_B + R_C(h_{FE,2}+1)} \quad \text{WHERE } h_{FE,2} = 100$$

$$= \frac{100(20 - 0.7)}{46.5 \cdot 10^3 + 0.98 \cdot 10^3(100+1)} = 13.3 \text{ mA}$$

$$\text{AND } V_{CE} = V_{CC} - I_{C2} R_C = 20 - 13.3 \cdot 10^{-3} (0.98 \cdot 10^3) = 7 \text{ V}$$

$$3.41) \text{ LET } V_{CC} = 12 \text{ V}, R_E = \frac{10\% V_{CC}}{I_C} = \frac{0.1(12)}{1 \text{ mA}} = 1.2 \text{ k}\Omega$$

$$V_{CC} = V_{CE} + I_C(R_C + R_E) \Rightarrow R_C + 1.2 \text{ k} = \frac{12 - 6}{6} = 6 \text{ k}\Omega \text{ OR } R_C = 4.8 \text{ k}\Omega.$$

$$\text{FROM } S_i = \frac{(\beta+1)(R_{TH} + R_E)}{R_{TH} + (\beta+1)R_E} \Rightarrow S = \frac{\frac{1 \text{ mA}}{101} (R_{TH} + 1.2 \text{ k})}{R_{TH} + (\frac{1 \text{ mA}}{101}) 1.2 \text{ k}} \therefore R_{TH} = 5.05 \text{ k}\Omega$$

$$V_{TH} = I_B R_{TH} + 0.7 + I_C R_E = \frac{1 \text{ mA}}{100} (4.8 \text{ k}) + 0.7 + 1 \text{ mA} (1.2 \text{ k}) = 1.95 \text{ V}$$

$$R_1 = R_{TH} \frac{V_{CC}}{V_{TH}} = 5.05 \text{ k} \frac{12}{1.95} = 31.1 \text{ k}\Omega$$

$$R_2 = \frac{R_{TH}}{1 - V_{TH}/V_{CC}} = \frac{5.05 \text{ k}}{1 - 1.95/12} = 6.03 \text{ k}$$

$$(b) I_{CBO,2} = 1 \cdot 10^{-6} 2 \frac{75-25}{10} = 32 \mu\text{A}, h_{FE,2} = 100 + \frac{0.5}{100} (75-25) 100 = 125$$

$$S_i = S, S_{V_{BE}} = \frac{-100}{5.05 \cdot 10^3 + (101) \cdot 1.2 \cdot 10^3} = 0.8 \cdot 10^3, S_{h_{FE}} = \frac{10^{-3} (5.4)}{100 (125)} = 4.3 \cdot 10^{-7}$$

$$\text{AT } 75^\circ\text{C}: I_C = \frac{125(1.95 - 0.7)}{5.05 \cdot 10^3 + (125) \cdot 1.2 \cdot 10^3} + \frac{125(32 \cdot 10^{-6})(5.05 \cdot 10^3 + 1.2 \cdot 10^3)}{5.05 \cdot 10^3 + (125) \cdot 1.2 \cdot 10^3} \\ = 1.16 \text{ mA}$$

$$3.42) \quad I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_P} \right]^2 \Rightarrow 10m = 30m \left[1 + \frac{V_{GS}}{3} \right]^2 \therefore V_{GS} = -1.268V$$

$$R_s = \frac{-V_{GS}}{I_D} = \frac{1.268}{10m} = 126.8 \Omega$$

LET $V_{CC} = V_{EE} = 10V$ AND $I_R = 20mA$, WHERE $I_R = I_c + I_D$
 $\therefore I_c = 20mA - 10mA = 10mA$

THE VOLTAGE AT THE GATE IS ZERO (i.e., ACROSS R_G). HENCE,

$$R_s = \frac{0 - (-V_{EE})}{I_c} = \frac{10}{10mA} = 1k\Omega$$

$$V_E = V_{DS} + V_{R_s} = 3 + 1.268 = 4.27V$$

THEN,
 $R_i = \frac{V_{CC} - V_E}{I_{R_1}} = \frac{10 - 4.27}{20mA} = 287 \Omega$


LET $I_{R_2} \approx I_{R_3} = 20mA$ $I_B = 20 \frac{10mA}{100} = 2mA$

$$V_B = V_E - 0.7 = 4.27 - 0.7 = 3.57V$$

$$R_2 = \frac{V_{CC} - V_B}{I_{R_2}} = \frac{10 - 3.57}{2mA} = 3.21k\Omega$$

$$R_3 = \frac{V_B}{I_{R_3}} = \frac{3.57}{2mA} = 1.78k\Omega$$

4.1) (a)

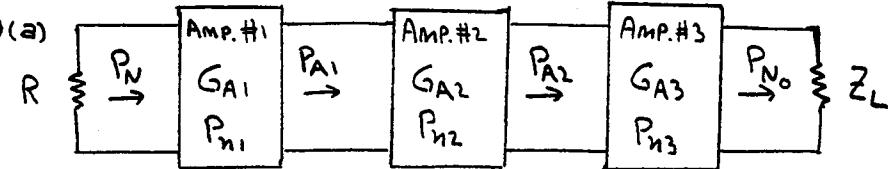

$$P_N = kTB \quad P_{A1} = G_{A1}P_N + P_{n1} \quad P_{A2} = G_{A2}P_{A1} + P_{n2} \quad P_{N_o} = G_{A3}P_{A2} + P_{n3}$$

$$F = \frac{P_{N_o}}{P_N G_{A1} G_{A2} G_{A3}} = \frac{G_{A3} G_{A2} G_{A1} P_N + G_{A3} G_{A2} P_{n1} + G_{A3} P_{n2} + P_{n3}}{P_N G_{A1} G_{A2} G_{A3}}$$

$$= 1 + \frac{P_{n1}}{P_N G_{A1}} + \frac{P_{n2}}{P_N G_{A1} G_{A2}} + \frac{P_{n3}}{P_N G_{A1} G_{A2} G_{A3}} \quad (1)$$

$$\text{LET: } F_1 = 1 + \frac{P_{n1}}{P_N G_{A1}}, \quad F_2 = 1 + \frac{P_{n2}}{P_N G_{A2}}, \quad F_3 = 1 + \frac{P_{n3}}{P_N G_{A3}}$$

THEREFORE, (1) CAN BE EXPRESSED IN THE FORM:

$$F = F_1 + \frac{F_2 - 1}{G_{A1}} + \frac{F_3 - 1}{G_{A1} G_{A2}}$$

$$(b) \quad F = 10^{\frac{0.1}{10}} + \frac{10^{\frac{0.3}{10}} - 1}{10^{\frac{0.1}{10}}} = 1.358 \text{ OR } 1.33 \text{ dB}$$

4.2) (a) THE GAIN-CIRCLES ARE THE CONSTANT-GAIN G_A CIRCLES.

FROM FIG. P.2(a): $F_{min} = 3.3 \text{ dB}$, $\Gamma_{opt} \approx 0.56 \angle -155^\circ$.

γ_n IS EVALUATED BY READING A VALUE OF F AND ITS ASSOCIATED Γ_n , AND USING (4.3.4). FROM FIG. P.2(a) WE READ:

$F = 4.5 \text{ dB}$ AT $\Gamma_n \approx 0.56 \angle -94^\circ$. THEN

$$10^{\frac{0.45}{10}} = 10^{\frac{0.33}{10}} + \frac{4\gamma_n |0.56 \angle -94^\circ - 0.56 \angle -155^\circ|^2}{(1 - (0.56)^2) |1 + 0.56 \angle -155^\circ|^2} \Rightarrow \gamma_n = 0.108$$

FROM FIG. P.2(b): $F_{min} = 1.7 \text{ dB}$, $\Gamma_{opt} \approx 0.215 \angle 149^\circ$.

USING: $F = 3 \text{ dB}$ AT $\Gamma_n = 0.445 \angle 26^\circ$ WE OBTAIN $\gamma_n = 0.202$

(b) FOR THE $G_A = 10.7 \text{ dB}$ CIRCLE IN FIG. 4.3.4:

$$g_a = 4.158, \quad C_a = 0.574 \angle -154^\circ, \quad \gamma_a = 0.423$$

4.3) (a) THE $G_A = 14 \text{ dB}$ CIRCLE AND THE $F = 2 \text{ dB}$ CIRCLE INTERSECT AT TWO POINTS. THE VALUE OF Γ_n AT THESE THE POINTS ARE:

$$\Gamma_n \approx 0.5 \angle 160^\circ \text{ AND } \Gamma_n \approx 0.25 \angle -150^\circ$$

(b) LET $\Gamma_n = 0.5 \angle 160^\circ$, THEN $\Gamma_{out} = 0.657 \angle -73.3^\circ$

$$\text{FOR } (VSWR)_{out} = 1 : \quad \Gamma_L = \Gamma_{out}^* = 0.657 \angle 73.3^\circ$$

$$\text{THEN, } \Gamma_{in} = 0.8 \angle 165.6^\circ, \quad |\Gamma_a| = 0.678, \quad (VSWR)_{in} = 5.2$$

4.4) (a) $K = 2.25$ AND $\Delta = 0.246 \angle 112.8^\circ \therefore$ UNCONDITIONALLY STABLE

$$(b) G_{A,\max} = \frac{|S_{21}|}{|S_{12}|} (K - \sqrt{K^2 - 1}) = 9.36 \text{ OR } 9.71 \text{ dB}$$

$$(c) G_A = 9.71 - 3 = 6.71 \text{ dB}$$

FOR THE $G_A = 6.71 \text{ dB}$ CIRCLE: $g_a = 1.173$,

$$C_a = 0.42 \angle 174.5^\circ, Y_a = 0.515$$


(d) FOR THE 3dB NOISE CIRCLE:

$$C_{F_t} = 0.405 \angle 145^\circ, Y_{F_t} = 0.388$$

FOR THE 4 dB NOISE CIRCLE:

$$C_{F_t} = 0.279 \angle 145^\circ, Y_{F_t} = 0.616$$

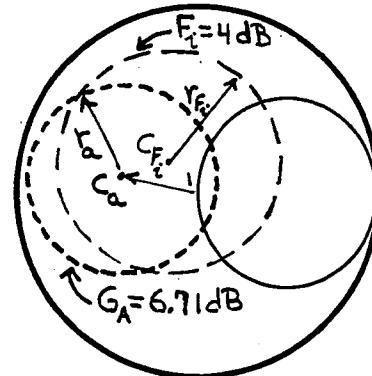THE $F_t = 4 \text{ dB}$ CIRCLE IS DRAWN ON
THE SMITH CHART.



Γ_h PLANE


(e) FOR $G_{A,\max}$: $\Gamma_h = \Gamma_{m_h} = 0.667 \angle 174.5^\circ, \Gamma_L = \Gamma_{m_L} = 0.587 \angle 102.2^\circ$.

$$\therefore F = 10^{0.25} + \frac{4(\frac{\Gamma}{50}) | 0.667 \angle 174.5^\circ - 0.5 \angle 145^\circ |^2}{(1 - (0.667)^2) | 1 + 0.5 \angle 145^\circ |^2} = 1.97 \text{ OR } 2.95 \text{ dB}$$

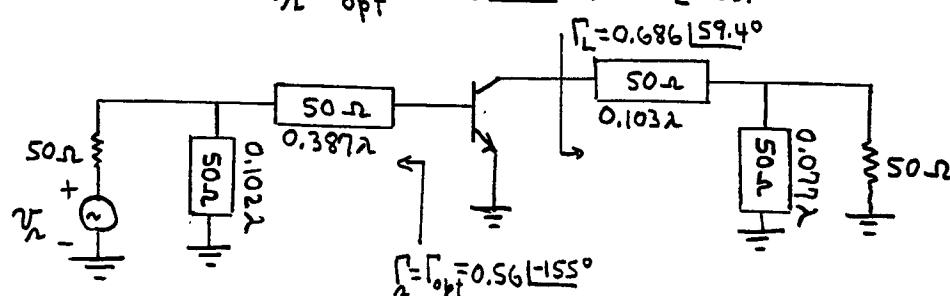4.5) $F_{min} = 3.3 \text{ dB}, \Gamma_{opt} = 0.56 \angle 155^\circ, Y_h = 0.108$

$K = 1.1, \Delta = 0.273 \angle 26.8^\circ \therefore$ UNCONDITIONALLY STABLE

DESIGN WITH $\Gamma_h = \Gamma_{opt} = 0.56 \angle 155^\circ$ AND $\Gamma_L = \Gamma_{out}^* = 0.686 \angle 59.4^\circ$



$$G_A = 16.67 \text{ OR } 12.2 \text{ dB}$$


$$G_T = G_A = 16.67 \text{ OR } 12.2 \text{ dB}$$

$$G_p = 20.62 \text{ OR } 13.1 \text{ dB}$$

ALSO: $\Gamma_{IN} = 0.801 \angle 156.2^\circ, |\Gamma_a| = 0.438, (VSWR)_{in} = 2.6, (VSWR)_{out} = 1$.

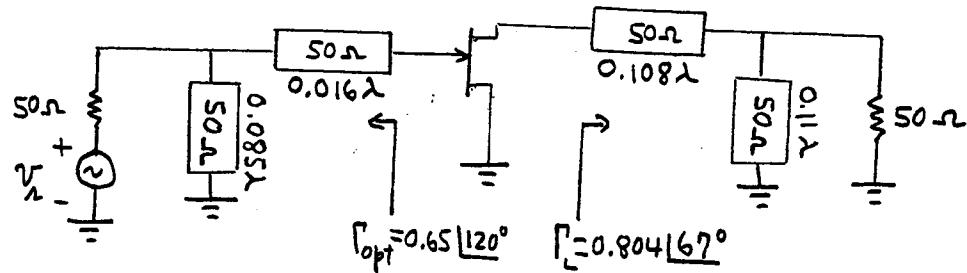4.6) $K = 2.18$, $\Delta = 0.555 \angle -178.3^\circ \therefore$ UNCONDITIONALLY STABLE

DESIGN WITH $\Gamma_L = \Gamma_{opt} = 0.65 \angle 120^\circ$ AND $\Gamma_L = \Gamma_{out}^* = 0.804 \angle 67^\circ$



$$G_A = G_T = 75.6 \text{ OR } 18.8 \text{ dB}$$


$$\text{ALSO: } \Gamma_{IN} = 0.806 \angle -119.6^\circ, |\Gamma_a| = 0.327, (\text{VSWR})_{in} = 1.97, (\text{VSWR})_{out} = 1$$

4.7) $K = 1.235$, $\Delta = 0.175 \angle 166.2^\circ \therefore$ UNCONDITIONALLY STABLE

$$G_{A,\max} = 43.07 \text{ OR } 16.3 \text{ dB}, \Gamma_{M_L} = 0.787 \angle -170.1^\circ, \Gamma_{ML} = 0.749 \angle 44.8^\circ$$


Γ_L	$\Gamma_L = \Gamma_{out}^*$	Γ_{IN}	$ \Gamma_a $	$(\text{VSWR})_{in}$	G_A (dB)	F (dB)
$0.2 \angle 155^\circ$	$0.528 \angle 41.7^\circ$	$0.704 \angle 170.8^\circ$	0.62	4.27	13.75	1.6
$0.32 \angle 172^\circ$	$0.559 \angle 42.9^\circ$	$0.715 \angle 170.8^\circ$	0.535	3.30	14.5	1.66
$0.43 \angle 180^\circ$	$0.592 \angle 43.7^\circ$	$0.726 \angle 170.7^\circ$	0.446	2.61	15.1	1.82
$0.59 \angle -174^\circ$	$0.650 \angle 44.5^\circ$	$0.747 \angle 170.6^\circ$	0.290	1.81	15.8	2.30
$0.787 \angle -170.1^\circ$	$0.749 \angle 44.8^\circ$	$0.787 \angle 170.1^\circ$	0	1	16.3	3.76

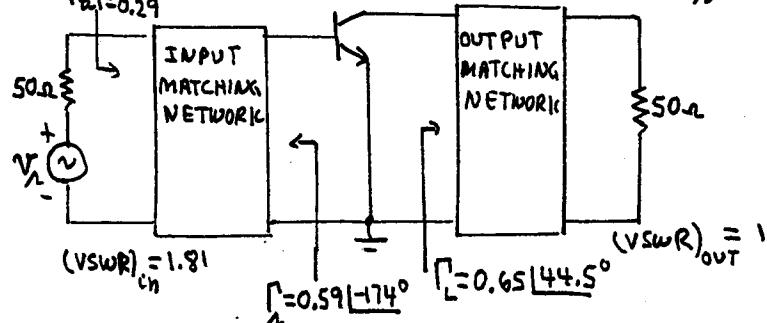THE DESIGN CAN BE PERFORMED WITH $\Gamma_L = 0.59 \angle -174^\circ$ AND $\Gamma_L = 0.65 \angle 44.5^\circ$.



$$G_A = 15.8 \text{ dB}$$

$$F = 2.3 \text{ dB}$$

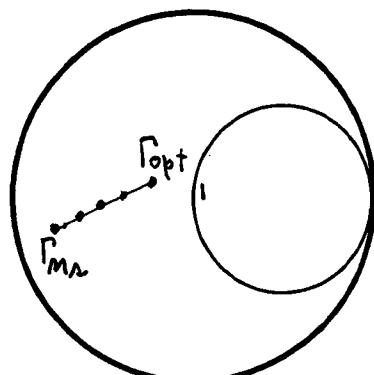

4.8) $K = 0.96$, $\Delta = 0.6 \angle -73.1^\circ$ \therefore POTENTIALLY UNSTABLE


INPUT STABILITY CIRCLE: $C_L = 1.34 \angle 62.7^\circ$, $\Gamma_L = 0.345$

OUTPUT STABILITY CIRCLE: $C_L = 1.55 \angle 47.2^\circ$, $\Gamma_L = 0.56$

DESIGN WITH $\Gamma_L = \Gamma_{opt} = 0.73 \angle 60^\circ$ AND $\Gamma_L = \Gamma_{out}^* = 0.787 \angle 42.2^\circ$

BOTH Γ_{opt} AND Γ_L ARE IN THE STABLE REGION (AS EXPECTED).

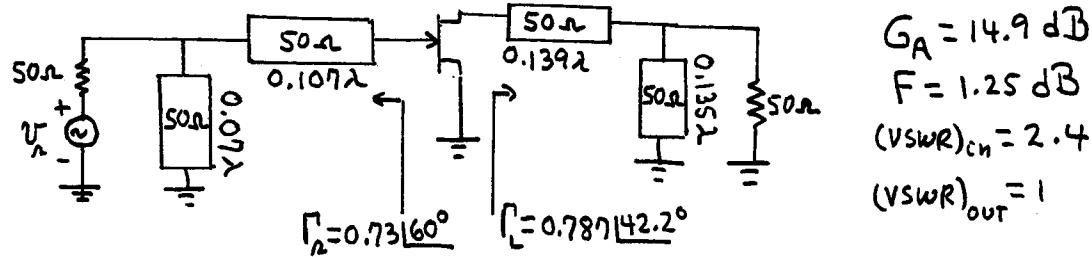A DESIGN FOR Γ_{opt} AND Γ_L IS SHOWN BELOW:



4.9) THIS TRANSISTOR IS POTENTIALLY UNSTABLE.

$G_{MSG} = 59.6$ OR 17.8 dB . LET US DESIGN FOR $G_A = 14 \text{ dB}$.


FIG. P4.2(b) SHOWS THAT THE $G_A = 14 \text{ dB}$ CIRCLE AND THE $F = 2 \text{ dB}$ CIRCLE INTERSECT AT TWO POINTS, NAMELY:

$$\Gamma_L \approx 0.5 \angle 160^\circ \text{ AND } \Gamma_L \approx 0.25 \angle -150^\circ$$

Γ_L	$G_A(\text{dB})$	$F(\text{dB})$	$\Gamma_L = \Gamma_{out}^*$	$(VSWR)_{out}$	Γ_{in}	$ \Gamma_{in} $	$(VSWR)_{in}$
$0.5 \angle 160^\circ$	13.6	2	$0.657 \angle 73.3^\circ$	1	$0.8 \angle 165.6^\circ$	0.678	5.2
$0.25 \angle -150^\circ$	13.5	1.9	$0.685 \angle 65.3^\circ$	1	$0.793 \angle 162.4^\circ$	0.683	5.3

SELECT $\Gamma_L = 0.5 \angle 160^\circ$ AND $\Gamma_L = 0.657 \angle 73.3^\circ$.

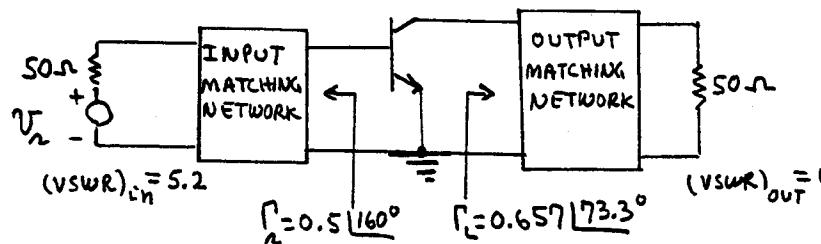$G_T = G_A = 13.6 \text{ dB}$ AND $G_p = 17.2 \text{ dB}$



4.10) TRANSISTOR #1: $K=0.869$, $\Delta=0.348 \angle -39.2^\circ$ \therefore POTENTIALLY UNSTABLE
 $G_{MSG}=44$ OR 16.4 dB.


INPUT STABILITY CIRCLE: $C_L=16.75 \angle -37.3^\circ$, $\Gamma_L=17.61$

OUTPUT STABILITY CIRCLE: $C_L=4.06 \angle 44.5^\circ$, $\Gamma_L=3.16$

THE $G_A=14$ dB, 12 dB, AND 10 dB CIRCLES, THE $F_L=2$ dB, AND 2.5 dB CIRCLES, AND THE INPUT STABILITY CIRCLE ARE DRAWN IN THE SMITH CHART.

G_A (dB)	C_A	Γ_A	F_L (dB)	C_{F_L}	Γ_{F_L}
14	$0.561 \angle 142.7^\circ$	0.597	2	$0.306 \angle 79^\circ$	0.258
12	$0.35 \angle 142.7^\circ$	0.724	2.5	$0.254 \angle 77^\circ$	0.458
10	$0.219 \angle 142.7^\circ$	0.821			

LET US TRY A DESIGN WITH Γ_L AT POINT "a": $\Gamma_a=0.08 \angle 31^\circ$. WITH THIS VALUE OF Γ_L WE FIND: $\Gamma_L=\Gamma_{out}^*=0.485 \angle 37.5^\circ$, $\Gamma_{in}=0.555 \angle -140^\circ$, $|\Gamma_a|=0.577$, AND $(VSWR)_{in}=3.7$. THE VALUE OF $(VSWR)_{out}$ CAN BE IMPROVED IF WE DESIGN FOR A HIGHER $(VSWR)_{out}$.

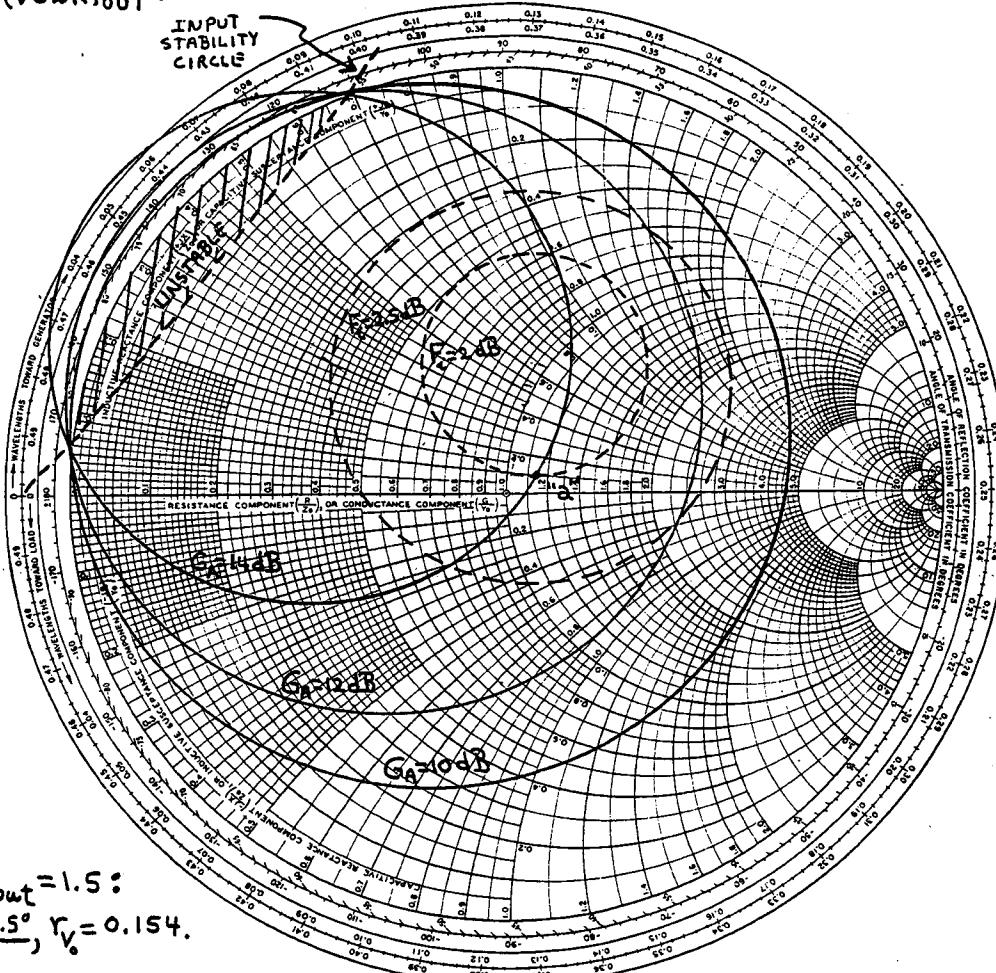

FOR $(VSWR)_{out}=1.5$:

$$C_{V_o}=0.47 \angle 37.5^\circ, \Gamma_V=0.154.$$

SELECTING $\Gamma_L=0.32 \angle 37.5^\circ$ IT FOLLOWS THAT

$$\Gamma_{in}=0.449 \angle -134.7^\circ, |\Gamma_a|=0.47, \text{ AND } (VSWR)_{in}=2.78$$

TRANSISTOR #2 : THE DESIGN PROCEDURE IS SIMILAR TO THE ONE USED WITH TRANSISTOR #1. ONLY THE CALCULATIONS FOR THE G_A CIRCLES AND FOR THE NOISE CIRCLES ARE GIVEN.

$$K = 0.244, \Delta = 0.263 \angle 56.2^\circ \therefore \text{POTENTIALLY UNSTABLE}$$

$$G_{MSG} = 22.5 \text{ dB}$$

$$\text{INPUT STABILITY CIRCLE: } C_L = 2.04 \angle 172.2^\circ, Y_L = 1.55$$

$$\text{OUTPUT STABILITY CIRCLE: } C_L = 1.63 \angle 21.9^\circ, Y_L = 1.07$$

THE CALCULATIONS FOR THE $G_A = 18 \text{ dB}$ AND 16 dB CIRCLES, AND FOR THE $F_t = 1.2 \text{ dB}$ AND 1.5 dB CIRCLES ARE:

$G_A(\text{dB})$	C_A	Y_A	$F_t(\text{dB})$	C_{F_t}	Y_{F_t}
18	$0.376 \angle 172.2^\circ$	0.796	1.2	$0.39 \angle 32^\circ$	0.246
16	$0.255 \angle 172.2^\circ$	0.849	1.5	$0.35 \angle 32^\circ$	0.378

4.11) $K = 0.774, \Delta = 0.46 \angle -129.3^\circ \therefore \text{POTENTIALLY UNSTABLE.}$

$$G_{MSG} = 14.36 \text{ dB}$$

$$\text{INPUT STABILITY CIRCLE: } \begin{cases} C_L = 2.06 \angle 120.3^\circ \\ Y_L = 1.19 \end{cases} \quad \text{OUTPUT STABILITY CIRCLE: } \begin{cases} C_L = 334.6 \angle -65.4^\circ \\ Y_L = 335.4 \end{cases}$$

$G_p(\text{dB})$	C_p	Y_p
12	$0.58 \angle 114.6^\circ$	0.663
10	$0.366 \angle 114.6^\circ$	0.754

THE TRANSFORMATIONS OF THE $G_p = 12 \text{ dB}$ AND 10 dB CIRCLES TO THE $\Gamma_h = \Gamma_{IN}^*$ PLANE ARE SHOWN IN THE SMITH CHART. ALSO, THE $F_t = 1.2 \text{ dB}$ AND 1.5 dB CIRCLES ARE SHOWN, AS WELL AS ONE $(VSWR)_{IN} = 2$ CIRCLE.

$$G_p = 12 \text{ dB} \text{ CIRCLE IN THE } \Gamma_h = \Gamma_{IN}^* \text{ PLANE: } C_{F_t} = 0.959 \angle 120.3^\circ, Y_{F_t} = 0.366$$


$$G_p = 10 \text{ dB} \text{ CIRCLE IN THE } \Gamma_h = \Gamma_{IN}^* \text{ PLANE: } C_{F_t} = 0.858 \angle 120.3^\circ, Y_{F_t} = 0.372$$

$$F_t = 1.2 \text{ dB} \text{ CIRCLE IN THE } \Gamma_h \text{ PLANE: } C_{F_t} = 0.654 \angle 55^\circ, Y_{F_t} = 0.188$$

$$F_t = 1.5 \text{ dB} \text{ CIRCLE IN THE } \Gamma_h \text{ PLANE: } C_{F_t} = 0.621 \angle 55^\circ, Y_{F_t} = 0.252$$

A POINT ON THE $G_p = 10 \text{ dB}$ CIRCLE IS $\Gamma_L = 0.416 \angle -57.3^\circ$. THEN, $\Gamma_{IN} = 0.62 \angle -97^\circ$. THE VALUE $\Gamma_h = \Gamma_{IN}^*$ RESULTS IN $(VSWR)_{IN} = 1$, AND A VERY-HIGH NOISE FIGURE. THE CIRCLE $(VSWR)_{IN} = 2$ IS DRAWN (i.e., $C_{V_h} = 0.576 \angle 97^\circ$ AND $Y_h = 0.214$). A CONVENIENT VALUE OF Γ_h IS AT POINT "a": $\Gamma_h = 0.56 \angle 79^\circ$, AND IT FOLLOWS THAT

Γ_h	Γ_L	$G_p(\text{dB})$	$F_t(\text{dB})$	Γ_{out}	$ \Gamma_a $	$(VSWR)_{IN}$	$ \Gamma_b $	$(VSWR)_{out}$
$0.56 \angle 79^\circ$	$0.416 \angle -57.3^\circ$	10	1.5	$0.35 \angle -107^\circ$	0.286	1.8	0.664	4.9

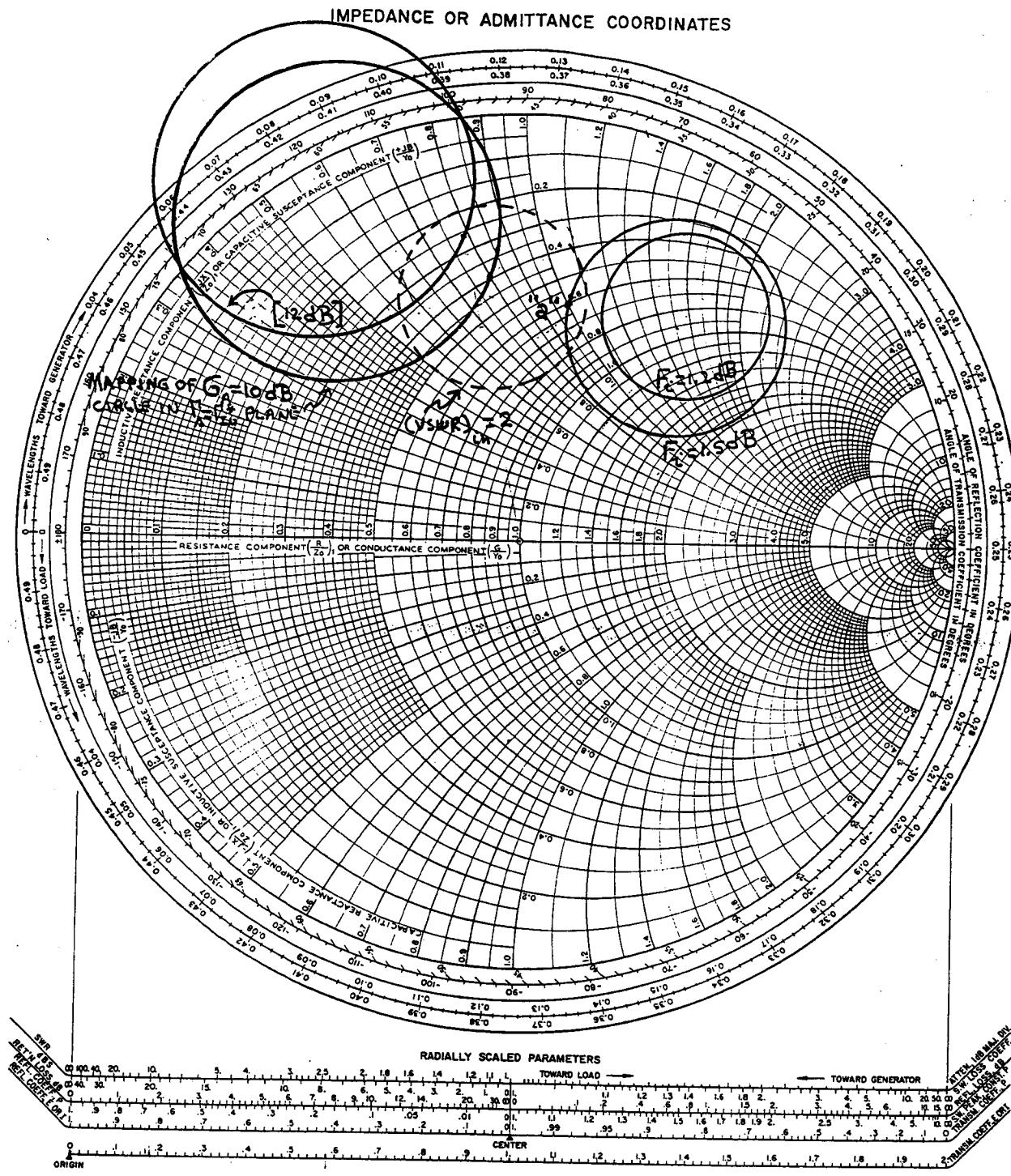

$$4.12) K = 1.04, \Delta = 0.83 \angle -47.5^\circ \therefore \text{UNCONDITIONALLY STABLE}$$

$G_{p,\max} = 5.166$ OR 7.13 dB . CONSIDER THE $G_p = 6 \text{ dB}$ AND 5 dB CIRCLES.

$G_p = 6 \text{ dB}$ CIRCLE IN THE $\Gamma_L = \Gamma_{IN}^*$ PLANE: $C_L = 0.257 \angle -10^\circ$, $R_L = 0.443$


$G_p = 5 \text{ dB}$ CIRCLE IN THE $\Gamma_L = \Gamma_{IN}^*$ PLANE: $C_L = 0.223 \angle -10^\circ$, $R_L = 0.541$

$F_i = 2.1 \text{ dB}$ CIRCLE IN THE Γ_L PLANE: $C_{F_i} = 0.569 \angle 71^\circ$, $R_{F_i} = 0.185$

$F_i = 2.3 \text{ dB}$ CIRCLE IN THE Γ_L PLANE: $C_{F_i} = 0.539 \angle 71^\circ$, $R_{F_i} = 0.262$

THESE CIRCLES ARE DRAWN IN THE SMITH CHART. SELECTING Γ_L AT POINT "a" RESULTS IN $F_i < 2.1 \text{ dB}$, $G_p = 6 \text{ dB}$, AND $(VSWR)_{in} = 1$. THAT IS:

Γ_L	Γ_{IN}	Γ_{OUT}	$ G_p(\text{dB}) $	$ F_i(\text{dB}) $	$(VSWR)_{in}$	$ \Gamma_b $	$(VSWR)_{out}$	
$0.44 \angle 63^\circ$	$0.86 \angle 50.5^\circ$	$0.44 \angle -63^\circ$	$0.765 \angle -44.70$	6	2	1	0.355	2.1

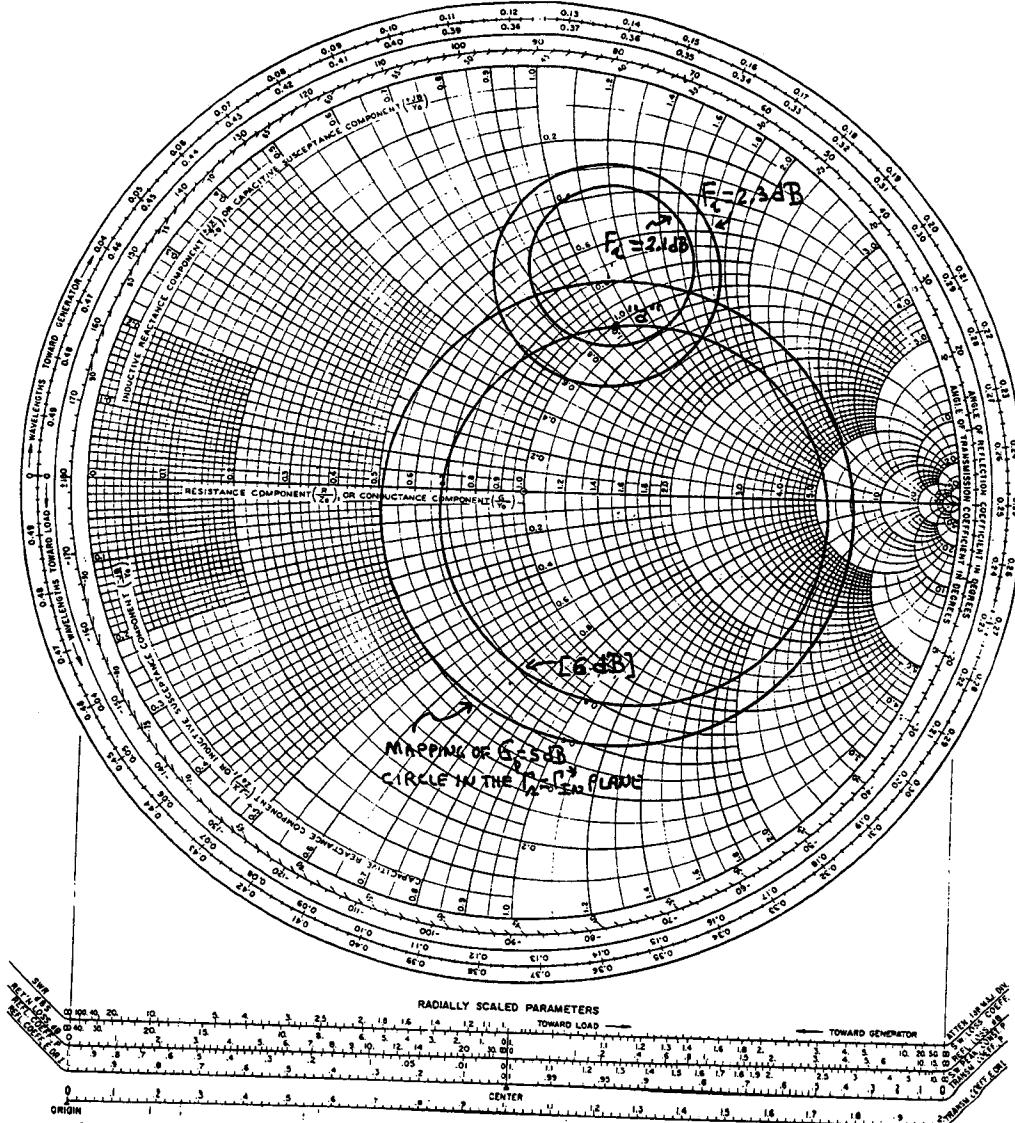

$$4.13) G_A(\text{dB}) = 14 + 14 + 14 - 7.5 + 16 + 16 = 66.5 \text{ dB}$$

THE NOISE FIGURE OF THE LNB IS DETERMINED BY THE NOISE FIGURE OF THE LNA (I.E., THE FIRST 3 AMPLIFIERS).

$$F = F_1 + \frac{F_2 - 1}{G_{A1}} + \frac{F_3 - 1}{G_{A1}G_{A2}} = 10^{0.05} + \frac{10^{0.09} - 1}{10^{1.4}} + \frac{10^{0.11} - 1}{10^{1.4} \cdot 10^{1.4}} = 1.131 \text{ OR } 0.54 \text{ dB}$$

THE CONTRIBUTION TO F FROM THE MIXER, AMP. 5, AND AMP. 6 IS NEGLECTABLE.

4.14) THE FOLLOWING CALCULATIONS ARE MADE:

$f(\text{MHz})$	$ S_{21} ^2$	$G_{A,\max}$	$G_{L,\max}$	$G_{TU,\max}$
150	25 (14dB)	0.45 dB	7.6 dB	22 dB
250	16 (12dB)	0.38 dB	5.8 dB	18.2 dB
400	7.94 (9dB)	0.28 dB	4.6 dB	13.9 dB

OBSERVE THAT $G_{A,\max}$ IS VERY SMALL AT THE THREE FREQUENCIES OF INTEREST. HENCE, ONLY THE LOAD MATCHING NETWORK WILL BE USED TO COMPENSATE FOR THE VARIATIONS IN $|S_{21}|^2$. THE INPUT MATCHING NETWORK CAN BE DESIGNED TO PROVIDE A GOOD (VSWR)_{in}, OR FOR $G_L = 0 \text{ dB}$.

FOR $G_{TU} = 12 \text{ dB}$, DESIGN G_L TO HAVE -2 dB AT 150 MHz, 0 dB AT 250 MHz, AND 3 dB AT 400 MHz.


$f(\text{MHz})$	$G_L(\text{dB})$	g_L	C_{g_L}	γ_{g_L}
150	-2	0.109	0.378 6°	0.62
250	0	0.260	0.494 15°	0.494
400	3	0.687	0.7 26°	0.242

THE GAIN CIRCLES ARE DRAWN IN THE SMITH CHART. AFTER SOME TRIALS AND ERRORS, THE FOLLOWING MATCHING CIRCUIT WAS OBTAINED:

$$Z_{L_1} = j\omega L_1$$


$$Y_{L_2} = -j/\omega L_2$$

$$Z_{L_3} = j\omega L_3$$

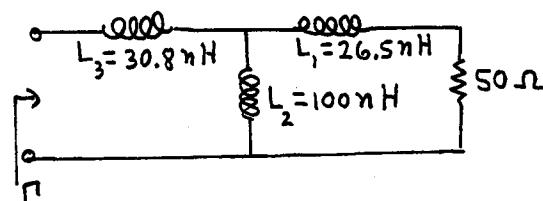

$f(\text{MHz})$	Z_{L_1}	$\beta_{L_1} = \frac{Z_{L_1}}{50}$	Y_{L_2}	γ_{L_2}	Z_{L_2}	β_{L_2}
150	$j24.97$	$j0.5$	$-j10.61 \text{ mS}$	$-j0.53$	$j29.03$	$j0.58$
250	$j41.62$	$j0.83$	$-j6.36 \text{ mS}$	$-j0.32$	$j48.4$	$j0.97$
400	$j66.6$	$j1.33$	$-j3.98 \text{ mS}$	$-j2$	$j77.4$	$j1.55$

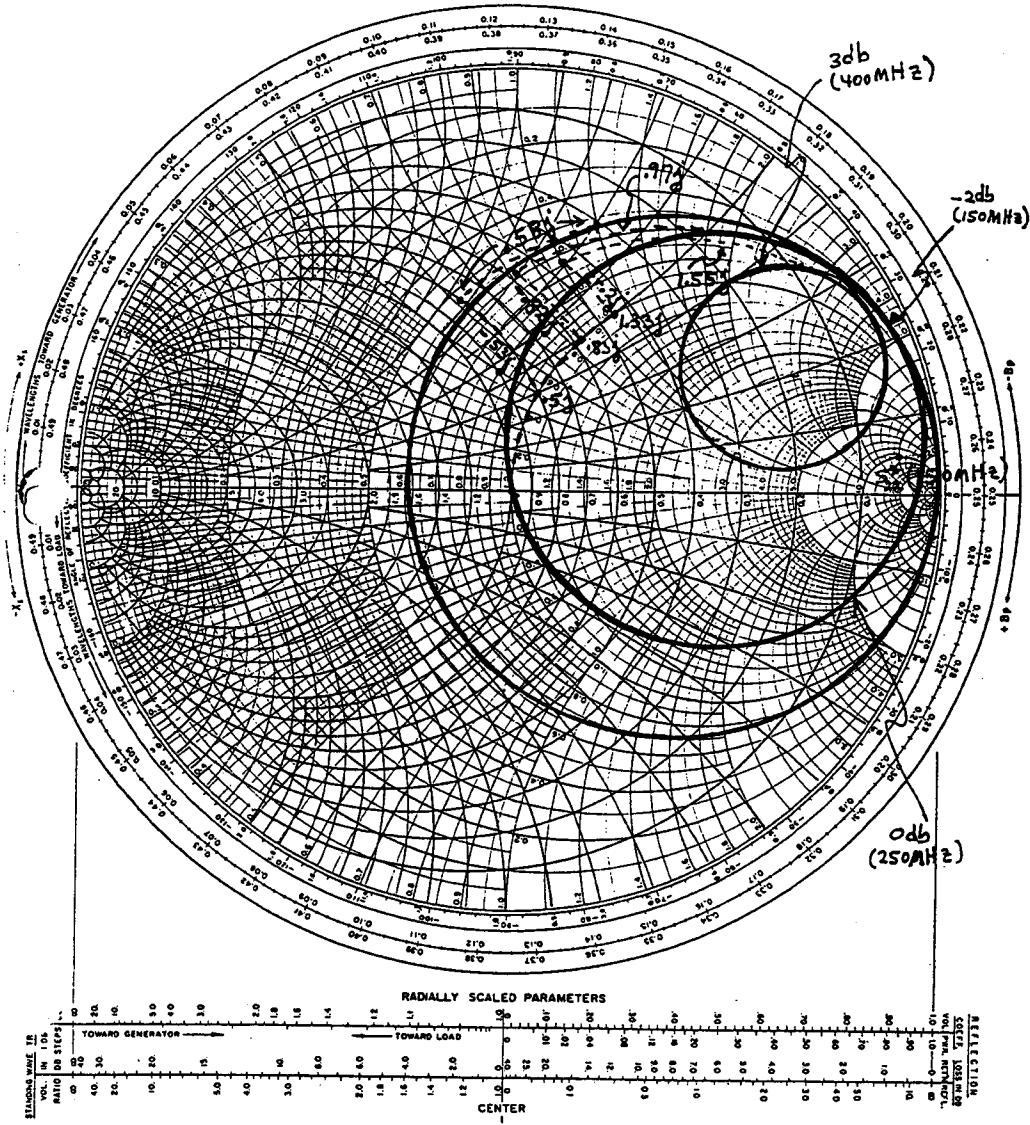NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES




$$4.15) \quad G_{TU} = G_a G_o G_L, \quad G_{TU}(\text{dB}) = G_a(\text{dB}) + G_o(\text{dB}) + G_L(\text{dB})$$

$f(\text{GHz})$	$G_{a,\text{max}}(\text{dB})$	$G_o = S_{21} ^2(\text{dB})$	$G_{L,\text{max}}(\text{dB})$	$G_{TU,\text{max}}(\text{dB})$
1	2.3	14.05	4.25	20.6
2	1.86	9.97	3.6	15.43

NOISE CIRCLE CALCULATIONS:


f (GHz)	F_i (dB)	C_{F_i}	γ_{F_i}
1	2	0.395 23°	0.378
	3	0.286 23°	0.591
	4	0.212 23°	0.708
2	2	0.377 88°	0.261
	3	0.304 88°	0.477
	4	0.244 88°	0.604

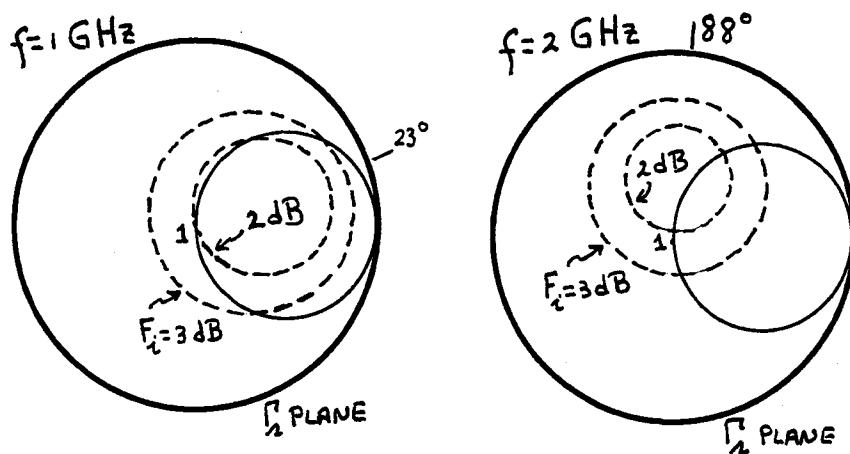

IT IS SEEN THAT THE NOISE FIGURE IS LESS THAN 3 dB AT 1 GHz AND 2 GHz WITH $\Gamma_2 = 0$. THE INPUT MATCHING NETWORK IS DESIGNED WITH $\Gamma_2 = 0$, AND IT FOLLOWS THAT $G_2 = 0$ dB.

A DESIGN FOR $G_{TU} = 10$ dB REQUIRES THAT $G_L = -4$ dB AT 1 GHz, AND $G_L = 0$ dB AT 2 GHz. THAT IS,
AT 1 GHz: $G_{TU} = 0 + 14.05 - 4 \approx 10$ dB ; AT 2 GHz: $G_{TU} = 0 + 9.97 + 0 \approx 10$ dB

A MATCHING CIRCUIT FOR THIS DESIGN IS :

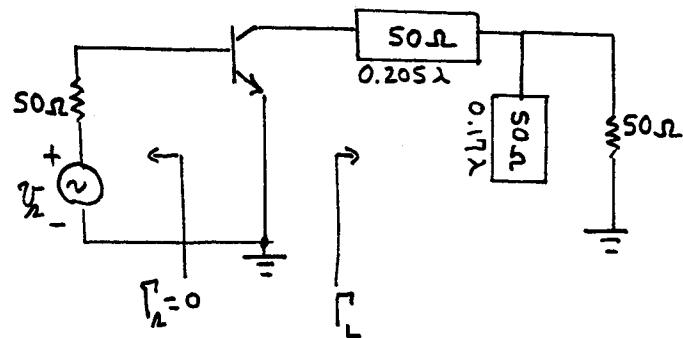

4.16) (a) $S_{11a} = S_{11b} = S_{11}$ $S_{21a} = S_{21b} = S_{21}$
 $S_{12a} = S_{12b} = S_{12}$ $S_{22a} = S_{22b} = S_{22}$

$$S_{11} = \frac{e^{-\delta\pi}}{2} (S_{11a} - S_{11b}) = 0, \text{ (VSWR)}_{in} = 1$$

$$S_{22} = \frac{e^{-\delta\pi}}{2} (S_{22a} - S_{22b}) = 0, \text{ (VSWR)}_{out} = 1$$

$$G_T = (0.5)^2 |S_{21a} + S_{21b}|^2 = (0.5)^2 [2(3.4)]^2 = 11.56 \text{ OR } 10.6 \text{ dB}$$

(b) $S_{11b} = 0.525 \angle 168^\circ, S_{12b} = 0.084 \angle 63^\circ, S_{21b} = 3.57 \angle 73.5^\circ, S_{22b} = 0.42 \angle 42.75^\circ$

$$S_{11} = \frac{e^{-\delta\pi}}{2} (0.5 \angle 160^\circ - 0.525 \angle 168^\circ) = 0.038 \angle -125.2^\circ, \text{ (VSWR)}_{in} = \frac{1+0.038}{1-0.038} = 1.08$$

$$S_{22} = \frac{e^{-\delta\pi}}{2} (0.4 \angle -45^\circ - 0.42 \angle -42.75^\circ) = 0.013 \angle -5^\circ, \text{ (VSWR)}_{out} = \frac{1+0.013}{1-0.013} = 1.03$$

$$G_T = (0.5)^2 |3.4 \angle 70^\circ + 3.57 \angle 73.5^\circ|^2 = 12.13 \text{ OR } 10.8 \text{ dB}$$

4.17)(a) FOR IDENTICAL AMPLIFIERS: $S_{11} = S_{22} = 0$. THEN,

$$K = \frac{1 + |\Delta|^2}{2|S_{12}S_{21}|} = \frac{1 + |S_{12}S_{21}|^2}{2|S_{12}S_{21}|} = \frac{1 + P^2}{2P}, P = |S_{12}S_{21}|$$

THE MINIMUM VALUE OF K OCCURS WHEN $P=1$, AND IT IS $K=1$.

(b) $S_{11} = 0, S_{22} = 0$

$$S_{21} = \frac{e^{-\delta\frac{\pi}{2}}}{2} (S_{21a} + S_{21b}) = \frac{e^{-\delta\frac{\pi}{2}}}{2} 2(-10.9 + j7.895) = 7.895 + j10.9$$

$$S_{12} = \frac{e^{-\delta\frac{\pi}{2}}}{2} (S_{12a} + S_{12b}) = \frac{e^{-\delta\frac{\pi}{2}}}{2} 2(0.009 + j0.015) = 0.015 - j0.009$$

$$P = |S_{12}S_{21}| = |0.017(13.46)| = 0.235, |\Delta| < 1 \text{ AND}$$

$$K = \frac{1 + (0.235)^2}{2(0.235)} = 2.25 \therefore \text{UNCONDITIONALLY STABLE.}$$

4.18) $\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 1/R_2 & -1/R_2 \\ \frac{g_m}{1+g_m R_1} - \frac{1}{R_2} & \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$

FROM TABLE 1.8.1 : $y'_{11} = y_{11} Z_0 = \frac{Z_0}{R_2}, y'_{12} = y_{12} Z_0 = -\frac{Z_0}{R_2},$
 $y'_{21} = y_{21} Z_0 = \frac{g_m Z_0}{1+g_m R_1} - \frac{Z_0}{R_2}, y'_{22} = y_{22} Z_0 = \frac{Z_0}{R_2}$

$$\Delta_3 = (1 + y'_{11})(1 + y'_{22}) - y'_{12}y'_{21} = (1 + \frac{Z_0}{R_2})^2 + \frac{Z_0}{R_2} \left(\frac{g_m Z_0}{1+g_m R_1} - \frac{Z_0}{R_2} \right)$$

OR $\Delta_3 = 1 + 2\frac{Z_0}{R_2} + \frac{g_m Z_0^2}{R_2(1+g_m R_1)}$

$$S_{11} = \frac{(1-y'_{11})(1+y'_{22}) + y'_{12}y'_{21}}{\Delta_3} = \frac{1}{\Delta_3} \left[(1-\frac{Z_0}{R_2})(1+\frac{Z_0}{R_2}) + \frac{Z_0}{R_2} \left(\frac{Z_0}{R_2} - \frac{g_m Z_0}{1+g_m R_1} \right) \right]$$

$$\therefore S_{11} = \frac{1}{\Delta_3} \left[1 - \frac{g_m Z_0^2}{R_2(1+g_m R_1)} \right]$$

$$S_{22} = \frac{(1+y'_{11})(1-y'_{22}) + y'_{12}y'_{21}}{\Delta_3} = \frac{1}{\Delta_3} \left[1 - \frac{g_m Z_0^2}{R_2(1+g_m R_1)} \right]$$

$$S_{21} = -\frac{2y'_{21}}{\Delta_3} = \frac{-2}{\Delta_3} \left[\frac{g_m Z_0}{1+g_m R_1} - \frac{Z_0}{R_2} \right] = \frac{1}{\Delta_3} \left[\frac{-2g_m Z_0}{1+g_m R_1} + \frac{2Z_0}{R_2} \right]$$

$$S_{12} = -\frac{2y'_{12}}{\Delta_3} = \frac{-2}{\Delta_3} \left(-\frac{Z_0}{R_2} \right) = \frac{2Z_0}{\Delta_3 R_2}$$

4.19) IF S_{11} IS APPROXIMATED BY $0.97 \angle 0^\circ$, THE ASSOCIATED γ_{be} IS $3.28 \text{ k}\Omega$.

$$G_T = 10 = |S_{21}|^2 \Rightarrow S_{21} = -3.16$$

FROM (4.4.10):

$$R_2 = Z_0(1-S_{21}) = 50(1+3.16) = 208 \Omega$$

THE VALUE OF g_m FOR $(VSWR)_{in} \approx 1$ AND $(VSWR)_{out} \approx 1$ FOLLOWS

FROM (4.4.9). THAT IS,

$$g_m = \frac{R_2}{Z_0^2} = \frac{208}{50^2} = 83 \text{ mS}$$

4.20) $G_T = 10 = |S_{21}|^2 \Rightarrow S_{21} = -3.16$.

$$\text{FROM (4.4.10): } R_2 = Z_0(1-S_{21}) = 50(1+3.16) = 208 \Omega$$

AT THE LOWER FREQUENCIES THE VALUE OF $S_{11} = 0.65 \angle 1.74^\circ (6+j14 \text{ mS})$ CORRESPONDS TO AN γ_{be} OF 166.6Ω . HENCE, THE CONDITION $\gamma_{be} \gg R_2$ IS NOT SATISFIED, AND A SERIES FEEDBACK RESISTOR R_1 IS NEEDED.

$$\text{FROM (4.4.10): } g_{m(\text{min})} = \frac{1+3.16}{50} = 83 \text{ mS}$$


THE VALUE OF THE TRANSISTOR g_m AT THE LOWER FREQUENCIES (WITH

$$S_{21} \approx 34 \angle 180^\circ) \text{ IS: } g_m = -\frac{S_{21}}{2Z_0} = \frac{34}{2(50)} = 340 \text{ mS}$$

SINCE $g_m > g_{m(\text{min})}$, R_1 IS CALCULATED USING (4.4.7):

$$R_1 = \frac{Z_0^2}{R_2} - \frac{1}{g_m} = \frac{50^2}{208} - \frac{1}{0.34} = 9 \Omega$$

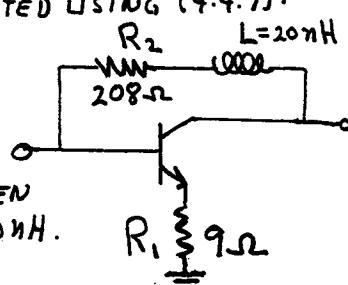AN INDUCTOR IS USUALLY NEEDED IN SERIES WITH R_2 IN ORDER TO REDUCE THE FEEDBACK AT THE HIGHER FREQUENCIES AND TO FLATTEN THE GAIN. TYPICAL VALUES OF L ARE $20 \mu\text{H}$ TO $30 \mu\text{H}$.



(b) THE FEEDBACK CIRCUIT WAS SIMULATED USING THE HEWLETT-PACKARD MDS PROGRAM. THE RESULTS ARE:

f (MHz)	S_{11}	S_{21}	S_{12}	S_{22}	$G_T = 10 \log S_{21} ^2$
100	$0.057 \angle -163^\circ$	$3.27 \angle 177.3^\circ$	$0.183 \angle -1.86^\circ$	$0.044 \angle 113.4^\circ$	10.3 dB
200	$0.062 \angle -146.6^\circ$	$3.29 \angle 174.5^\circ$	$0.182 \angle -3.8^\circ$	$0.083 \angle 95.4^\circ$	10.3 dB
400	$0.086 \angle -120.3^\circ$	$3.35 \angle 168.6^\circ$	$0.177 \angle -7.6^\circ$	$0.161 \angle 78.4^\circ$	10.5 dB
600	$0.132 \angle -105.3^\circ$	$3.45 \angle 161.7^\circ$	$0.169 \angle -11.4^\circ$	$0.243 \angle 66.4^\circ$	10.8 dB
800	$0.196 \angle -102.9^\circ$	$3.52 \angle 154^\circ$	$0.157 \angle -14.4^\circ$	$0.32 \angle 54.1^\circ$	10.9 dB
1000	$0.27 \angle -104.5^\circ$	$3.56 \angle 145.3^\circ$	$0.142 \angle -6.8^\circ$	$0.393 \angle 42.4^\circ$	11.0 dB
1500	$0.46 \angle -117.7^\circ$	$3.38 \angle 121.9^\circ$	$0.102 \angle -11.6^\circ$	$0.518 \angle 13.6^\circ$	10.6 dB

$$4.21) (a) Q_1 = \frac{X_C}{R} = \frac{1}{\omega_0 C R} = \frac{1}{2\pi 500 \cdot 10^6 (100 \cdot 10^{-4}) 5} = 0.637$$

$$Q_2 = \frac{f_0}{f_2 - f_1} = \frac{500 \cdot 10^6}{600 \cdot 10^6 - 400 \cdot 10^6} = 2.5$$

$$\Gamma_x = e^{-\pi(Q_2/Q_1)} = e^{-\pi(2.5/0.637)} = 4.4 \cdot 10^{-6}$$

$$(b) Q_1 = \frac{R}{X_C} = \omega_0 R C = 2\pi (9 \cdot 10^9) 50 (10^{-12}) = 2.83$$

$$Q_2 = \frac{f_0}{f_2 - f_1} = \frac{9 \cdot 10^9}{12 \cdot 10^9 - 6 \cdot 10^9} = 1.5$$

$$\Gamma_x = e^{-\pi(Q_2/Q_1)} = e^{-\pi(1.5/2.83)} = 0.19$$

$$4.22) \int_0^\infty \frac{1}{\omega^2} \ln \left| \frac{1}{\Gamma_x} \right| d\omega \leq \pi R C \Rightarrow \ln \left| \frac{1}{\Gamma_x} \right| \int_{\omega_a}^{\omega_b} \frac{d\omega}{\omega^2} = \pi R C$$

$$\text{OR } \ln \left| \Gamma_x \right| \left(\frac{1}{\omega_b} - \frac{1}{\omega_a} \right) = \pi R C \Rightarrow \ln \left| \Gamma_x \right| = \frac{\omega_a \omega_b \pi R C}{\omega_b - \omega_a} = \frac{-\pi \omega_0^2 R C}{\omega_b - \omega_a}$$

$$\text{OR } \ln \left| \Gamma_x \right| = -\pi \frac{Q_2}{Q_1} \text{ WHERE } \omega_0 = \sqrt{\omega_a \omega_b}, Q_2 = \frac{\omega_0}{\omega_b - \omega_a}, Q_1 = \frac{1}{\omega_0 R C}$$

$$\therefore \left| \Gamma_x \right| = e^{-\pi Q_2 / Q_1}, \omega_0 \text{ IS THE GEOMETRIC MEAN OF } \omega_a \text{ AND } \omega_b.$$

$$\text{FOR: } \int_0^\infty \frac{1}{\omega^2} \ln \left| \frac{1}{\Gamma} \right| d\omega \leq \frac{\pi L}{R} \Rightarrow \ln |\Gamma_x| \left(\frac{1}{\omega_b} - \frac{1}{\omega_a} \right) = \frac{\pi L}{R}$$

$$\text{OR } \ln |\Gamma_x| = \frac{-\pi \omega_0^2 L}{(\omega_b - \omega_a) R} = -\pi \frac{Q_2}{Q_1} \Rightarrow |\Gamma_x| = e^{-\pi Q_2 / Q_1}$$

$$\text{WHERE } \omega_0 = \sqrt{\omega_a \omega_b}, Q_2 = \frac{\omega_0}{\omega_b - \omega_a}, Q_1 = \frac{R}{\omega_0 L}$$

$$\text{FOR: } \int_0^\infty \ln \left| \frac{1}{\Gamma} \right| d\omega \leq \frac{\pi R}{L} \Rightarrow \ln |\Gamma_x| = -\frac{\pi R}{(\omega_b - \omega_a)} = -\pi \frac{Q_2}{Q_1} \Rightarrow |\Gamma_x| = e^{-\pi Q_2 / Q_1}$$

$$\text{WHERE } Q_2 = \frac{\omega_0}{\omega_b - \omega_a}, Q_1 = \frac{\omega_0 L}{R}$$

$$4.23)(a) \quad \Gamma_{IN} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} = \frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\frac{\partial \Gamma_{IN}}{\partial \Gamma_L} = \frac{(1 - S_{22} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} \Gamma_L S_{22}}{(1 - S_{22} \Gamma_L)^2}$$

$$S_{IN} = \left| \frac{\frac{d\Gamma_{IN}}{d\Gamma_L}/\Gamma_{IN}}{\frac{d\Gamma_L}{\Gamma_L}} \right| = \left| \frac{\Gamma_L (1 - S_{22} \Gamma_L) [(1 - S_{22} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} S_{22} \Gamma_L]}{(S_{11} - \Delta \Gamma_L) (1 - S_{22} \Gamma_L)^2} \right|$$

$$S_{IN} = \left| \frac{\Gamma_L (1 - S_{22} \Gamma_L) S_{12} S_{21} + S_{12} S_{21} S_{22} \Gamma_L^2}{(S_{11} - \Delta \Gamma_L) (1 - S_{22} \Gamma_L)} \right| = \frac{|S_{21}| |S_{12}| |\Gamma_L|}{|1 - S_{22} \Gamma_L| |S_{11} - \Delta \Gamma_L|}$$

$$(b) \quad |1 - S_{22} \Gamma_L| |S_{11} - \Delta \Gamma_L| = |S_{21} S_{12}| S_{IN}^{-1} |\Gamma_L|$$

$$|S_{11} - \Delta \Gamma_L - S_{11} S_{22} \Gamma_L + S_{22} \Delta \Gamma_L^2 - S_{21} S_{12} S_{IN}^{-1} \Gamma_L| = 0$$

$$\left| \Gamma_L^2 - \Gamma_L \left(\frac{\Delta + S_{11} S_{22} + S_{12} S_{21} S_{IN}^{-1}}{S_{22} \Delta} \right) + \frac{S_{11}}{S_{22} \Delta} \right| = 0$$

$$\therefore |\Gamma_L| = \left| \alpha \pm \left| \alpha^2 - \frac{S_{11}}{S_{22} \Delta} \right|^{\frac{1}{2}} \right| \text{ WHERE } \alpha = \frac{\Delta + S_{11} S_{22} + S_{12} S_{21} S_{IN}^{-1}}{2 S_{22} \Delta}$$

$$(c) \quad \Gamma_{OUT} = S_{22} + \frac{S_{12} S_{21} \Gamma_n}{1 - S_{11} \Gamma_n} = \frac{S_{22} - \Delta \Gamma_n}{1 - S_{11} \Gamma_n}$$

$$\frac{\partial \Gamma_{OUT}}{\partial \Gamma_n} = \frac{(1 - S_{11} \Gamma_n) S_{12} S_{21} + S_{12} S_{21} \Gamma_n S_{11}}{(1 - S_{11} \Gamma_n)^2}$$

$$S_{OUT} = \left| \frac{\frac{\partial \Gamma_{OUT}}{\partial \Gamma_n}/\Gamma_{OUT}}{\frac{d\Gamma_n}{\Gamma_n}} \right| = \left| \frac{\Gamma_n (1 - S_{11} \Gamma_n) [(1 - S_{11} \Gamma_n) S_{12} S_{21} + S_{12} S_{21} S_{11} \Gamma_n]}{(S_{22} - \Delta \Gamma_n) (1 - S_{11} \Gamma_n)^2} \right|$$

$$S_{OUT} = \left| \frac{\Gamma_n (1 - S_{11} \Gamma_n) S_{12} S_{21} + S_{12} S_{21} S_{11} \Gamma_n^2}{(S_{22} - \Delta \Gamma_n) (1 - S_{11} \Gamma_n)} \right| = \frac{|S_{21}| |S_{12}| |\Gamma_n|}{|1 - S_{11} \Gamma_n| |S_{22} - \Delta \Gamma_n|}$$

$$4.24) (a) \Gamma_1 = S_{11}^* = 0.75 \angle 100^\circ \text{ AND } \Gamma_L = S_{22}^* = 0.7 \angle 50^\circ$$

$$(b) Y_1 = \frac{1}{Z_1} = 7 - j23 \text{ mS}, Y_L = \frac{1}{Z_L} = 4 - j9 \text{ mS}$$

$$(BW)_{IN}^i = \frac{2f_0 G_{IN}}{|B_{IN}|} = \frac{2(8 \cdot 10^9) 0.007}{0.023} = 4.87 \text{ GHz}$$

$$(BW)_{OUT}^i = \frac{2f_0 G_{OUT}}{|B_{OUT}|} = \frac{2(8 \cdot 10^9) (0.004)}{0.009} = 7.11 \text{ GHz}$$

$$(c) (BW)_{IN} = 20\% (BW)_{IN}^i = 974 \text{ MHz}$$

$$Y_{IN} = 7 + j23 \text{ mS}$$

THE REQUIRED VALUE OF C_{IN} (FROM (4.6.5)) IS:

$$C'_{IN} = \frac{B_{IN,M}}{\omega_0} \left[\frac{(BW)_{IN}^i}{(BW)_{IN}} - 1 \right] = \frac{23 \cdot 10^3}{2\pi(8 \cdot 10^9)} \left[\frac{4.87}{0.974} - 1 \right] = 1.83 \text{ pF}$$

$$(d) Y'_{IN} = Y_{IN} + j\omega C'_{IN} = (7 + j23) 10^{-3} + j2\pi(8 \cdot 10^9) (1.83 \cdot 10^{-12}) = 7 + j115 \text{ mS}$$

$$\Gamma'_{IN} = 0.98 \angle -160.4^\circ, \therefore \Gamma_1 = \Gamma'_{IN}^* = 0.98 \angle 160.4^\circ, \Gamma_L = S_{22}^* = 0.7 \angle 50^\circ$$

$$G_{TU,max} = \frac{1}{1 - (0.98)^2} (2.5)^2 \frac{1}{1 - (0.7)^2} = 309.4 \text{ OR } 24.9 \text{ dB}$$

$$4.25) \Gamma_{ML} = 0.476 \angle 166^\circ \Rightarrow Y_{ML} = 51 - j15 \text{ mS}$$

$$\Gamma_{ML} = 0.846 \angle 72^\circ \Rightarrow Y_{ML} = 3 - j14 \text{ mS}$$

$$(BW)_{IN}^i = \frac{2(4 \cdot 10^9) 0.051}{0.015} = 27.2 \text{ GHz}, (BW)_{OUT}^i = \frac{2(4 \cdot 10^9) 0.003}{0.014} = 1.714 \text{ GHz}$$

THE VALUE OF L_{OUT} REQUIRED FOR $BW \approx (BW)_{OUT} = 400 \text{ MHz}$ IS

$$L'_{OUT} = \frac{1}{\omega_0 |B_{OUT,M}| \left[\frac{(BW)_{OUT}^i}{(BW)_{OUT}} - 1 \right]} = \frac{1}{2\pi(4 \cdot 10^9) 0.014 \left[\frac{1.714 \cdot 10^9}{0.4 \cdot 10^9} - 1 \right]} = 0.865 \text{ nH}$$

$$4.26) \text{ FROM (4.7.4): } P_{i,mds} = -174 + 10 \log_{10} 10^6 + 5 + 3 = -76.97 \text{ dBm}$$

$$\text{FROM (4.7.5): } P_{o,mds} = P_{i,mds} + G_A = -76.97 + 30 = -46.97 \text{ dBm.} \\ (\text{WITH } G_A = G_T)$$

$$DR = P_{1dB} - P_{o,mds} = 28 - (-46.97) = 74.97 \text{ dB}$$


$$P_{IP} = P_{1dB} + 10 = 28 + 10 = 38 \text{ dBm}$$

$$DR_f = \frac{2}{3} (P_{IP} - P_{o,mds}) = \frac{2}{3} (38 - (-46.97)) = 69.3 \text{ dB}$$

FOR NO THIRD-ORDER IM:

$$P_{out} = P_{o,mds} + DR_f = -46.97 + 69.3 = 22.3 \text{ dBm}$$

4.27)

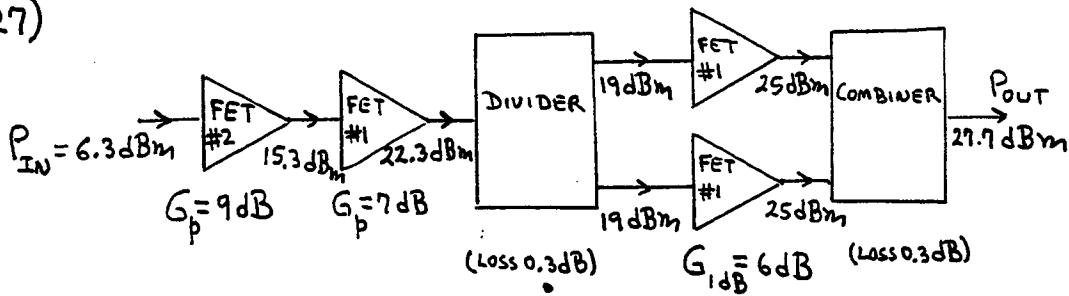


$$4.28) K = 1.61, \Delta = 0.313 \angle 18.8^\circ \therefore \text{UNCONDITIONALLY STABLE}$$

$$\Gamma_L = \Gamma_{LP} = 0.1 \angle 0^\circ \text{ AND } \Gamma_z = \Gamma_{SP} = \Gamma_{IN}^* = 0.324 \angle 146.6^\circ$$


OUTPUT MATCHING CIRCUIT:

$$Z_{LP} = 61.1 \Omega \text{ USING A } \lambda/4 \text{ TRANSFORMER}$$

$$Z_0 = \sqrt{61.1(50)} = 55.3 \Omega$$

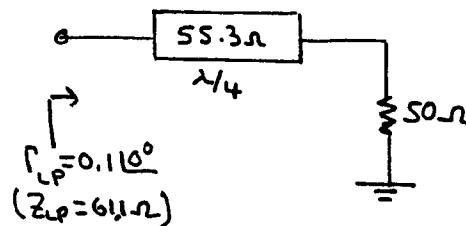

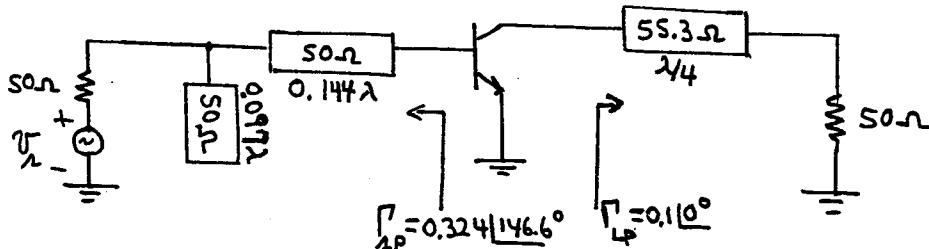INPUT MATCHING CIRCUIT: USE A SHUNT STUB (OPEN CIRCUIT) OF LENGTH 0.097λ FOLLOWED BY A SERIES TRANSM. LINE OF LENGTH 0.144λ .



$$4.29) P_{IN} = \frac{E_{AVG}^2}{4(50)} = \frac{(79.5 \times 10^{-3})^2}{200} = 3.16 \times 10^{-5} \text{ W OR } -15 \text{ dBm}$$

$$P_{OUT} = P_{IN} + 13 + 13 + 10 + 9 = -15 + 45 = 30 \text{ dBm}$$

$$\text{OR } P_{OUT} = 1 \text{ W}$$

4.30) THE BLOCK DIAGRAM IS IDENTICAL TO THE ONE IN FIG. 4.7.18,
EXCEPT THAT $Z_n = 1.19 + j1.35 \Omega$ AND $Z_L = 8.1 - j4.1 \Omega$

4.31) YES.

$$5.1) \beta(j\omega) A_{v_0} = 1 \text{ OR } [\beta_r(j\omega) + j\beta_i(j\omega)] A_{v_0} = 1$$

$$\therefore A_{v_0} = \frac{1}{\beta_r(\omega)} \text{ AND } \beta_i(j\omega) = 0$$

$$\beta(j\omega) = \frac{10^{-5}}{1 + (\omega - 10^3)^2} - j \frac{10^{-5}(\omega - 10^3)}{1 + (\omega - 10^3)^2}$$

$$\beta_i(j\omega) = 0 \text{ WHEN } \omega = 10^3 \text{ rad/s}$$

$$\text{AT } \omega = \omega_0 = 10^3 \text{ rad/s : } \beta_r(j\omega_0) = 10^{-5}$$

$$\text{THEN, } A_{v_0} = \frac{1}{10^{-5}} = 10^5$$

$$5.2) X_L(j\omega_0) = j\omega_0 L + \frac{1}{j\omega_0 C} = 0 \text{ OR } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{50 \cdot 10^9 \cdot 10 \cdot 10^{-12}}} = 225 \text{ MHz}$$

$$R_L = \frac{R_o}{3} = \frac{30}{3} = 10 \Omega$$

$$5.3) B_L(j\omega_0) = j\omega_0 C + \frac{1}{j\omega_0 L} = 0 \text{ OR } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{25 \cdot 10^9 \cdot 5 \cdot 10^{-12}}} = 450 \text{ MHz}$$

$$G_L = \frac{G_o}{3} = \frac{40 \cdot 10^{-3}}{3} = 13.3 \text{ mS}$$

$$5.4) (a) Z_{IN}(A', \omega) = \frac{1}{G(A') + j\omega C} = \frac{G(A')}{G^2(A') + \omega^2 C^2} + j \frac{-\omega C}{G^2(A') + \omega^2 C^2}$$

$$\therefore R_{IN}(A', \omega) = \frac{G(A')}{G^2(A') + \omega^2 C^2} \text{ AND } X_{IN}(A', \omega) = \frac{-\omega C}{G^2(A') + \omega^2 C^2}$$

FROM (5.2.16), (5.2.17), AND (5.2.20), A STABLE OSCILLATION OCCURS

$$R_L = -R_{IN}(A', \omega) = \frac{-G(A')}{G^2(A') + \omega^2 C^2}$$

$$X_L = -X_{IN}(A', \omega) = \frac{\omega C}{G^2(A') + \omega^2 C^2}$$

AND

$$\left| \frac{\partial R_{IN}}{\partial A'} \right|_{A'=A_0} \left| \frac{\partial X_L}{\partial \omega} \right|_{\omega=\omega_0} > 0$$

$$(b) P = \frac{1}{2} |V|^2 |G(A')| = \frac{1}{2} A'^2 G_o (1 - A'/A_m') , \frac{\partial P}{\partial A'} = \frac{G_o}{2} \left(2A' - \frac{3A'^2}{A_m'} \right) = 0$$

OR $A' \equiv A_{o,\max} = \frac{2}{3} A_m'$. AT $A' = A_{o,\max}$ THE VALUE OF $G_{IN}(A')$ IS:

$$G_{IN}(A_{o,\max}) = -G_o/3 . \text{ THEREFORE: } G_L = G_o/3 .$$

5.5) $K = -0.505$, $\Delta = 0.933 \angle 141.9^\circ$ \therefore POTENTIALLY UNSTABLE

INPUT STABILITY CIRCLE: $C_2 = 1.56 \angle 2.55^\circ$, $r_2 = 0.789$

OUTPUT STABILITY CIRCLE: $C_L = 0.89 \angle -155.2^\circ$, $r_L = 0.295$

SELECT THE GATE TO SOURCE AS THE TERMINATING PORT. THE VALUE FOR Γ_T SELECTED IS $\Gamma_T = 0.5 \angle -145^\circ$.



THEN, $\Gamma_{IN} = 1.116 \angle 173^\circ$

$$Z_{IN} = -2.74 + j3.03 \Omega$$

LET $Z_L = \frac{2.74}{3} - j3.03 = 0.91 - j3.03 \Omega$



NEGLECTING THE 0.91Ω , Z_L CAN BE IMPLEMENTED WITH AN OPEN-CIRCUITED LINE OF LENGTH 0.24λ .

A DESIGN FOR THE OSCILLATOR IS:

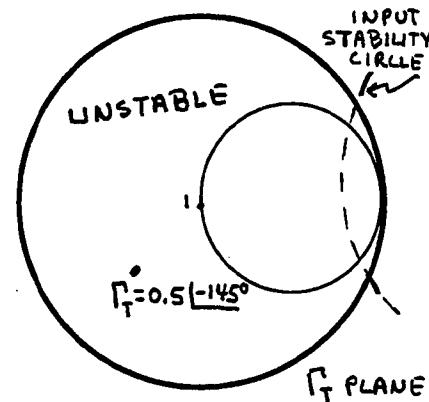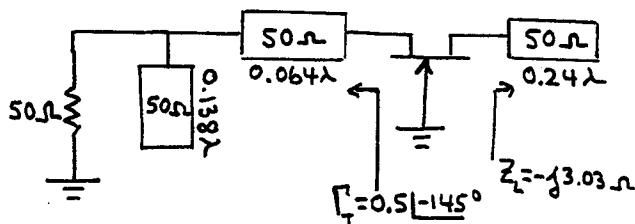

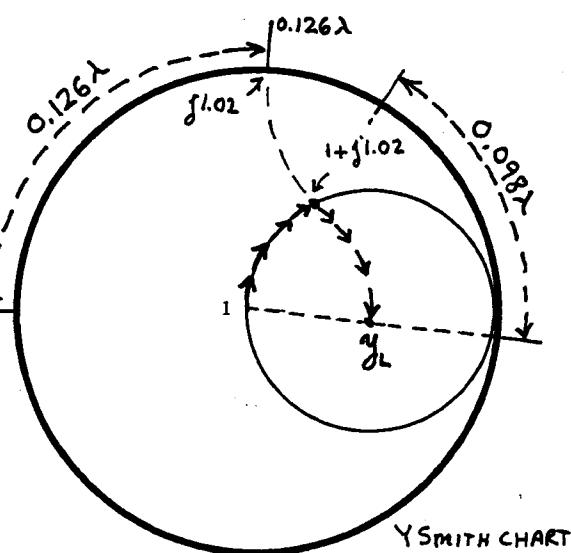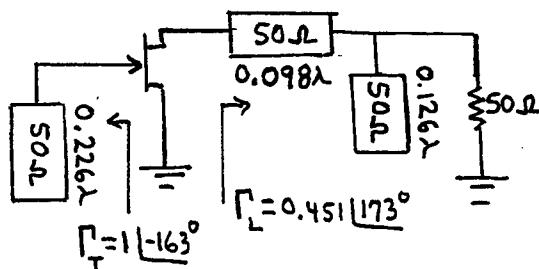5.6) $Z_L = 19 + j2.6 \Omega$, $\beta_L = 0.38 + j0.052$, $\Gamma_L = 0.451 \angle 173^\circ$

$$\gamma_L = \frac{1}{\beta_L} = 2.58 - j0.353$$



- 5.7) WITH $L = 0.5 \text{nH}$: $K = -0.834$, $\Delta = 1.02 \angle 157^\circ$ ∴ POTENTIALLY UNSTABLE
 INPUT STABILITY CIRCLE: $C_{IN} = 1.38 \angle -50.9^\circ$, $Y_{IN} = 2.1$
 OUTPUT STABILITY CIRCLE: $C_L = 0.78 \angle 119.7^\circ$, $Y_L = 1.39$

SELECTING THE OUTPUT PORT (i.e., BASE TO COLLECTOR) AS THE TERMINATING PORT WITH:

$$\Gamma_T = 0.5 \angle 30^\circ$$

$$\text{THEN: } \Gamma_{IN} = 1.126 \angle 172.4^\circ$$



$$Z_{IN} = -2.98 + j3.31 \Omega$$

$$\text{LET } Z_L = \frac{2.98}{3} - j3.31 = 0.99 - j3.31 \Omega$$

NEGLECTING THE 0.99Ω WE CAN DESIGN THE LOAD CIRCUIT WITH A CAPACITOR, NAMELY

$$-j3.31 = \frac{1}{WC} \text{ OR } C = \frac{1}{2\pi(210)3.31} = 24 \text{ pF}$$

A DESIGN FOR THE OSCILLATOR IS:

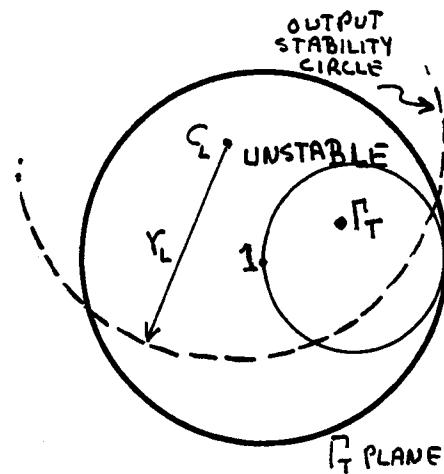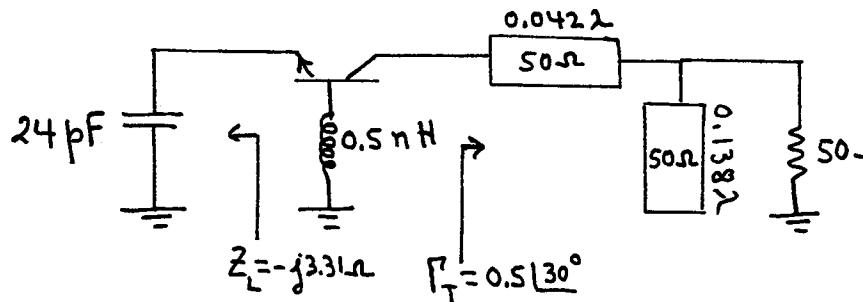

- 5.8) $K = 0.654$, $\Delta = 0.812 \angle -59.8^\circ$ ∴ POTENTIALLY UNSTABLE

From (5.4.4) AND (5.4.5): $C_{IN} = 0.78 \angle -162^\circ$, $Y_{IN} = 0.842$


$$\text{From (5.4.6): } \Gamma_{IN,max} = (0.78 + 0.842) \angle -162^\circ = 1.622 \angle -162^\circ$$

$$\text{From (5.4.7): } \Gamma_{T,0} = 1 \angle -174^\circ, Z_{T,0} = -j2.62 \Omega$$

$$Z_{IN,max} = -12.1 - j7.5 \Omega$$

THE LARGE-SIGNAL CHARACTERISTICS SHOW THAT A POWER OF 150 mW IS POSSIBLE WITH $Z_L = 50(0.2 - j0.35) = 10 - j17.5 \Omega$

THE BLOCK DIAGRAM OF THE OSCILLATOR IS:

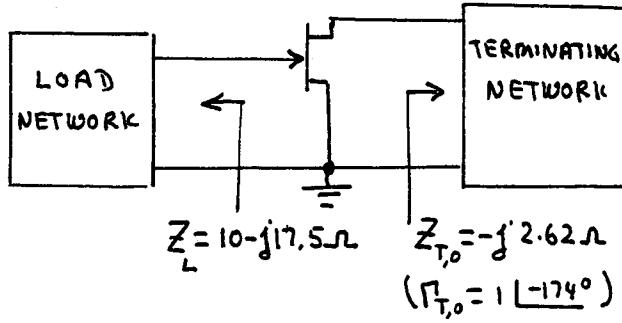

$$5.9) \quad \Gamma_{IN} = \frac{S_{11} - \Delta \Gamma_T}{1 - S_{22} \Gamma_T} = \frac{S_{11}(1 - |S_{22}|^2) - \Delta \Gamma_T(1 - |S_{22}|^2)}{(1 - S_{22} \Gamma_T)(1 - |S_{22}|^2)}$$

$$\Gamma_{IN} = \frac{S_{11} - S_{11} S_{22} S_{22}^* - S_{11} S_{22} \Gamma_T + S_{21} S_{12} \Gamma_T + \Delta \Gamma_T S_{22} S_{22}^*}{(1 - S_{22} \Gamma_T)(1 - |S_{22}|^2)}$$

ADDING AND SUBTRACTING IN THE NUMERATOR THE TERM $S_{21} S_{12} S_{22}^*$ GIVES

$$\Gamma_{IN} = \frac{S_{11} - \Delta S_{22}^* - S_{11} S_{22} \Gamma_T + \Delta \Gamma_T S_{22} S_{22}^* + S_{21} S_{12} (\Gamma_T - S_{22}^*)}{(1 - S_{22} \Gamma_T)(1 - |S_{22}|^2)}$$

$$\Gamma_{IN} = \frac{S_{11}(1 - S_{22} \Gamma_T) - \Delta S_{22}^*(1 - S_{22} \Gamma_T) + S_{21} S_{12} (\Gamma_T - S_{22}^*)}{(1 - S_{22} \Gamma_T)(1 - |S_{22}|^2)}$$

$$\Gamma_{IN} = \frac{S_{11} - \Delta S_{22}^*}{1 - |S_{22}|^2} + \frac{S_{12} S_{21}}{1 - |S_{22}|^2} \frac{\Gamma_T - S_{22}^*}{1 - S_{22} \Gamma_T} = \Gamma_{IN,0} + \alpha \Gamma_T'$$

WHERE $\Gamma_{IN,0} = \frac{S_{11} - \Delta S_{22}^*}{1 - |S_{22}|^2}$ AND $\alpha \Gamma_T' = \frac{S_{12} S_{21}}{1 - |S_{22}|^2} \frac{\Gamma_T - S_{22}^*}{1 - S_{22} \Gamma_T}$

IF α IS DEFINED AS: $\alpha = \frac{S_{12} S_{21}}{1 - |S_{22}|^2} \frac{1 - S_{22}^*}{1 - S_{22}}$, THEN

$$\Gamma_T' = \frac{\Gamma_T - S_{22}^*}{1 - S_{22} \Gamma_T} \frac{1 - S_{22}}{1 - S_{22}^*} . \text{ LETTING } \Gamma_T = \frac{Z_T - Z_0}{Z_T + Z_0} \text{ AND } S_{22} = \frac{Z_{22} - Z_0}{Z_{22} + Z_0}$$

$$\therefore \Gamma_T' = \frac{\left(\frac{Z_T - Z_0}{Z_T + Z_0}\right) - \left(\frac{Z_{22}^* - Z_0}{Z_{22}^* + Z_0}\right)}{1 - \left(\frac{Z_{22} - Z_0}{Z_{22} + Z_0}\right)\left(\frac{Z_T - Z_0}{Z_T + Z_0}\right)} \left(\frac{Z_{22}^* + Z_0}{Z_{22} - Z_0}\right) = \frac{Z_T - Z_{22}^*}{Z_T + Z_{22}}$$

$\Gamma_{IN,max}$ (SEE FIG. 5.4.3) OCCURS WHEN $|\Gamma_T'| = 1$ AND $|\alpha| = |\Gamma_{IN,0}|$. HENCE,

$$\Gamma_{IN,max} = \Gamma_{IN,0} + |\alpha| \hat{u}_{IN,0} \quad (1)$$

WHERE $\hat{u}_{IN,0}$ IS A UNIT VECTOR IN THE DIRECTION OF $\Gamma_{IN,0}$.

(b) (1) IS IDENTICAL TO (5.4.6) BECAUSE $\Gamma_{IN,0} = C_{IN}$, $|\alpha| = |\Gamma_{IN}|$, AND

$$\hat{u}_{IN,0} = \hat{C}_{IN}$$

$$\Gamma_{IN,max} = (|\Gamma_{IN,0}| + |\alpha|) \hat{C}_{IN}$$

WHICH IS THE SAME AS (5.4.6).

- 5.10) THE S PARAMETERS OF A SERIES IMPEDANCE Z IN A Z_0 SYSTEM WERE DERIVED IN EXAMPLE 1.6.1. IN THE CASE OF A DRO THE VALUE OF Z IS GIVEN BY 5.5.6, NAMELY

$$Z = \frac{R}{1+j2Q_u\delta} = \frac{2\beta Z_0}{1+j2Q_u\delta}$$

USING (1.6.24) AND (1.6.25) WE OBTAIN:

$$S_{11} = S_{22} = \frac{Z}{Z+2Z_0} = \frac{\beta}{\beta+1+j2Q_u\delta}$$

$$S_{21} = S_{12} = \frac{2Z_0}{Z+2Z_0} = \frac{1+j2Q_u\delta}{\beta+1+j2Q_u\delta}$$

- 5.11) AT 12 GHz: $K = 1.36$ AND $\Delta = 0.41 \angle 139.8^\circ$, \therefore UNCONDITIONALLY STABLE.

THE S PARAMETERS ARE CLOSE TO THOSE USED IN EXAMPLE 5.5.1. HENCE, THE DESIGN PROCEDURE IS SIMILAR TO THE ONE USED IN EXAMPLE 5.5.1.

USING A SERIES FEEDBACK CAPACITOR (SEE FIG. 5.5.12a) WITH $Z = -j120\Omega$ RESULTS IN A POTENTIALLY UNSTABLE CONFIGURATION WITH: $S_{11} = 1.255 \angle 117^\circ$, $S_{12} = 1.65 \angle -78.4^\circ$, $S_{21} = 1.87 \angle -23.2^\circ$, AND $S_{22} = 0.9 \angle 102^\circ$.

THE GATE TO GROUND PORT IS SELECTED AS THE TERMINATING PORT. THE STABILITY CIRCLE AT THE TERMINATING PORT IS SIMILAR TO THE ONE DRAWN IN FIG. 5.5.12b (i.e., $C_L = 0.773 \angle 26.5^\circ$ AND $\gamma_L = 0.805$).

WITH $\beta = 10$: $R = 10 (2 \times 50) = 1000\Omega$ AND $\Gamma_T = \frac{10}{10+1} e^{-j2\theta} = \frac{10}{11} e^{-j2\theta}$

LETTING $\lambda = \lambda/4$ (i.e., $\theta = \pi/2$), THEN $\Gamma_T = 0.909 \angle -180^\circ$, $\Gamma_{IN} = 2.68 \angle 33.4^\circ$ (OR $Z_{IN} = -83.4 + j39.8\Omega$), AND Z_L IS SELECTED AS: $Z_L = 27.8 - j39.8\Omega$

THE DRO CIRCUIT IS SHOWN IN FIG. 5.5.12c.

- 5.12) FROM THE RESULTS IN EXAMPLE 5.2.2 A STABLE OSCILLATION OCCURS AT

$$\omega_o = \frac{1}{\sqrt{L_o C_o}}$$

AT THE AMPLITUDE $A' = A'_o$, DETERMINED BY

$$G_{IN}(A'_o) + G_o = 0$$

THE OSCILLATION IS STABLE (SEE EXAMPLE 5.2.2) BECAUSE

$$\left. \frac{\partial G_{IN}(A')}{\partial A'} \right|_{A'=A'_o} \left. \frac{\partial B_o(\omega)}{\partial \omega} \right|_{\omega=\omega_o} > 0$$

$$\text{WHERE } B_o(\omega) = j\omega C_o + \frac{1}{j\omega L_o}$$

THE START OF OSCILLATION CONDITION REQUIRES THAT


$$|G_{IN}(0)| + G_o > 0$$

$$5.13) \quad Z_L = 8.5 - j24 \Omega, \quad \beta_L = \frac{Z_L}{50} = 0.17 - j0.48, \quad y_L = 0.656 + j1.85$$

THE MATCHING USED IS SHOWN IN THE Y SMITH CHART. THE MOTION FROM THE ORIGIN TO "a" IS IMPLEMENTED WITH A SHORT-CIRCUITED SHUNT STUB. THE MOTION FROM "a" TO "b" IS IMPLEMENTED WITH A SERIES TRANSMISSION LINE OF LENGTH 0.018λ . THE MOTION FROM "b" TO y_L (i.e., ALONG A CONSTANT CONDUCTANCE CIRCLE) IS IMPLEMENTED WITH A CAPACITOR IN SHUNT. THIS CAPACITOR CAN BE OBTAINED USING A VARACTOR DIODE. THE VALUE OF THE CAPACITOR IS:

$$y_C = j1.85 - (j1.8) = j3.65$$
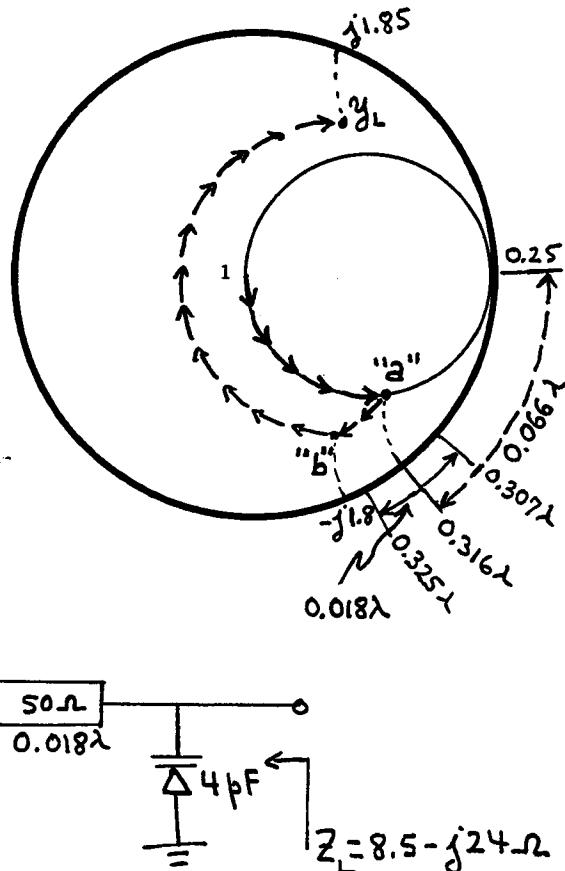
$$\therefore C = \frac{3.65/50}{2\pi(2.75 \cdot 10^9)} = 4 \text{ pF}$$



5.14) IT IS A POTENTIALLY UNSTABLE TRANSISTOR

$$\text{OUTPUT STABILITY CIRCLE: } C_L = 0.921 \angle -76.1^\circ, \quad Y_L = 0.858$$


SEVERAL VALUES OF Γ_T IN THE UNSTABLE REGION SHOULD BE TRIED, AND THE ASSOCIATED Γ_{IN} CALCULATED. FOR THIS DESIGN WE USED

$$\Gamma_T = 0.7 \angle -130^\circ, \text{ THEN } \Gamma_{IN} = 2.09 \angle -136^\circ \text{ AND } Z_{IN} = -20 - j17.2 \Omega.$$

$$\text{LET } Z_L = \frac{20}{3} + j17.2 = 6.7 + j17.2 \quad \text{OR} \quad \Gamma_L = 0.786 \angle 141.5^\circ$$

AN IMPLEMENTATION OF THE OSCILLATOR IS:

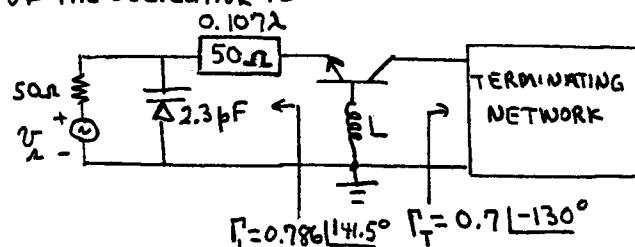THE CAPACITOR ($C = 2.3 \text{ pF}$) IS IMPLEMENTED WITH A VARACTOR DIODE).



$$5.15) (a) P_{out} = P_{sat} \left(1 - e^{-G_o P_{IN}/P_{sat}}\right) \quad (1)$$

MAXIMUM OSCILLATOR POWER OCCURS WHEN $P_{out} - P_{IN}$ IS A MAXIMUM, OR $\frac{\partial P_{out}}{\partial P_{IN}} = 1$. SINCE

$$\frac{\partial P_{out}}{\partial P_{IN}} = P_{sat} \left(-\frac{G_o}{P_{sat}}\right) \left(e^{-G_o P_{IN}/P_{sat}}\right) = G_o e^{-G_o P_{IN}/P_{sat}} = 1$$

THEN, $e^{-G_o P_{IN}/P_{sat}} = \frac{1}{G_o}$ OR $P_{IN} = P_{sat} \frac{\ln G_o}{G_o}$ (2)

SUBSTITUTING (2) INTO (1), P_{out} CAN BE EXPRESSED AS:

$$P_{out} = P_{sat} \left(1 - \frac{1}{G_o}\right) \quad (3)$$

FROM (3) AND (2), THE MAXIMUM OSCILLATOR POWER ($P_{osc}^{(max)}$) IS

$$P_{osc}^{(max)} = P_{out} - P_{IN} = P_{sat} \left(1 - \frac{1}{G_o} - \frac{\ln G_o}{G_o}\right)$$

(b) $G_o = 7.5 \text{ dB}$ OR 5.623

$$P_{sat} = 1 \text{ W}$$

$$P_{osc}^{(max)} = 1 \left(1 - \frac{1}{5.623} - \frac{\ln 5.623}{5.623}\right) = 0.515 \text{ W}$$

(c)

